

CS 303

Logic & Digital System Design

Ömer Ceylan

**. Sabancı .
Universitesi**



Chapter 7 Part I

Memory & Programmable Logic

- A device
 - to which binary data is transferred for storage and
 - from which data is available when needed for processing
- When data processing takes place
 - data from the memory is transferred to selected register in the processing unit
 - Intermediate and final results obtained in the processing unit are transferred back to the memory for storage

- Used to communicate with an input/output device
 - binary information received from an input device is stored in memory
 - information transferred to an output device is taken from memory
- A collection of cells capable of storing a large quantity of binary information
- Two types
 - RAM (random-access memory)
 - ROM (read-only memory)

- RAM
 - We can read stored information (read operation)
 - Accepts new information for storage (write operation)
 - Perform both read and write operation
- ROM
 - only performs read operation
 - existing information cannot be modified
 - “Programming” the device
 - specifying the binary information and storing it within the programmable device
 - a.k.a. programmable logic device

Programmable Logic Devices


- PLD
 - ROM is one example
 - Programmable Logic Array (PLA)
 - Programmable Array Logic (PAL)
 - Field Programmable Gate Array (FPGA)
- PLD is
 - an integrated circuit (IC) with internal logic gates
 - Interconnection between the gates can be programmed through fuses
 - At the beginning they are all intact
 - By programming we remove some of them, while keeping the others

Random Access Memory (RAM)

- RAM : the reason for the name
 - The time it takes to transfer information to or from any desired random location is always the same.
- Word
 - group of bits in which a memory unit stores information
 - At one time, memory move in and out certain number of bits
 - 8 bit – byte
 - 16 bit
 - 32 bit
 - Capacity is usually given in number of bytes

Memory Unit


- Block diagram

 

- A memory unit is specified by
 1. the number of words it contains
 2. number of bits in each word
- Each word (or location for a word) in memory is assigned an identification number
 - address
 - 0 to 2^k-1
- Selection
 - selection process to read and write a word is done by applying k-bit address to the address lines
 - A **decoder** accepts the address and selects the specified word in the memory

Memory Map and Address Selection

- 1 K x 16 Memory

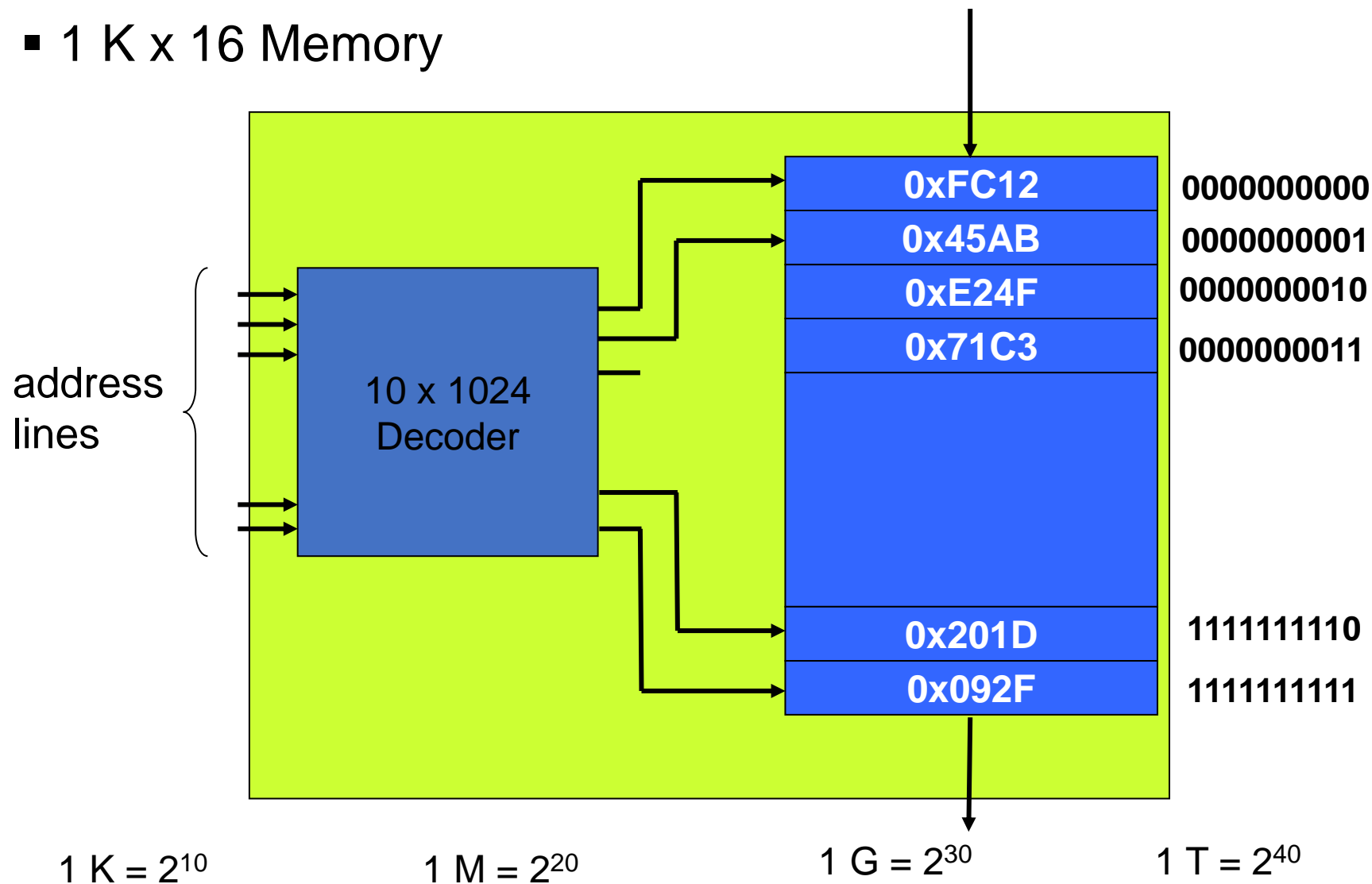

Write and Read Operations

- Write
 - transfer in
- Read
 - transfer out
- Steps for write operation
 1. Apply the binary address of the desired word to the address lines
 2. Apply the data word that is be stored in memory to the data input lines
 3. Activate the “write” input
- Steps for read operation
 1. Apply the binary address of the desired word to the address lines
 2. Activate the “read” input
 - The desired word will appear on the (data) output lines
 - reading does no affect the content of the word


Control Inputs to Memory Chip

- Commercial memory components usually provide a “memory enable” (or “chip select”) control input
- memory enable is used to activate a particular memory chip in a multi-chip implementation of a large memory

Memory Enable	Read/Write	Memory Operation
0	X	None
1	0	write
1	1	read

Timing

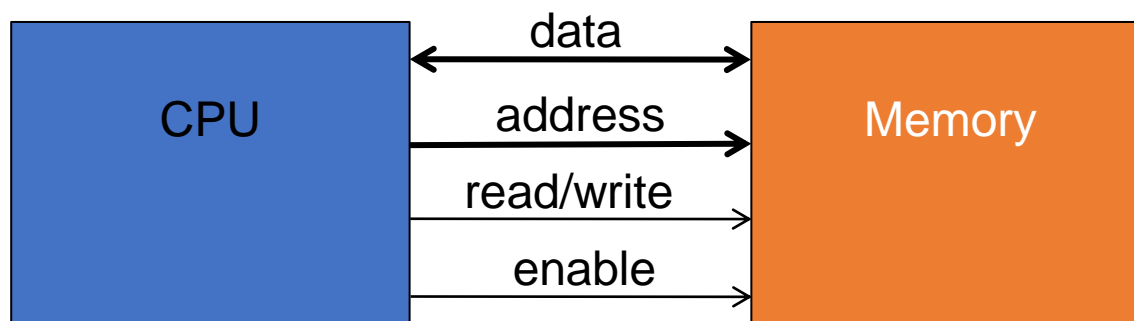
- Memory does not have to use an internal clock
 - It only reacts to the control inputs, e.g., “read” and “write”
 - operation of a memory unit is controlled by an external device (e.g. CPU) that has its own clock
- Access time
 - the time required to select a word and read it
- Cycle time
 - the time required to complete a write operation



Write Cycle

- CPU clock: 2 GHz
- Cycle time: 1.25 ns

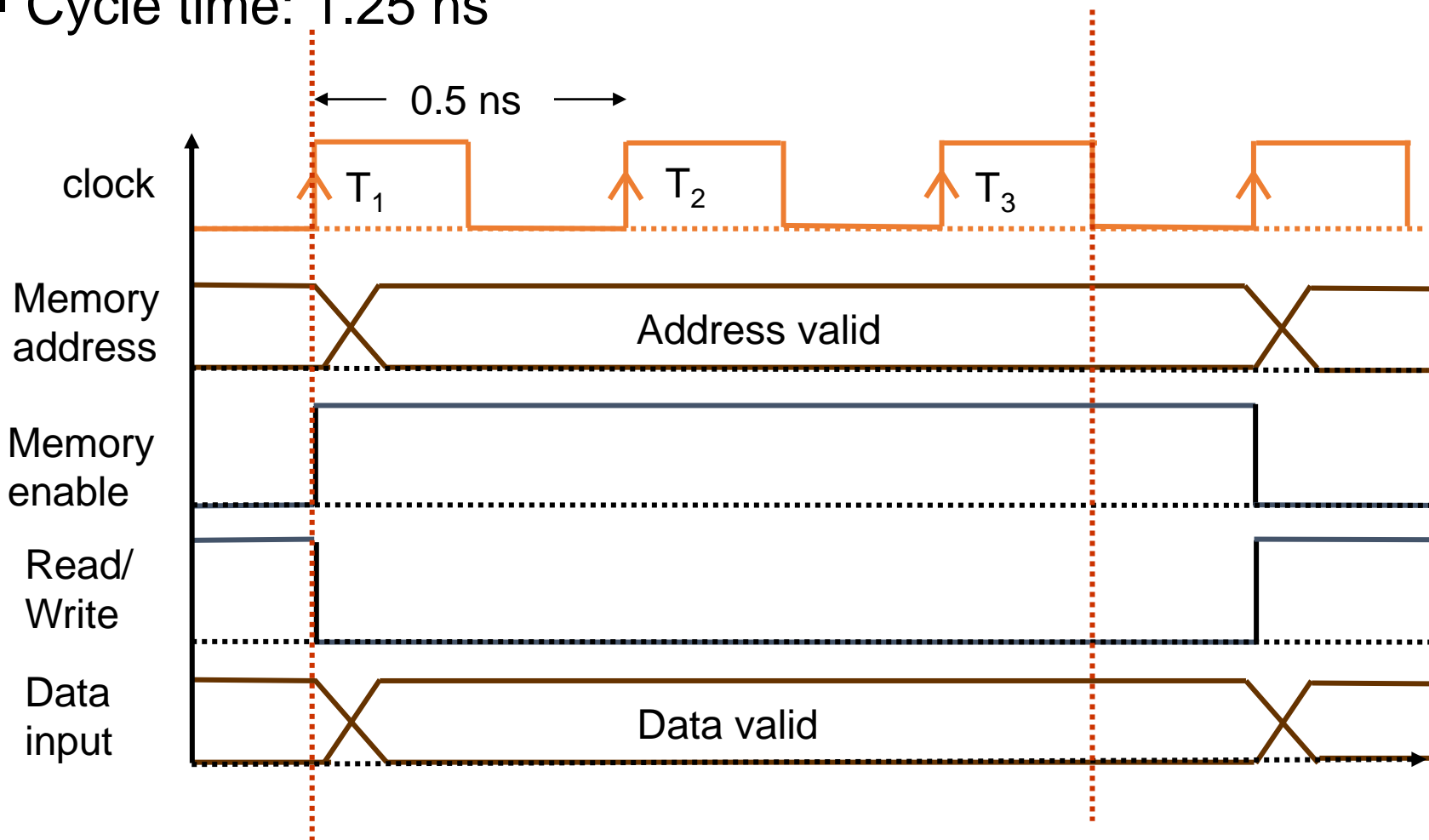
CPU must devote three clock cycles for each write operation



Read Cycle

- CPU clock: 2 GHz
- Access time: 1.25 ns

 The desired word appears at output, 1.25 ns after memory enable is activated





Types of Memory 1/2

- RAM
 - access time is always the same no matter where the desired data is actually located
- Sequential-access memory
 - Access time is variable
 - e.g., magnetic disks, tapes
- RAM
 - SRAM (static RAM)
 - latches, stores information as long as power is on
 - DRAM (dynamic RAM)
 - information is stored as charge on a capacitor
 - refreshing is necessary due to discharge




Types of Memory 2/2


- Volatile memory
 - When the power is turned off, the stored information is lost
 - RAM (SRAM or DRAM)
- Nonvolatile memory
 - retains the stored information even after removal of power
 - magnetic disks
 - data is represented as the direction of magnetization
 - ROM
 - programs needed to start a computer are kept in ROM

Memory Cell

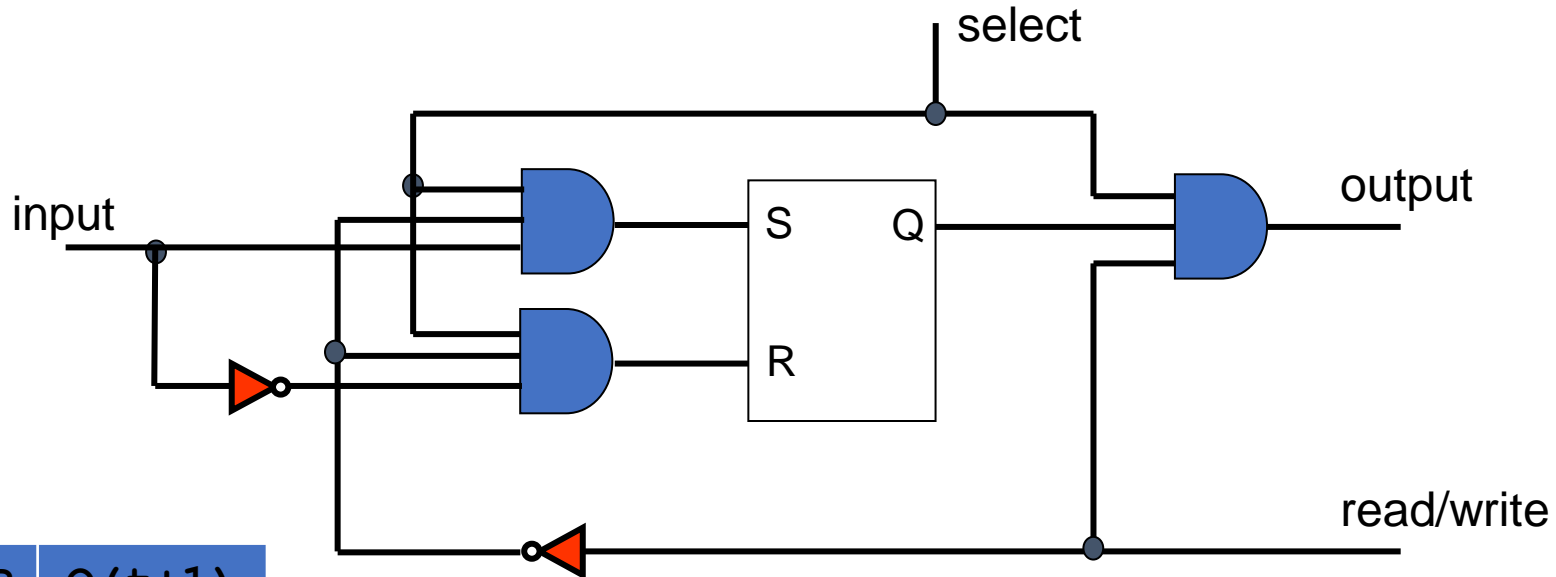
- Equivalent logic of a memory cell for storing one bit of information




S	R	$Q(t+1)$
0	0	Q
0	1	0
1	0	1
1	1	x

 

4 x 4 RAM

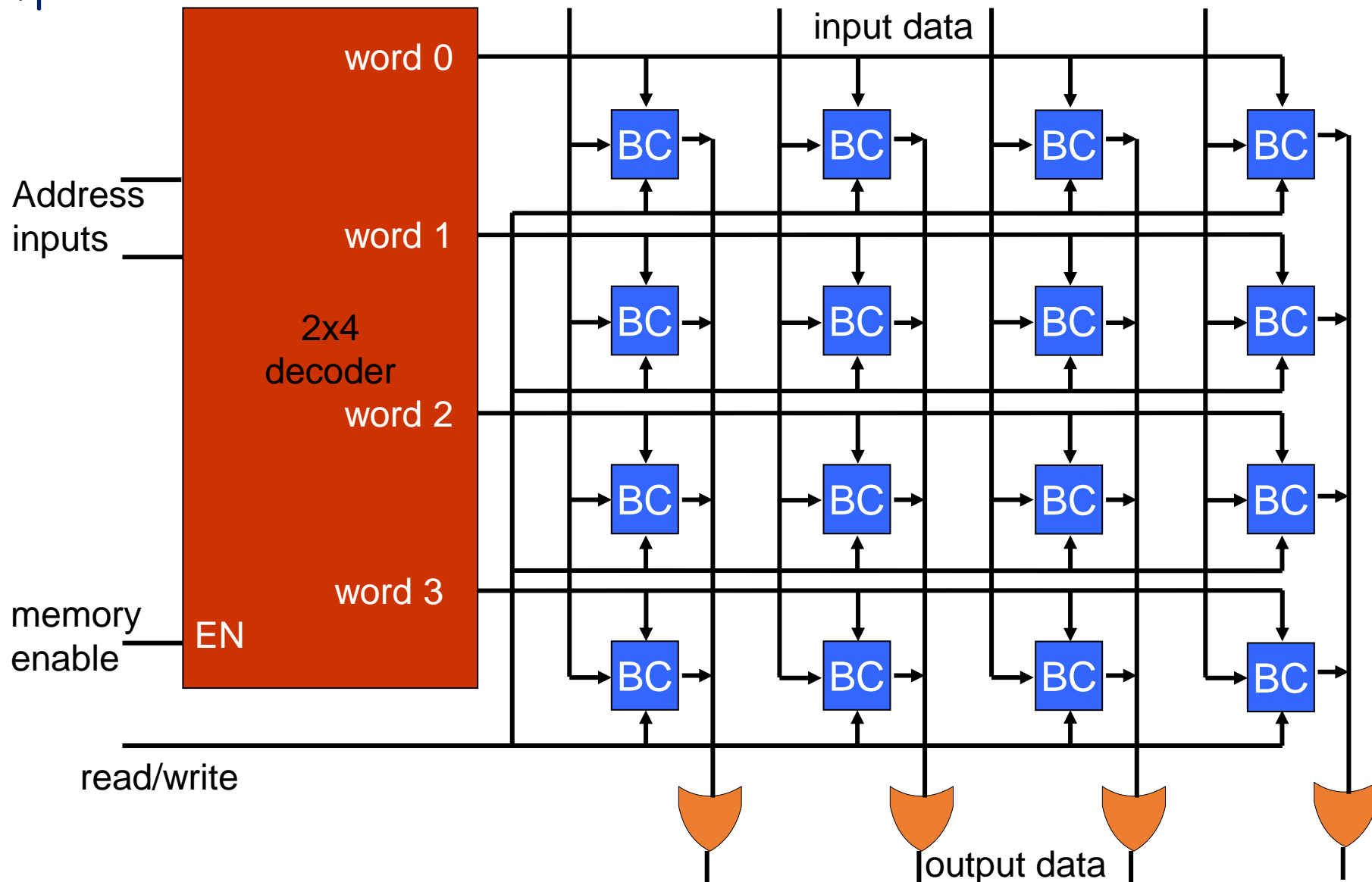


4 x 4 RAM

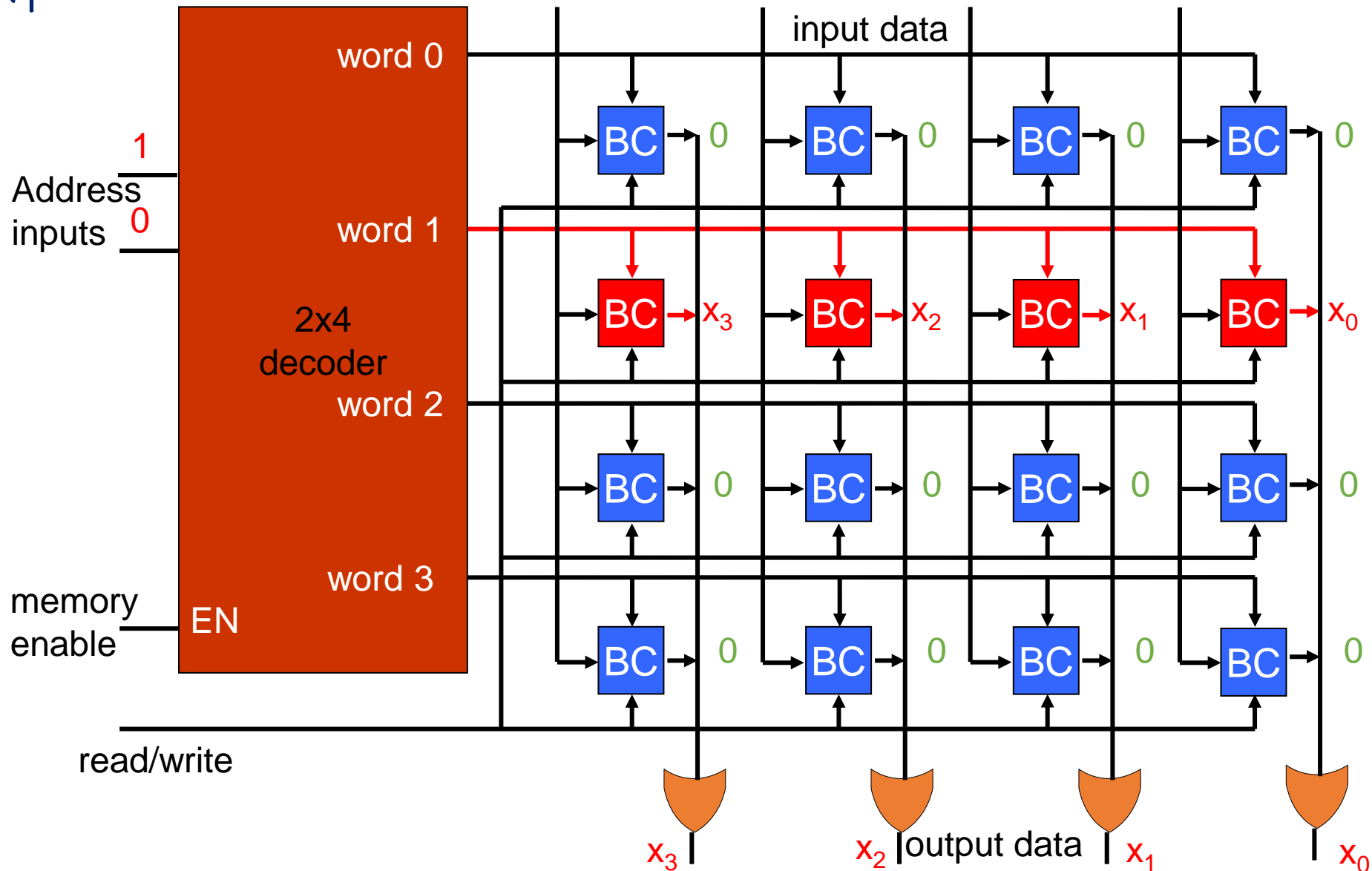


Commercial RAMs

 - Physical construction
 - Capacity of thousands of words
 - each word may range from 1 to 64 bits
- Example:
 - We have memory chips of 1024×4
 - Logical construction: 1024×8





Combining Memories

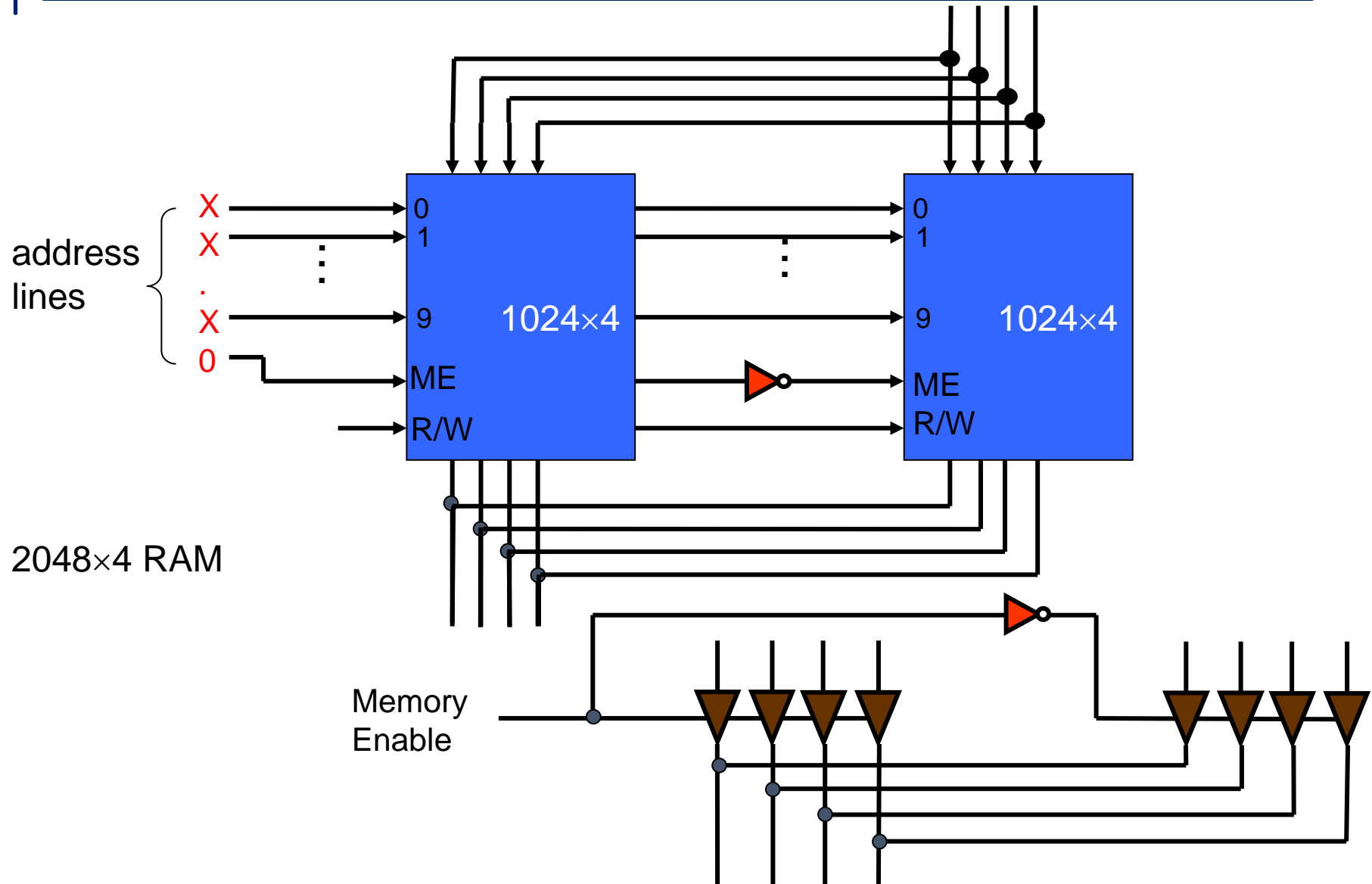



Coincident Decoding


- A memory with 2^k words requires a $k \times 2^k$ decoder
- $k \times 2^k$ decoder requires 2^k AND gates with k inputs per gate
- There are ways to reduce the total number of gates and number of inputs per gate
- Two dimensional selection scheme
 - Arrange the memory words in a two-dimensional array that is as close as possible to square
 - Use two $k/2$ -input decoders instead of one k -input decoder.
 - One decoder performs the row selection
 - The other does the column selection

Example: Coincident Decoding

1024 word memory

Binary address


0110010100

 



- SRAM memory is expensive
 - One cell typically contains four to six transistors
 - Usually used for on-chip cache memories and embedded systems (cameras, smart phones, etc.)
- DRAM is much less expensive
 - One MOS transistor and a capacitor
 - Four times the density of SRAM in a given chip area
 - cost per bit storage is three to four times less than SRAM
 - low power requirement
 - Perfect technology for large memories such as main memory
 - Most DRAMs have short word sizes

DRAMs and Address Multiplexing

 - In order to reduce number of pins on a memory chip, the same pins are used for both row and column addresses
- Example: 1 GB DRAM



DRAMs and Address Multiplexing

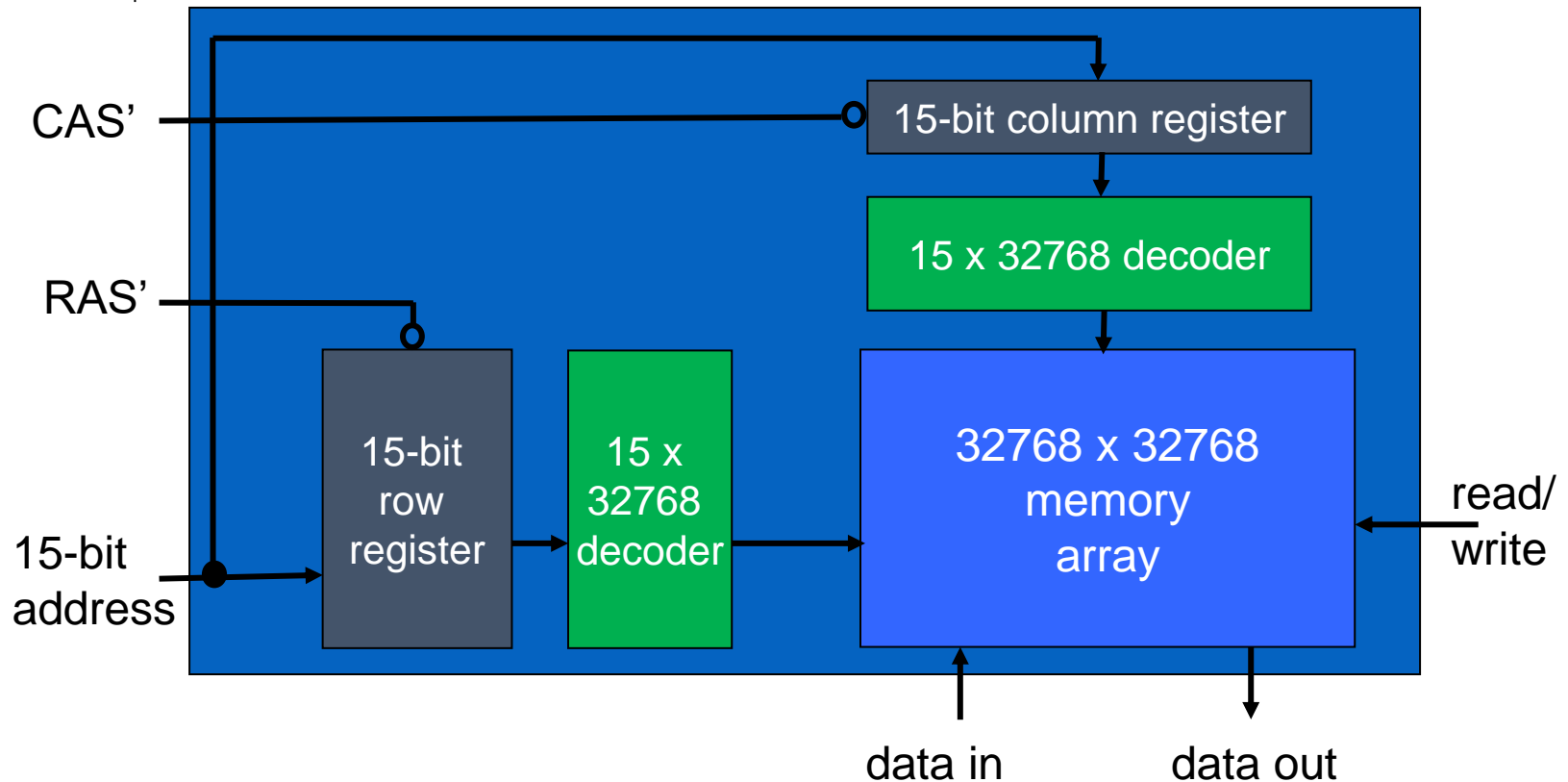 


Read-Only Memory

■ ROM

- memory device in which permanent binary information is stored
- Binary information is **programmed** into the device
- It then is embedded in the unit to form the required **interconnection pattern**
- nonvolatile


■ Block diagram

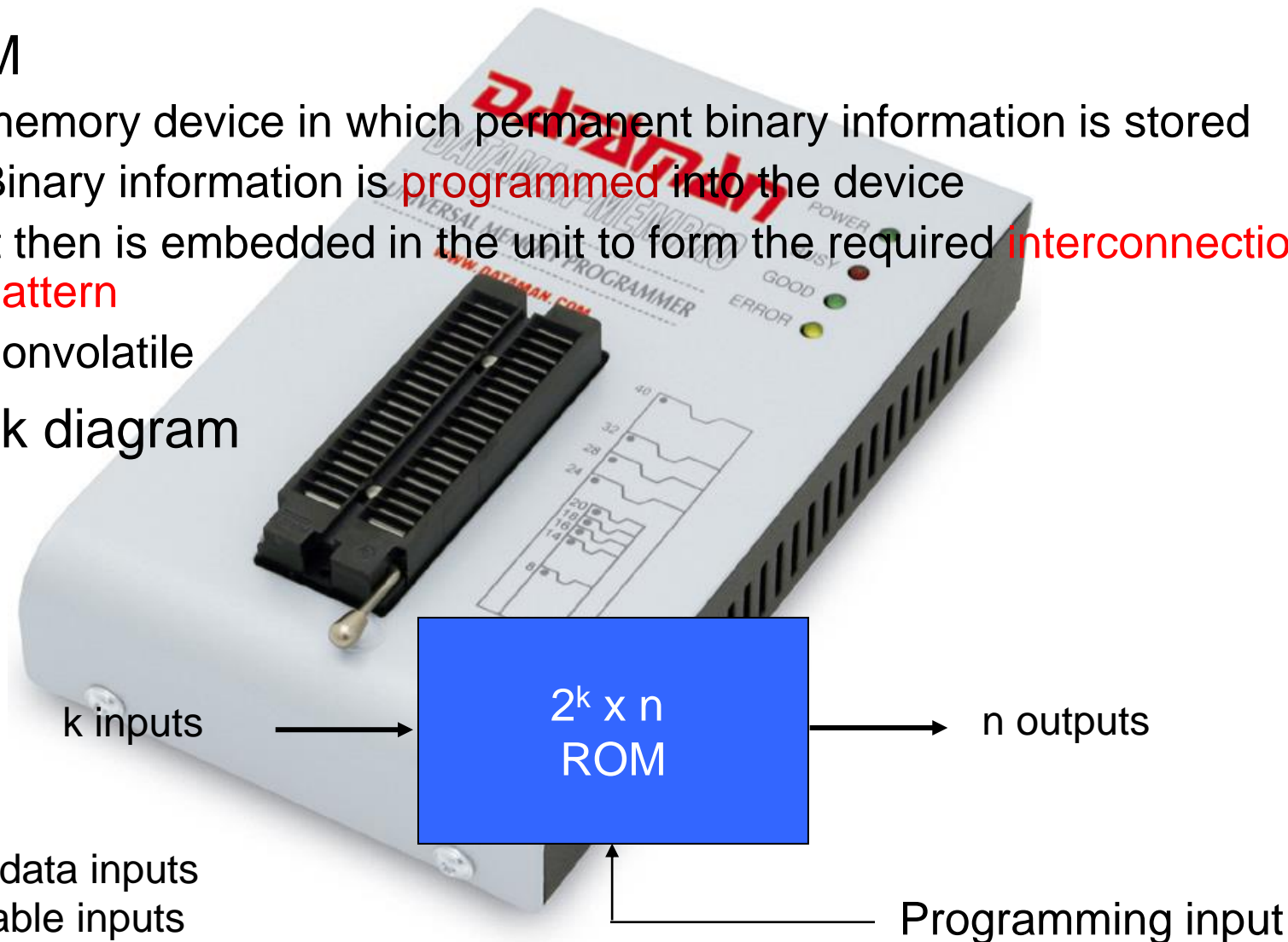

- no data inputs
- enable inputs
- three-state outputs

Example: ROM

■ 32 x 8 ROM

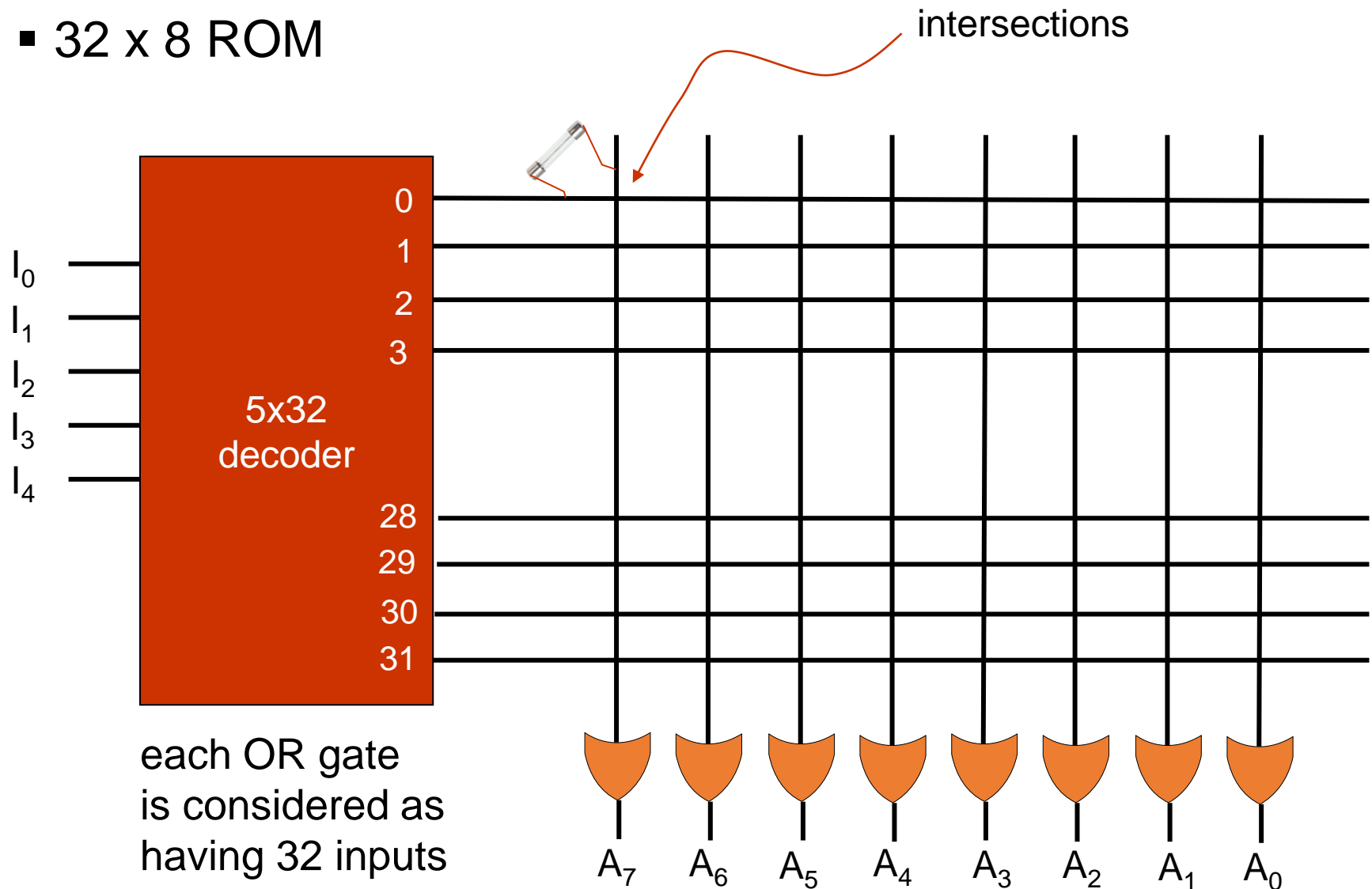

Example: ROM

- Number of connections
 - 32×8 ROM has $32 \times 8 = 256$ internal connections
- In general
 - $2^k \times n$ ROM will have a $k \times 2^k$ decoder and n OR gates
 - Each OR gate has 2^k inputs
 - inputs of every OR gate are initially connected to each output of the decoder
- These intersections are programmable
 - they are initially closed (connected to the input of OR gate)
 - A fuse is used to connect two wires
 - During programming, some of these fuses are blown by applying high voltage.


Programming ROM

- Internal storage specified by a table
- Example: 32×8 ROM

Inputs					Outputs							
I_4	I_3	I_2	I_1	I_0	A_7	A_6	A_5	A_4	A_3	A_2	A_1	A_0
0	0	0	0	0	1	0	1	1	0	1	1	0
0	0	0	0	1	0	0	0	1	1	1	0	1
0	0	0	1	0	1	1	0	0	0	1	0	1
0	0	0	1	1	1	0	1	1	0	0	1	0
...
1	1	1	0	0	0	0	0	0	1	0	0	1
1	1	1	0	1	1	1	1	0	0	0	1	0
1	1	1	1	0	0	1	0	0	1	0	1	0
1	1	1	1	1	0	0	1	1	0	0	1	1

Programming ROM

Inputs					Outputs							
I_4	I_3	I_2	I_1	I_0	A_7	A_6	A_5	A_4	A_3	A_2	A_1	A_0
0	0	0	0	0	1	0	1	1	0	1	1	0

 


Combinational Circuit Design with ROM

- Formerly,
 - we have shown that a $k \times 2^k$ decoder generates 2^k minterms of k input variables
- Furthermore,
 - by inserting OR gates to sum these minterms, we were able to realize any desired combinational circuit.
- A ROM is essentially a device that includes both the decoder and the OR gates within a single device.
 - first interpretation: a memory unit that stores words

Combinational Circuit Design with ROM

■ ROM (cont.)

 - Second interpretation: a programmable device that can realize any combinational circuit




Combinational Circuit Design with ROM

- Example: Truth table

Inputs			Outputs					
A_2	A_1	A_0	B_5	B_4	B_3	B_2	B_1	B_0
0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	1	1
0	1	0	0	0	0	1	0	0
0	1	1	0	0	1	0	1	0
1	0	0	0	1	0	0	0	0
1	0	1	0	1	1	0	0	1
1	1	0	1	0	0	1	1	1
1	1	1	1	1	0	0	0	1

Example: Design with ROM


8 x 6 ROM would suffice

 

Inputs			Outputs					
A_2	A_1	A_0	B_5	B_4	B_3	B_2	B_1	B_0
0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	1	1
0	1	0	0	0	0	1	0	0
0	1	1	0	0	1	0	1	0
1	0	0	0	1	0	0	0	0
1	0	1	0	1	1	0	0	1
1	1	0	1	0	0	1	1	1
1	1	1	1	1	0	0	0	1

ROM Truth Table

Example: Design with ROM

 


Inputs			Outputs					
A_2	A_1	A_0	B_5	B_4	B_3	B_2	B_1	B_0
0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	1	1
0	1	0	0	0	0	1	0	0
0	1	1	0	0	1	0	1	0
1	0	0	0	1	0	0	0	0
1	0	1	0	1	1	0	0	1
1	1	0	1	0	0	1	1	1
1	1	1	1	1	0	0	0	1

Types of ROM 1/2

- Programming can be done in different ways
 - Mask programming:
 - customer provides the truth table
 - manufacturer generates the mask for the truth table
 - can be costly, since generating a custom mask is charged to the customer.
 - economical only if a large quantity of the same ROM configuration is to be ordered.
 - Field Programmable
 - Programmable ROM (PROM):
 - Customer can program the ROM by blowing fuses by applying high voltage through a special pin
 - Special instrument called PROM programmer is needed.


Types of ROM 2/2

 - Programming ROM and PROMs is irreversible.
- Erasable PROM (EPROM)
 - can be programmed repeatedly.
 - EPROM is placed under a special ultra-violet light for a given period of time
 - At the end, the former program is erased
 - After erasure, EPROM becomes ready for another programming
- Electronically erasable PROM (EEPROM or E²PROM)




Programmable Logic Devices

 
- EPROM is an example of combinational **p**rogrammable **l**ogic **d**evice (PLD)
- Configuration of PROM



- Two other types

 


Programmable Logic Array (PLA)

 


Programmable Array Logic (PAL)

Programmable Logic Array (PLA)

 

- Similar to PROM
- However, PLA does not generate all the minterms
- Decoder is replaced by an array of AND gates
 - can be programmed to generate **any product term** of input variables
- The product terms are then connected to OR gates
 - that provide the sum of products

PLA: Example

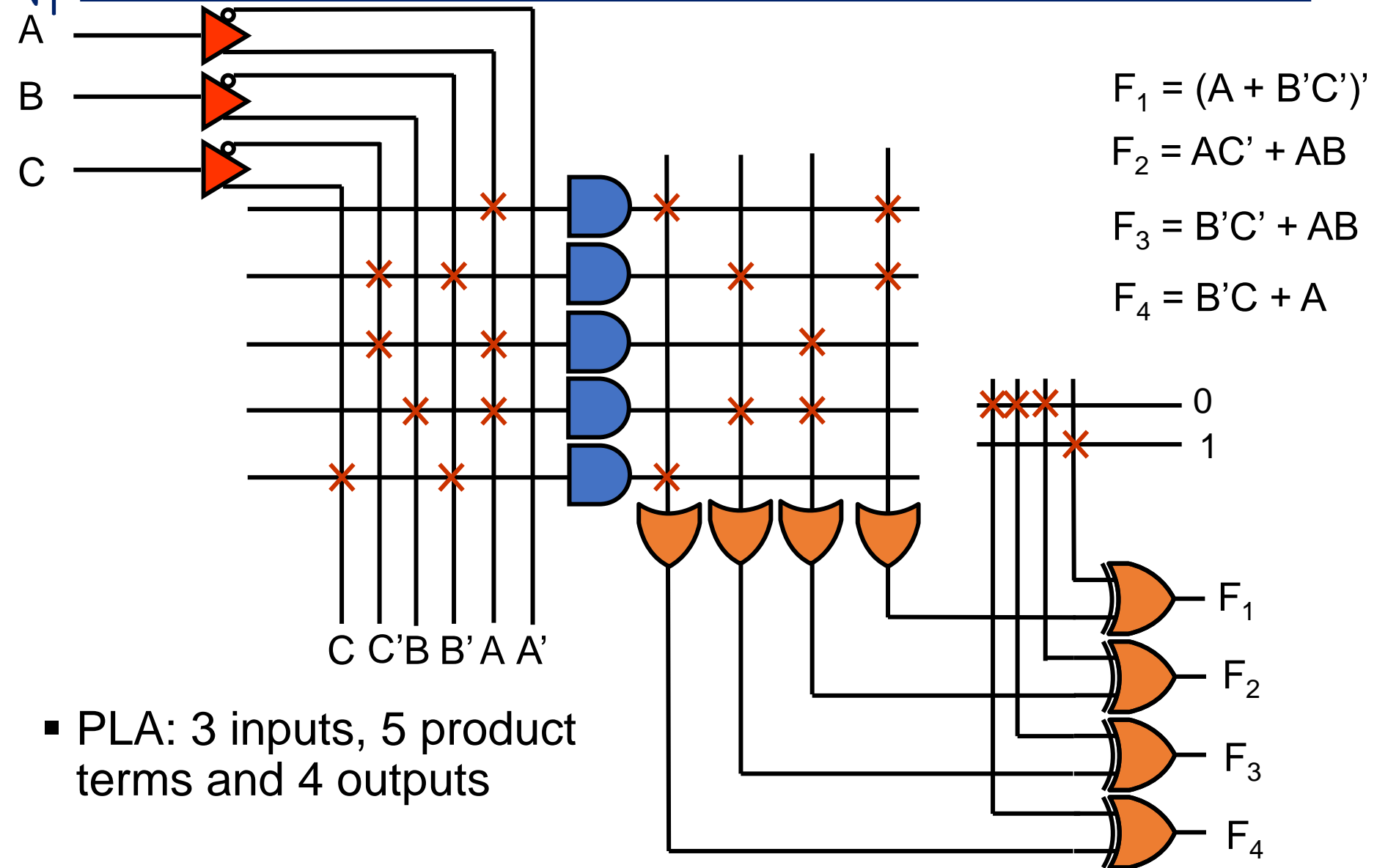

- PLA: 3 inputs, 5 product terms and 4 outputs



PLA Programming Table

$$F_1 = (A + B'C')'$$

$$F_3 = B'C' + AB$$

$$F_2 = AC' + AB$$

$$F_4 = B'C + A$$

					Outputs			
		Inputs						
	Product Term	A	B	C	F_1	F_2	F_3	F_4
	1							
	2							
	3							
	4							
	5							

- Specified by
 - number of **inputs**, number of **product terms**, number of **outputs**
- A typical IC PLA (F100)
 - 16 inputs, 48 product terms, and 8 outputs
- n input, k product terms, m output PLA has
 - k AND gates, m OR gates, m XOR gates
 - $2n \times k$ connections between input and the AND array
 - $k \times m$ connections between the AND and OR arrays
 - $2m$ connections associated with XOR gates
 - $(2n \times k + k \times m + 2m)$ connections to program

- Optimization

- number of literals in a product term is not important
- When implementing more than one function, functions must be optimized together in order to share more product terms
 - multiple output optimization (espresso)
- both the true and complement of each function should be simplified to see which one requires fewer number of product terms

<http://web.eecs.umich.edu/~ksewell/espresso/>

Example: Programming PLA

- Two functions

- $F_1(A, B, C) = \sum(0, 1, 2, 4)$

- $F_2(A, B, C) = \sum(0, 5, 6, 7)$

		BC			
		00	01	11	10
A	0	1	1	0	1
	1	1	0	0	0

$$F_1 = A'B' + A'C' + B'C'$$

$$F_1 = (AB + AC + BC)'$$

		BC			
		00	01	11	10
A	0	1	0	0	0
	1	0	1	1	1

$$F_2 = AB + AC + A'B'C'$$

$$F_2 = (A'C + A'B + AB'C')'$$

Example: Programming PLA


- PLA programming table

$$F_1 = (AB + AC + BC)'$$

$$F_2 = AB + AC + A'B'C'$$

					Outputs	
		Inputs			C	T
	Product Term	A	B	C	F ₁	F ₂
AB	1	1	1	-	1	1
AC	2	1	-	1	1	1
BC	3	-	1	1	1	-
A'B'C'	4	0	0	0	-	1

Programmable Array Logic (PAL)

 


Programmable Array Logic (PAL)

- Easier to program than PLA
- But, not as flexible
- A typical PAL
 - 8 inputs, 8 outputs, 8-wide AND-OR array



Example: PAL

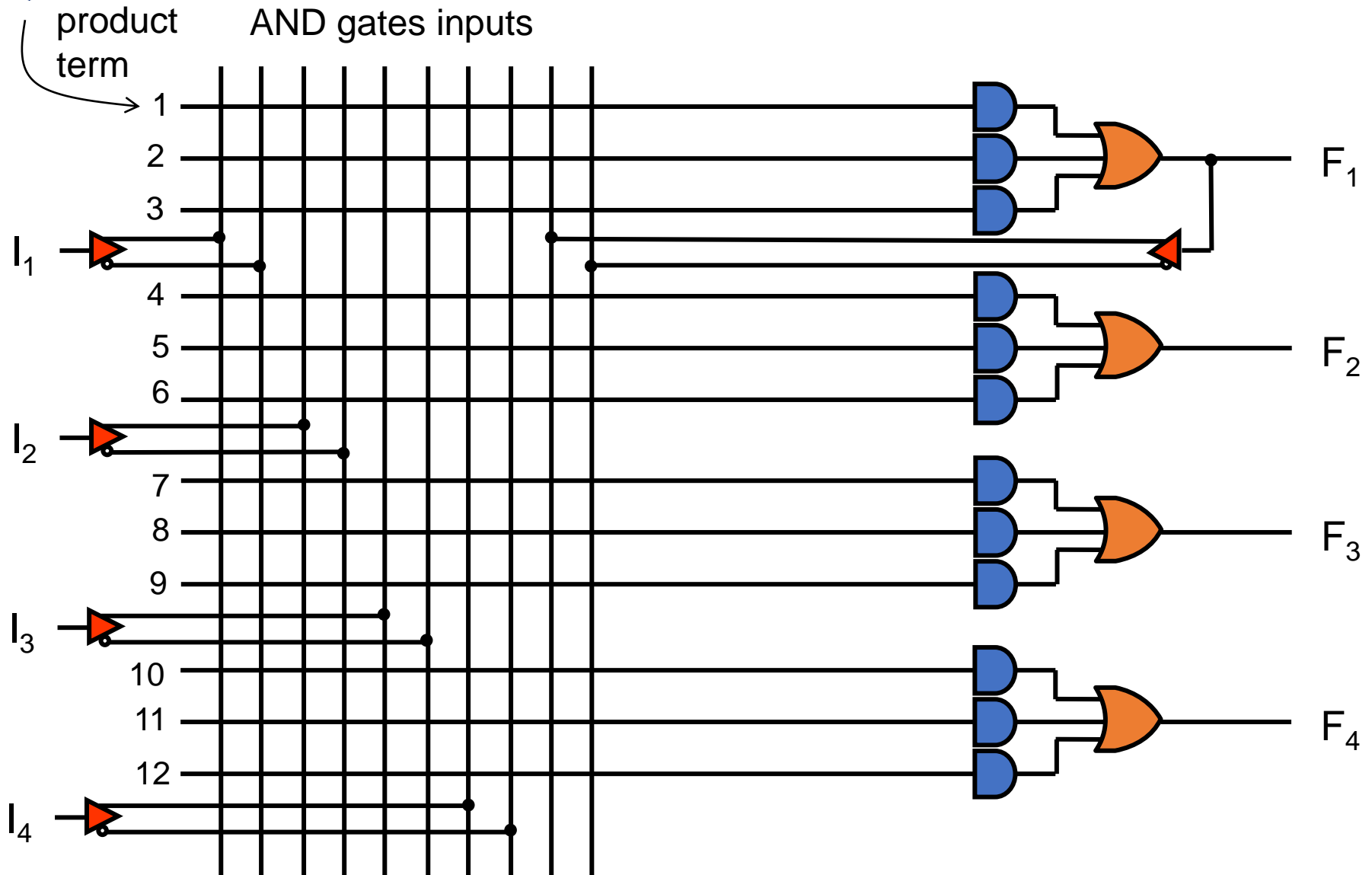



Design with PAL

- Each Boolean function must be simplified to fit into each section.
- Product terms cannot be shared among OR gates
 - Each function can be simplified by itself without regard to common product terms
- The number of product terms in each section is fixed
 - If the number of product terms is too many, we may have to use two sections to implement the function.

Example: Design with PAL


- Four functions
 - $A(x, y, z, t) = \sum (2, 12, 13)$
 - $B(x, y, z, t) = \sum (7, 8, 9, 10, 11, 12, 13, 14, 15)$
 - $C(x, y, z, t) = \sum (0, 2, 3, 4, 5, 6, 7, 8, 10, 11, 15)$
 - $D(x, y, z, t) = \sum (1, 2, 8, 12, 13)$
- First step is to simplify four functions separately
 - $A = xyz' + x'y'zt'$
 - $B = x + yzt$
 - $C = x'y + zt + y't'$
 - $D = xyz' + x'y'zt' + xy't' + x'y'z't$



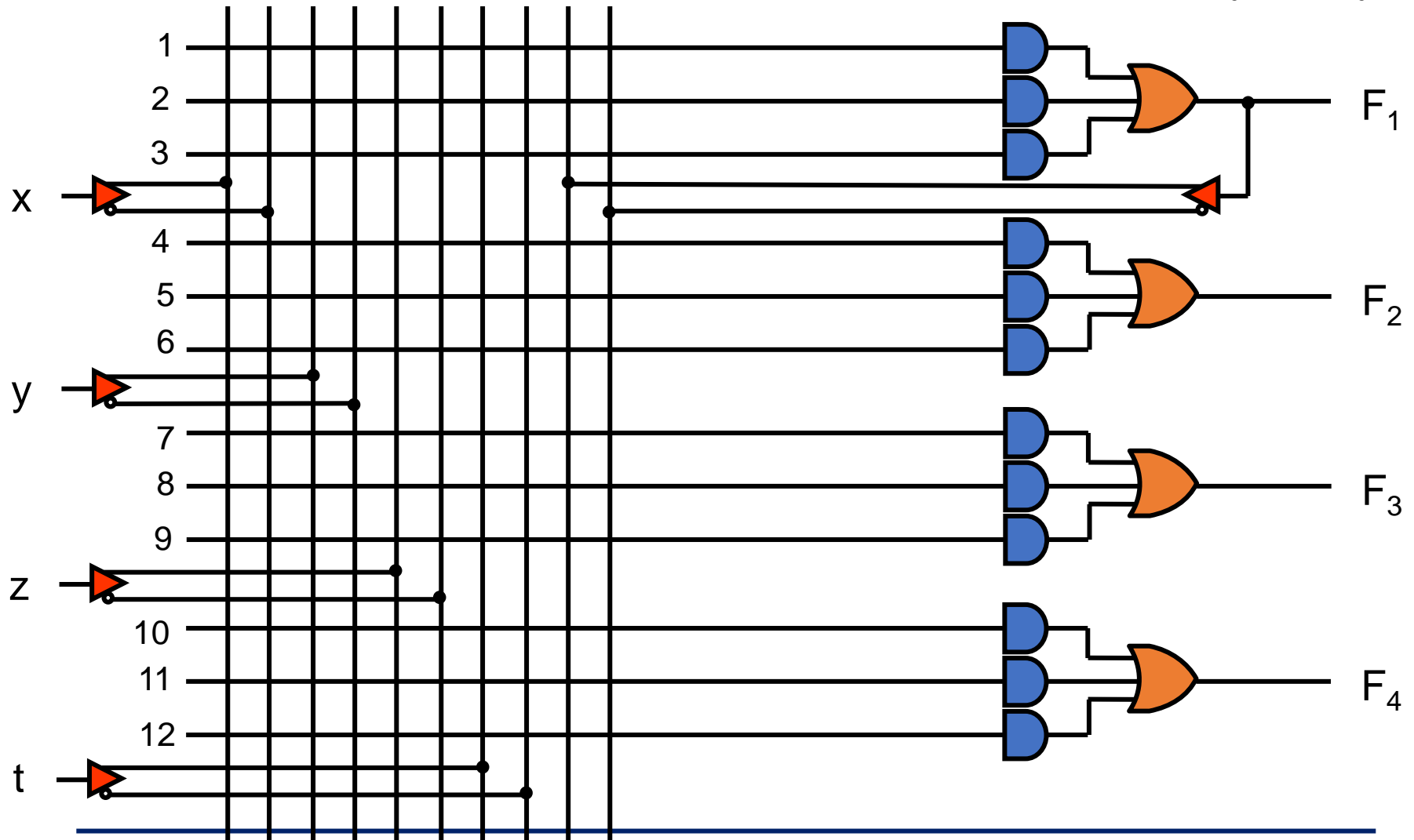Example: Design with PAL

$$A = xyz' + x'y'zt' \quad B = x + yzt$$

$$C = x'y + zt + y't' \quad D = xyz' + x'y'zt' + xy't' + x'y'z't = A + xy't' + x'y'z't$$




Example: Design with PAL

▪ $D = A + xy't' + x'y'z't$

Product Term	AND Inputs					Outputs
	x	y	z	t	F_1	
1	1	1	0	-	-	$A = F_1 = xyz' + x'y'zt'$
2	0	0	1	0	-	
3	-	-	-	-	-	
4	1	-	-	-	-	$B = F_2 = x + yzt$
5	-	1	1	1	-	
6	-	-	-	-	-	
7	0	1	-	-	-	$C = F_3 = x'y + zt + y't'$
8	-	-	1	1	-	
9	-	0	-	0	-	
10	-	-	-	-	1	$D = F_4 = F_1 + xy't' + x'y'z't$
11	1	0	-	0	-	
12	0	0	0	1	-	

Example: Design with PAL

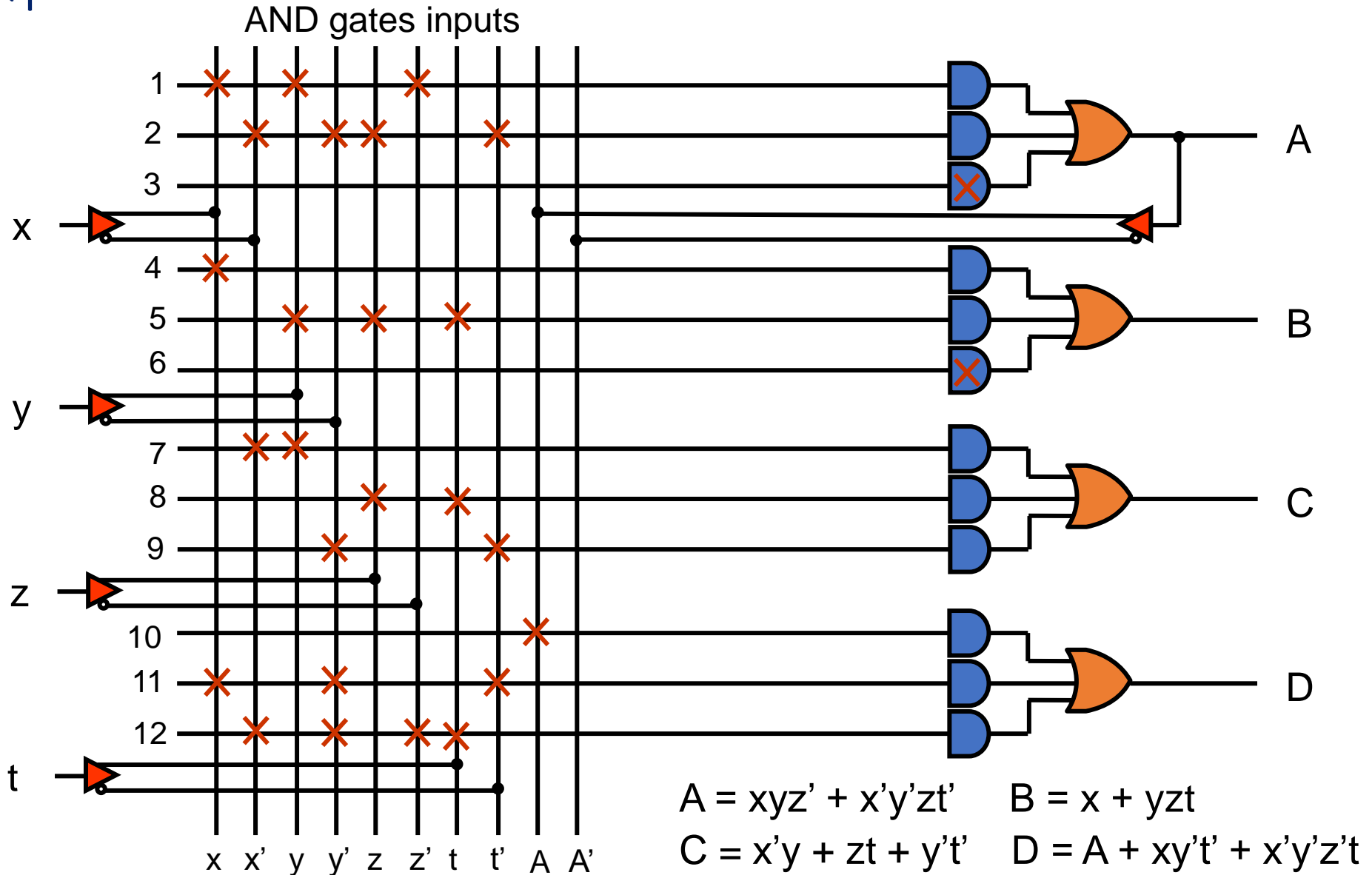

$$A = xyz' + x'y'zt'$$

$$B = x + yzt$$


$$C = x'y + zt + y't'$$

$$D = A + xy't' + x'y'z't$$

PAL: BCD to 7-Segment-Display Decoder

▪ $(ABCD)_{10} \rightarrow (a\ b\ c\ d\ e\ f\ g)$

A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
X	X	X	X	X	X	X	X	X	X	X

 


PAL: BCD to 7-Segment-Display Decoder

▪ $(ABCD)_{10} \rightarrow (a\ b\ c\ d\ e\ f\ g)$

- $a = A + BD + C + B'D'$
- $b = C'D' + CD + B'$
- $c = B + C' + D$
- $d = B'D' + CD' + BC'D + B'C + A$
- $e = B'D' + CD'$
- $f = A + C'D' + BD' + BC'$
- $g = A + CD' + BC' + B'C$
- we need 4 inputs, 7 outputs, at most 5 product terms per output
- P16H8: 10 inputs, 8 outputs, 7 product terms per output.

 P14H8: 14 inputs, 8 outputs (2 have four product terms, 6 have 2 product terms)



7-Segment-Display Decoder

- Different way to optimize

- multiple output optimization → espresso supports this

- $a = BC'D + CD + B'D' + A + BCD'$

- $b = B'C' + C'D' + CD + B'D'$

- $c = B'C' + BC'D + C'D' + CD + BCD'$

- $d = B'C + BC'D + B'D' + BCD' + A$

- $e = B'D' + BCD'$

- $f = BC'D + C'D' + A + BCD'$

- $g = BD' + B'C + A + BC'D$

- 9 product terms in total
(previous one has 15)

- $a = A + BD + C + B'D'$

- $b = C'D' + CD + B'$

- $c = B + C' + D$

- $d = B'D' + CD' + BC'D + B'C + A$

- $e = B'D' + CD'$

- $f = A + C'D' + BD' + BC'$

- $g = A + CD' + BC' + B'C$