

CS 303

Logic & Digital System Design

Ömer Ceylan

**Sabancı
Universitesi**



Boolean Algebra



Boolean Algebra 1/2

- A set of elements B
 - There exist at least two elements $x, y \in B$ s. t. $x \neq y$
- Binary operators: $+$ and \cdot
 - closure w.r.t. both $+$ and \cdot
 - additive identity ?
 - multiplicative identity ?
 - commutative w.r.t. both $+$ and \cdot
 - Associative w.r.t. both $+$ and \cdot
- Distributive law:
 - \cdot is distributive over $+$?
 - $+$ is distributive over \cdot ?
 - We do not have both in ordinary algebra



Boolean Algebra 2/2

- Complement
 - $\forall x \in B$, there exist an element $x' \in B$ \ni
 - a. $x + x' = 1$ (multiplicative identity) and
 - b. $x \cdot x' = 0$ (additive identity)
 - Not available in ordinary algebra
- Differences btw ordinary and Boolean algebra
 - Ordinary algebra with real numbers
 - Boolean algebra with elements of set B
 - Complement
 - Distributive law
 - Do not substitute laws from one to another where they are not applicable

Two-Valued Boolean Algebra 1/3

- To define a Boolean algebra
 - The set B
 - Rules for two binary operations
 - The elements of B and rules should conform to our axioms
- Two-valued Boolean algebra
 - $B = \{0, 1\}$

x	y	$x \cdot y$
0	0	0
0	1	0
1	0	0
1	1	1

x	y	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

x	x'
0	1
1	0

Two-Valued Boolean Algebra 2/3

- Check the axioms
 - Two distinct elements, $0 \neq 1$
 - Closure, associative, commutative, identity elements
 - Complement
 - $x + x' = 1$ and $x \cdot x' = 0$
 - Distributive law

x	y	z
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

$y \cdot z$	$x + (y \cdot z)$

$x + y$	$x + z$	$(x + y) \cdot (x + z)$
0	0	
0	1	
1	0	
1	1	
1	1	
1	1	
1	1	
1	1	

Two-Valued Boolean Algebra 3/3

- Two-valued Boolean algebra is actually equivalent to the binary logic defined heuristically before
 - Operations:
 - $\cdot \rightarrow$ AND
 - $+$ \rightarrow OR
 - Complement \rightarrow NOT
- Binary logic is the application of Boolean algebra to the gate-type circuits
 - Two-valued Boolean algebra is developed in a formal mathematical manner
 - This formalism is necessary to develop theorems and properties of Boolean algebra

Duality Principle

- An important principle

- every algebraic expression deducible from the axioms of Boolean algebra remains valid if the operators and identity elements are interchanged

- Example:

- $x + x = x$

- $x + x = (x+x) \cdot 1$ (identity element)
 $= (x+x) \cdot (x+x')$ (complement)
 $= x+x \cdot x'$ (+ over ·)
 $= x$ (complement)

- duality principle

$x \cdot x = x \rightarrow ?$

Duality Principle & Theorems

- Theorem a:

- $x + 1 = 1$

- $$\begin{aligned} x + 1 &= 1 \cdot (x+1) \\ &= (x+x') \cdot (x+1) \\ &= x+x' \cdot 1 \\ &= x+x' \\ &= 1 \end{aligned}$$

- Theorem b: (using duality)

- ?



Absorption Theorem

a. $x + xy = x$

b. ?

Involution & DeMorgan's Theorems

- Involution Theorem:
 - $(x')' = x$
 - $x + x' = 1$ and $x \cdot x' = 0$
 - Complement of x' is x
 - Complement is unique
- DeMorgan's Theorem:
 $(x + y)' = x' \cdot y'$

Truth Tables for DeMorgan's Theorem

$$(x + y)' = x' \cdot y'$$

x	y	x+y	(x+y)'	x · y	(x · y)'
0	0				
0	1				
1	0				
1	1				



x'	y'	x' · y'	x' + y'



Operator Precedence

1. Parentheses
 2. NOT
 3. AND
 4. OR
- Example:
 - $(x + y)'$
 - $x' \cdot y'$
 - $x + x \cdot y'$

Boolean Functions

- Consists of
 - binary variables (normal or complement form)
 - the constants, 0 and 1
 - logic operation symbols, “+” and “.”


- Example:

- $F_1(x, y, z) = x + y' z$
- $F_2(x, y, z) = x' y' z + x' y z + xy'$

x	y	z	F ₁	F ₂
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	0	1
1	0	0	1	1
1	0	1	1	1
1	1	0	1	0
1	1	1	1	0

Logic Circuit Diagram of F_1


$$F_1(x, y, z) = x + y' z$$

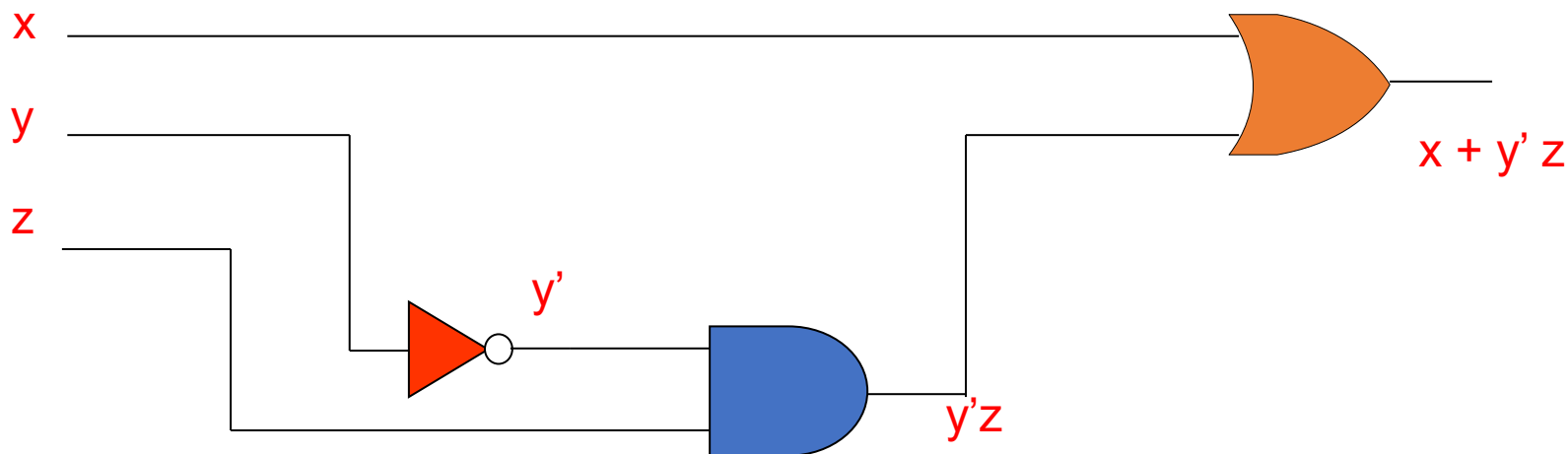

Gate Implementation of $F_1 = x + y' z$

Logic Circuit Diagram of F_2


$$F_2 = x' y' z + x' y z + xy'$$

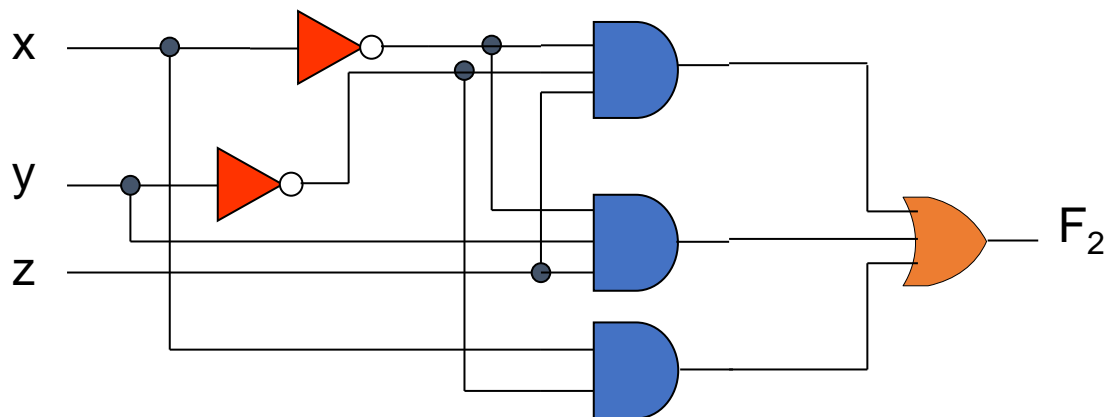


- Algebraic manipulation
- $F_2 = x' y' z + x' y z + xy'$
 $= ?$

Alternative Implementation of F_2

$$F_2 = x'z + xy'$$

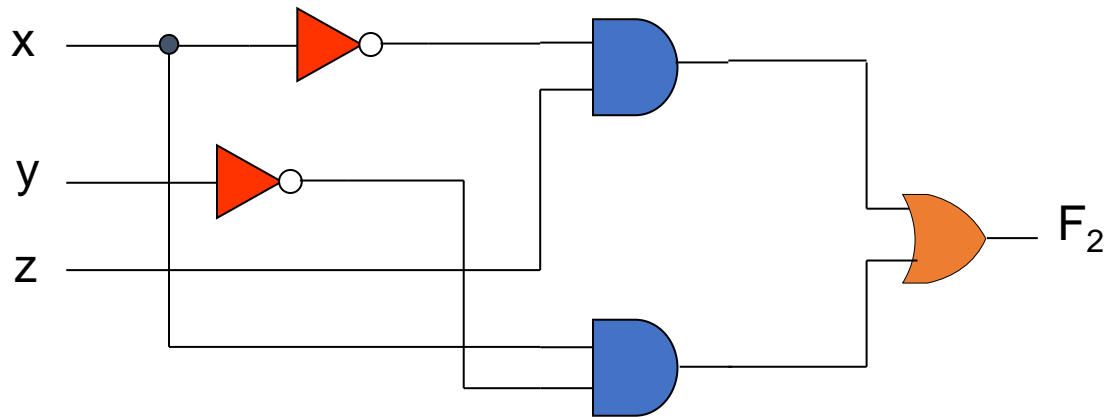

$$F_2 = x'y'z + x'yz + xy'$$

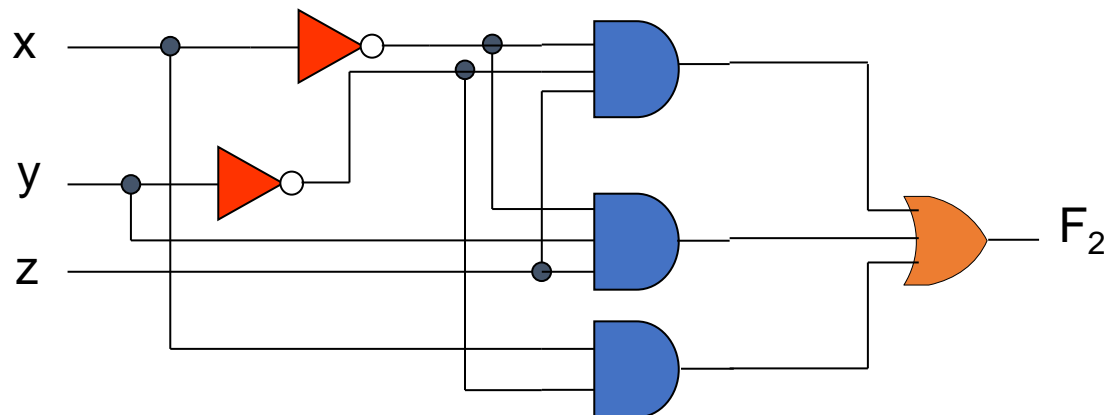

Complement of a Function

- F' is complement of F
 - We can obtain F' , by interchanging of 0's and 1's in the truth table

x	y	z	F	F'
0	0	0	0	1
0	0	1	0	1
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	1	0
1	1	0	0	1
1	1	1	0	1

$$F = x'yz' + xy'z' + xy'z$$

$$F' = ?$$

Generalizing Demorgan's Theorem

- We can also utilize DeMorgan's Theorem
 - $(x + y)' = x' y'$
 - $(A + B + C)' = A'B'C'$
- We can generalize DeMorgan's Theorem
 1. $(x_1 + x_2 + \dots + x_N)' = x_1' \cdot x_2' \cdot \dots \cdot x_N'$
 2. $(x_1 \cdot x_2 \cdot \dots \cdot x_N)' = x_1' + x_2' + \dots + x_N'$

Example: Complement of a Function

- Example:

- $F_1 = x'yz' + x'y'z$

- $F_1' = (x'yz' + x'y'z)'$

$= ?$

$$= (x + y' + z)(x + y + z')$$

- $F_2 = x(y'z' + yz)$

- $F_2' = (x(y'z' + yz))'$

$= ?$

$$= x' + (y + z)(y' + z')$$

- Easy Way to Complement: take the dual of the function and complement each literal

■ Minterms

- A product term: all variables appear (either in its normal, x , or its complement form, x')
- How many different terms we can get with x and y ?
 - $x'y' \rightarrow 00 \rightarrow m_0$
 - $x'y \rightarrow 01 \rightarrow m_1$
 - $xy' \rightarrow 10 \rightarrow m_2$
 - $xy \rightarrow 11 \rightarrow m_3$
- m_0, m_1, m_2, m_3 (minterms or AND terms, standard product)
- n variables can be combined to form 2^n minterms

- Maxterms (OR terms, standard sums)
 - $M_0 = x + y \rightarrow 00$
 - $M_1 = x + y' \rightarrow 01$
 - $M_2 = x' + y \rightarrow 10$
 - $M_3 = x' + y' \rightarrow 11$
 - n variables can be combined to form 2^n maxterms
 - $m_0' = M_0$
 - $m_1' = M_1$
 - $m_2' = M_2$
 - $m_3' = M_3$

Example

xyz	m_i	M_i	F
000	$m_0 = x' y' z'$	$M_0 = x + y + z$	0
001	$m_1 = x' y' z$	$M_1 = x + y + z'$	1
010	$m_2 = x' y z'$	$M_2 = x + y' + z$	1
011	$m_3 = x' y z$	$M_3 = x + y' + z'$	0
100	$m_4 = x y' z'$	$M_4 = x' + y + z$	0
101	$m_5 = x y' z$	$M_5 = x' + y + z'$	0
110	$m_6 = x y z'$	$M_6 = x' + y' + z$	1
111	$m_7 = x y z$	$M_7 = x' + y' + z'$	0

$$F(x, y, z) = x'y'z + x'yz' + xyz' =$$

$$F(x, y, z) = (x+y+z)(x+y'+z')(x'+y+z)(x'+y+z')(x'+y'+z') =$$



Another Example

x	y	z	F_1	F_2
0	0	0	0	1
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

▪ $F_1(x, y, z) =$

▪ $F_2(x, y, z) =$



Important Properties

- Any Boolean function can be expressed as a sum of minterms
- Any Boolean function can be expressed as a product of maxterms
- Example:
 - $F(x,y,z) = \sum (0, 2, 3, 5, 6)$
 $= x'y'z' + x'yz' + x'yz + xy'z + xyz'$
 - How do we find the complement of F?
 - $F'(x,y,z) = (x + y + z)(x + y' + z)(x + y' + z')(x' + y + z')(x' + y' + z)$
 $= M_0 M_2 M_3 M_5 M_6$
 $= \prod(0, 2, 3, 5, 6)$

Canonical Form

- If a Boolean function is expressed as a *sum of minterms* or *product of maxterms* the function is said to be in canonical form.
- Example: $F = x + y'z \rightarrow$ canonical form?
 - No
 - But we can put it in canonical form.
 - $x \rightarrow x(y+y')(z+z') = (xy+xy')(z+z') = xyz + xyz' + xy'z + xy'z'$
 - $y'z \rightarrow$
 - $x + y'z = xyz + xyz' + \textcolor{red}{xy'z} + xy'z' + \textcolor{red}{xy'z} + x'y'z$
 - $F = x + y'z = \sum (7, 6, 5, 4, 1)$
- Alternative way:
 - Obtain the truth table first and then the canonical term.

Example: Product of Maxterms

- $F = xy + x'z$
 - Use the distributive law + over ·
 - $F = xy + x' \cdot z$
 $= (xy + x') \cdot (xy + z)$

$$= \Pi (4, 5, 0, 2)$$



Conversion Between Canonical Forms

- Fact:

- The complement of a function (given in sum of minterms) can be expressed as a sum of minterms missing from the original function

- Example:

- $F(x, y, z) = \sum (1, 4, 5, 6, 7)$
- $F'(x, y, z) =$
- Now take the complement of F' and make use of DeMorgan's theorem
- $(F')' = (m_0 + m_2 + m_3)' =$
- $F = M_0 \cdot M_2 \cdot M_3 = \prod (0, 2, 3)$

General Rule for Conversion

- Important relation:

- $m_j' = M_j$.
- $M_j' = m_j$.

- The rule:

- Interchange symbols Π and Σ , and
- list those terms missing from the original form

- Example: $F = xy + x'z$

- $F = \Sigma(1, 3, 6, 7) \rightarrow F = \Pi(?, ?, ?, ?)$




- Fact:
 - Canonical forms are very seldom the ones with the least number of literals
- Alternative representation:
 - Standard form
 - a term may contain any number of literals
 - Two types
 1. the sum of products
 2. the product of sums
 - Examples:
 - $F_1 = y' + xy + x'yz'$
 - $F_2 = x(y' + z)(x' + y + z')$




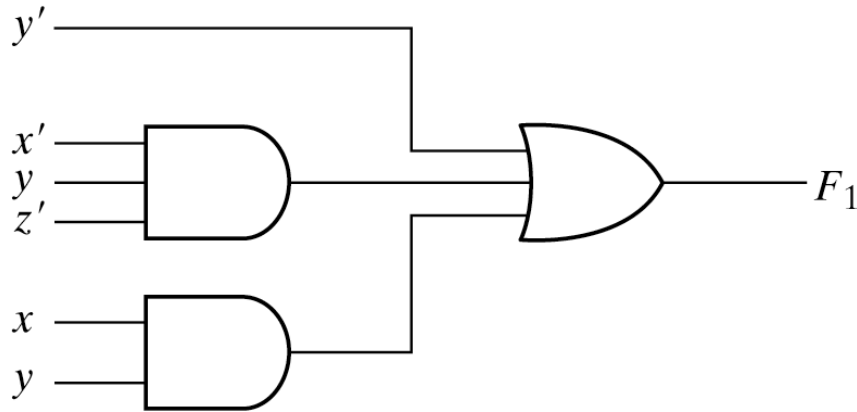Example: Standard Forms

- $F_1 = y' + xy + x'yz'$
- $F_2 = x(y' + z)(x' + y + z')$



(a) Sum of Products

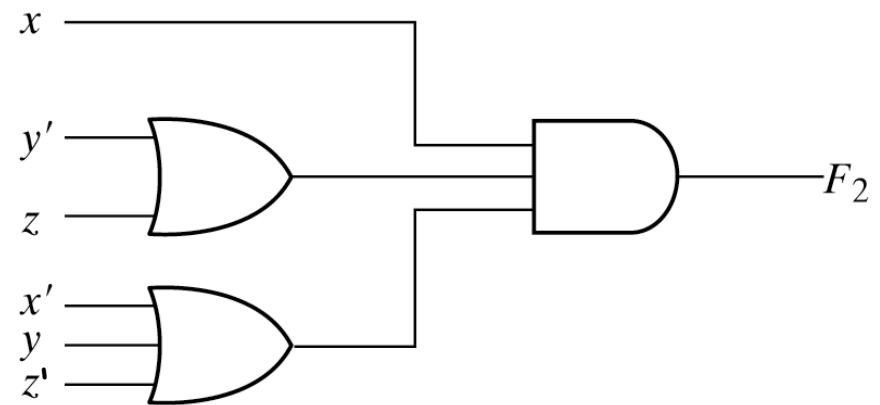


(b) Product of Sums

Fig. 2-3 Two-level implementation




Nonstandard Forms

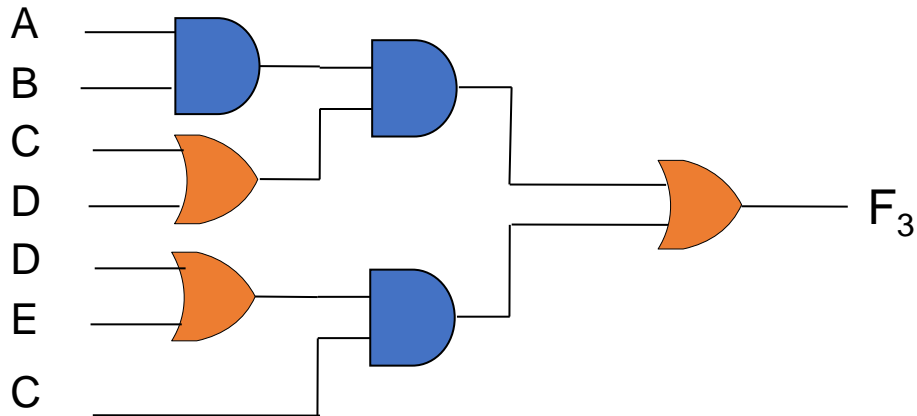- $F_3 = AB(C+D) + C(D + E)$
- This hybrid form yields three-level implementation



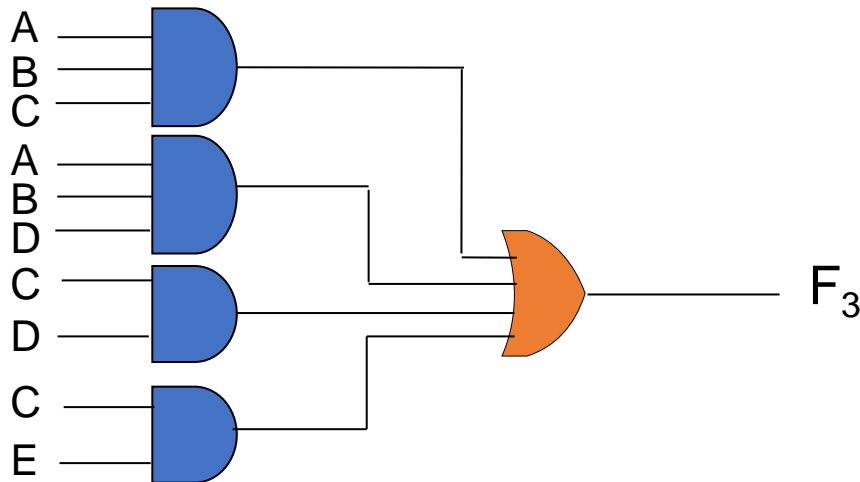- The standard form: $F_3 = ABC + ABD + CD + CE$



OTHER LOGIC OPERATORS - 1

- AND, OR, NOT are logic operators
 - Boolean functions with two variables
 - three of the 16 possible two-variable Boolean functions


x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7
0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1

x	y	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1


OTHER LOGIC OPERATORS - 2

- Some of the Boolean functions with two variables
 - Constant functions: $F_0 = 0$ and $F_{15} = 1$
 - AND function: $F_1 = xy$
 - OR function: $F_7 = x + y$
 - XOR function:
 - $F_6 = x' y + xy' = x \oplus y$ (x or y, but not both)
 - XNOR (Equivalence) function:
 - $F_9 = xy + x' y' = (x \oplus y)'$ (x equals y)
 - NOR function:
 - $F_8 = (x + y)' = (x \downarrow y)$ (Not-OR)
 - NAND function:
 - $F_{14} = (x y)' = (x \uparrow y)$ (Not-AND)


Logic Gate Symbols

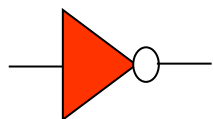


NOT

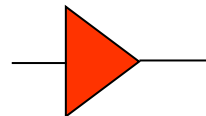


TRANSFER

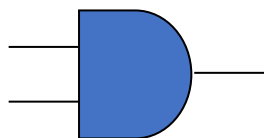


AND

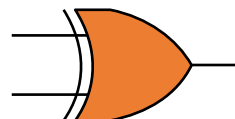


XOR

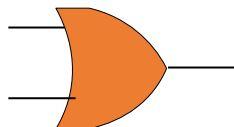


OR

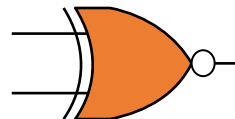

XNOR

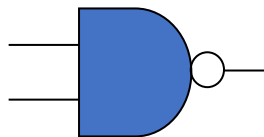

NAND

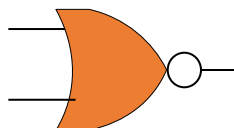




NOR

Universal Gates




- NAND and NOR gates are universal
- We know any Boolean function can be written in terms of three logic operations:
 - AND, OR, NOT
- In return, NAND gate can implement these three logic gates by itself
 - So can NOR gate

x	y	$(xy)'$	x'	y'	$(x' y')'$
0	0	1	1	1	0
0	1	1	1	0	1
1	0	1	0	1	1
1	1	0	0	0	1

NAND Gate

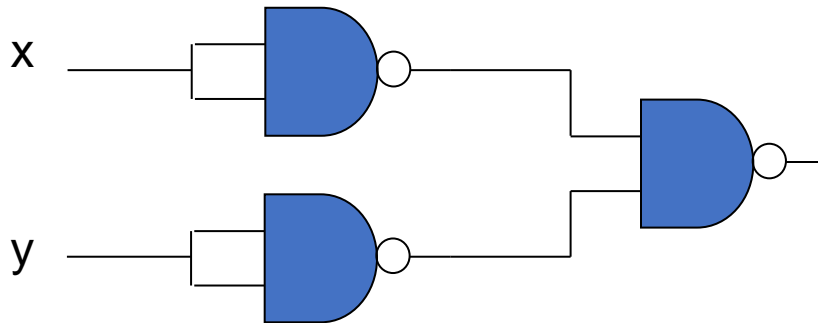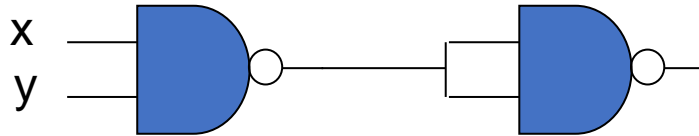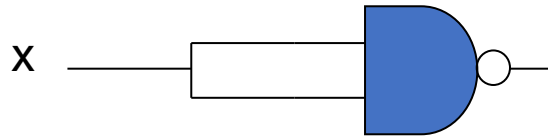

NOR Gate

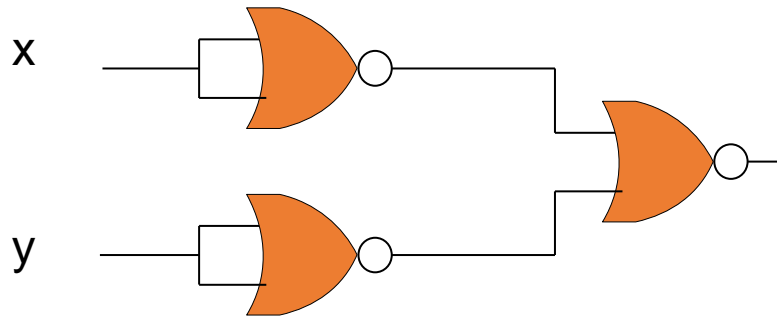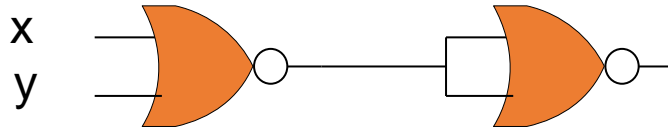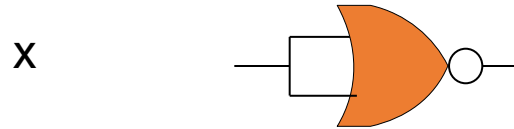




Designs with NAND gates


Example 1/2

- A function:
 - $F_1 = x' y + x y'$

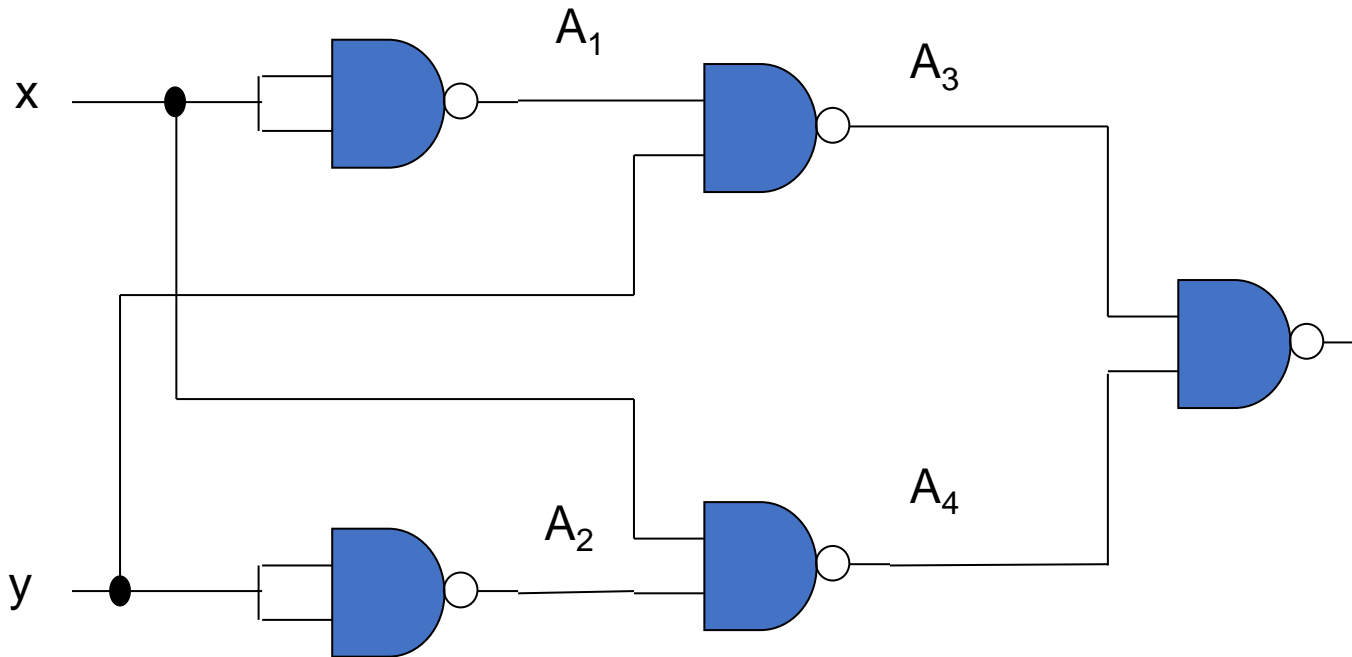

Example 2/2

$$\blacksquare F_2 = x' y' + xy'$$

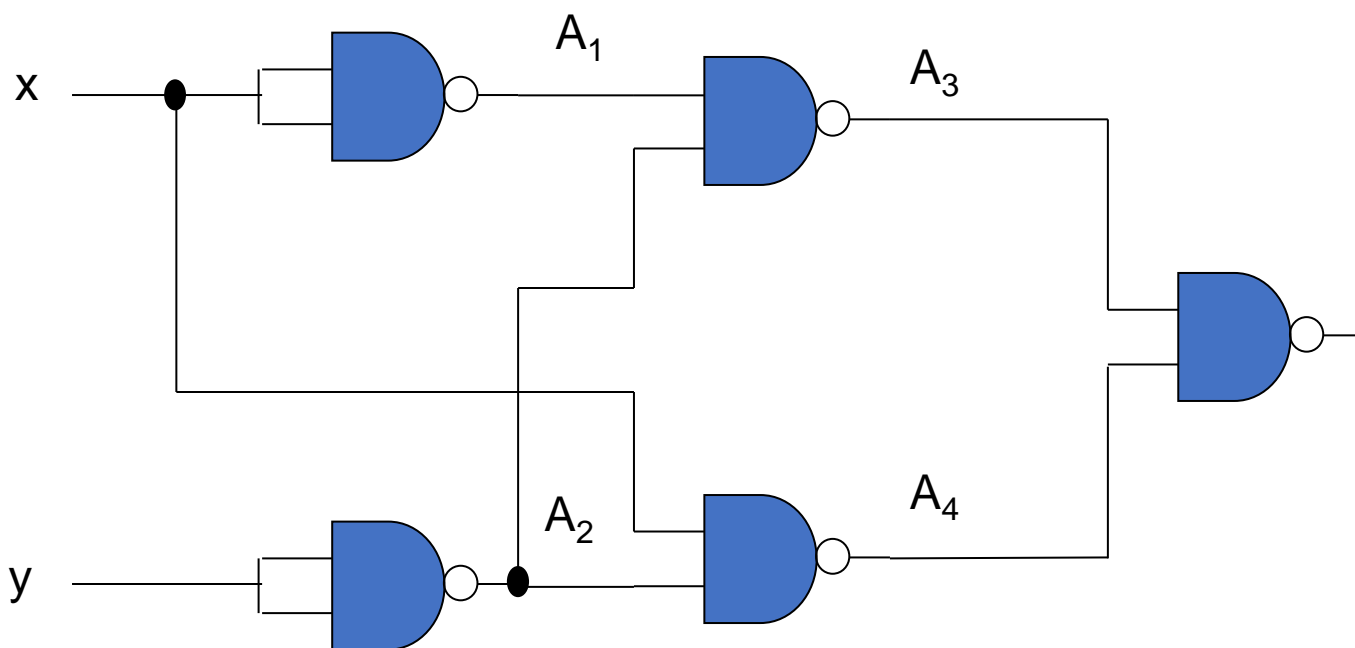

Multiple Input Gates

- AND and OR operations:
 - They are both commutative and associative
 - No problem with extending the number of inputs
- NAND and NOR operations:
 - they are both commutative but not associative
 - Extending the number of inputs is not obvious
- Example: NAND gates
 - $((xy)'z)' \neq (x(yz)')'$
 - $((xy)'z)' = ?$
 - $(x(yz)')' = ?$

Nonassociativity of NOR operation


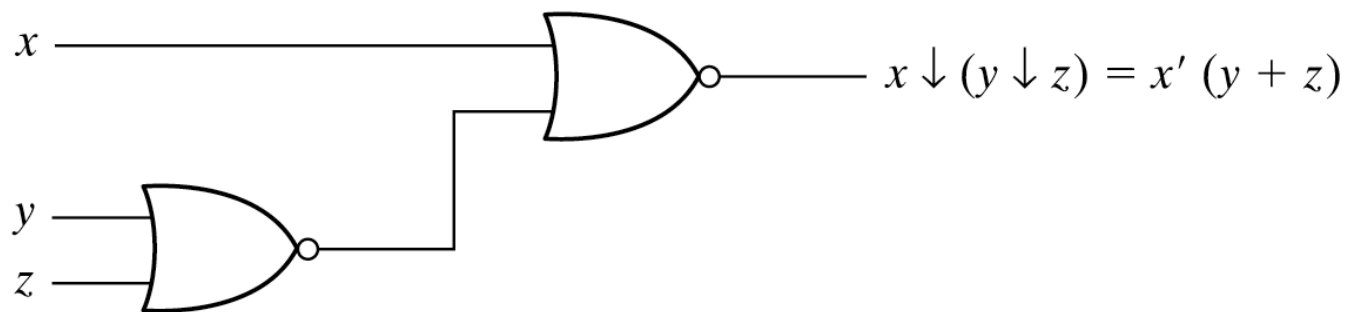
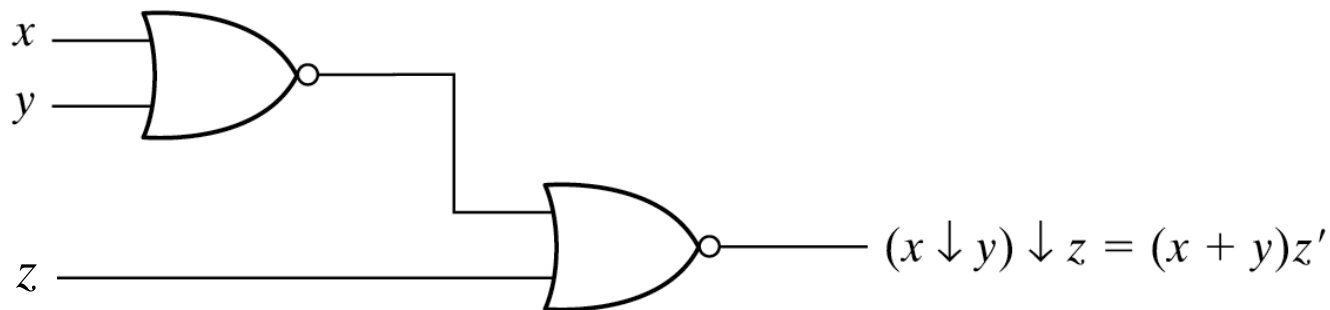


Fig. 2-6 Demonstrating the nonassociativity of the NOR operator; $(x \downarrow y) \downarrow z \neq x \downarrow (y \downarrow z)$


Multiple Input Universal Gates

- To overcome this difficulty, we define multiple-input NAND and NOR gates in slightly different manner


Three input NAND gate: $(x y z)'$

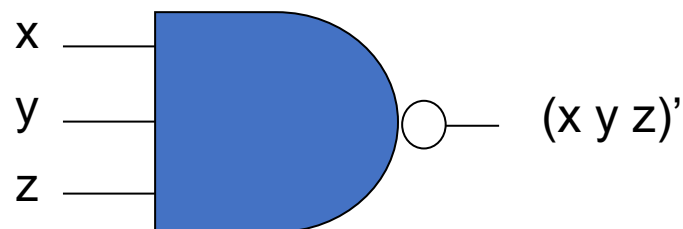


Three input NOR gate: $(x + y + z)'$

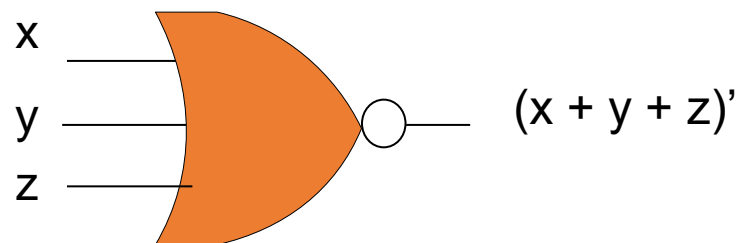


Multiple Input Universal Gates

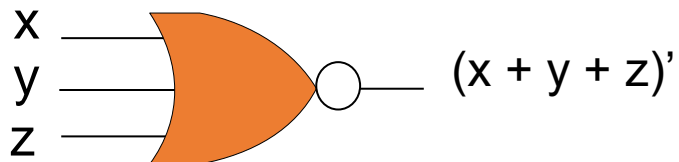

3-input NOR gate

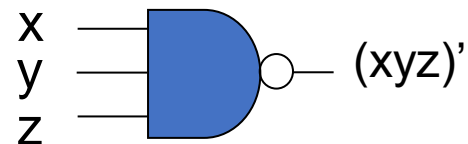


3-input NAND gate

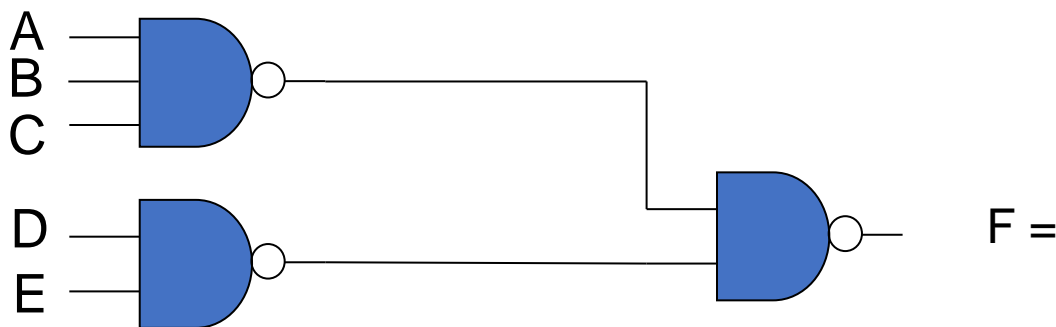


Cascaded NAND gates

XOR and XNOR Gates

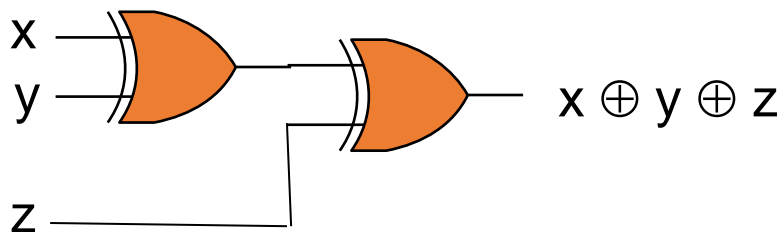
- XOR and XNOR operations are both commutative and associative.
- No problem manufacturing multiple input XOR and XNOR gates
- They are more costly from hardware point of view than AND, OR NAND and NOR gates.



3-input XOR Gates

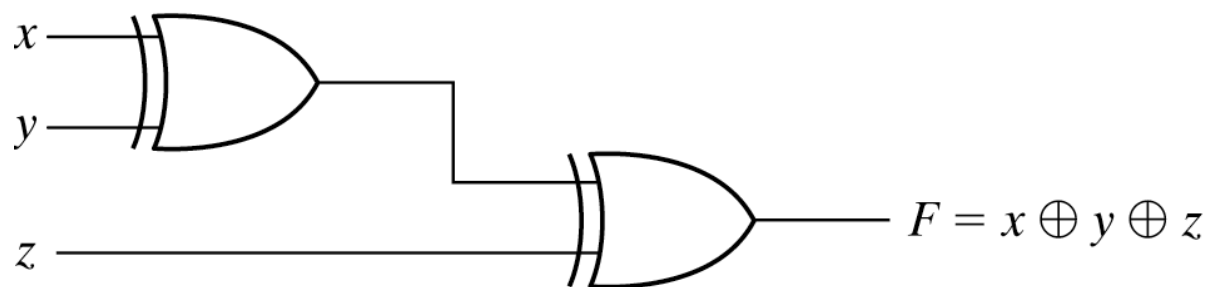

(a) Using 2-input gates

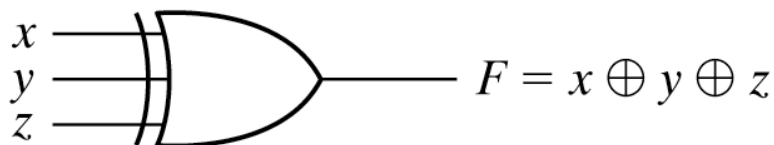

(b) 3-input gate


x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(c) Truth table


Fig. 2-8 3-input exclusive-OR gate

Positive & Negative Logic

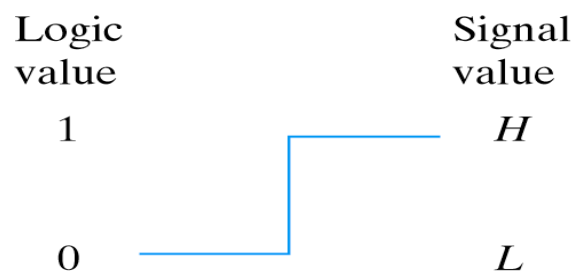- In digital circuits, we have two digital signal levels:
 - H – (higher signal level; e.g. 3 ~ 5 V)
 - L - (lower signal level; e.g. 0 ~ 1 V)
- There is no logic-1 or logic-0 at the circuit level
- We can do any assignment we wish
 - For example:
 - H \rightarrow logic-1
 - L \rightarrow logic-0



(a) Positive logic

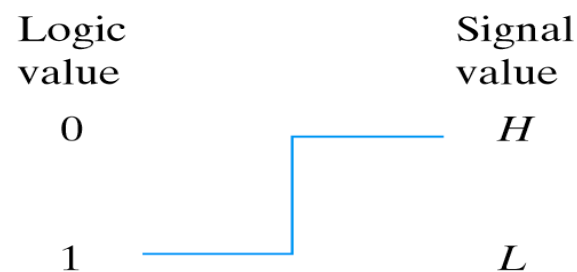


(b) Negative logic

Fig. 2-9 signal assignment and logic polarity



Signal Designation - 1

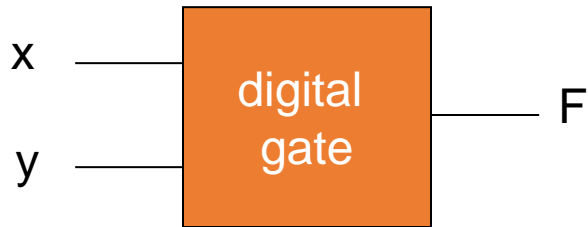


x	y	F
L	L	L
L	H	H
H	L	H
H	H	H

- What kind of logic function does it implement?




Signal Designation - 2

x	y	F
0	0	0
0	1	1
1	0	1
1	1	1

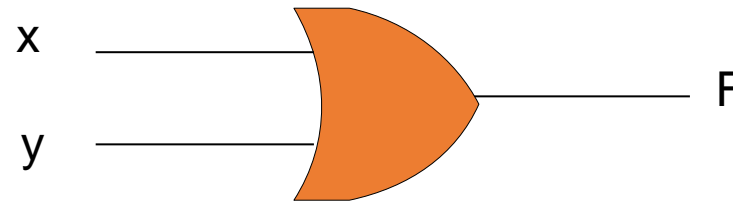

positive logic

x	y	F
1	1	1
1	0	0
0	1	0
0	0	0

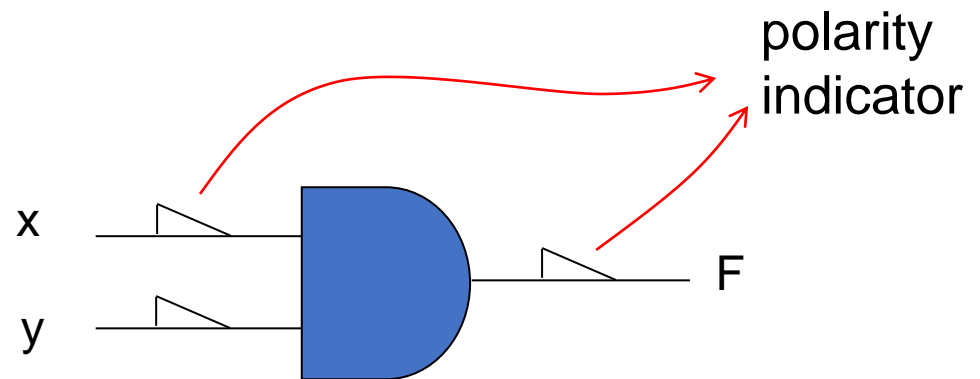

negative logic






Another Example

x	y	F
L	L	H
L	H	H
H	L	H
H	H	L

74LS00

Integrated Circuits

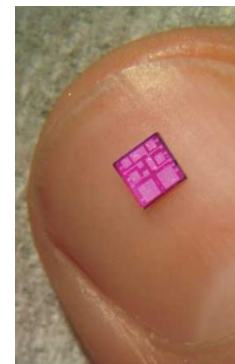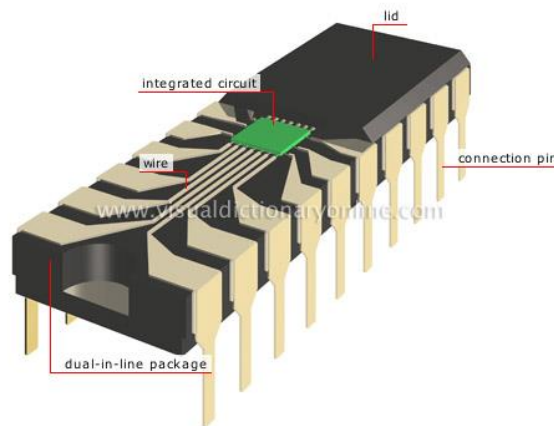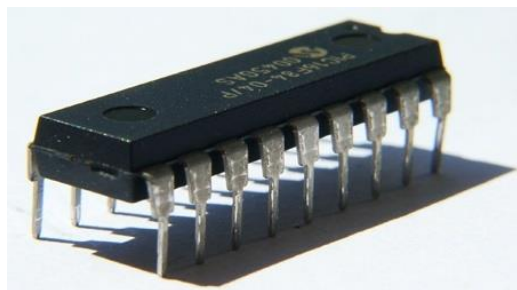- IC – silicon semiconductor crystal (“chip”) that contains gates.
 - gates are interconnected inside to implement a “Boolean” function
 - Chip is mounted in a ceramic or plastic container
 - Inputs & outputs are connected to the external pins of the IC.
 - Many external pins (14 to hundreds)





Levels of Integration

- SSI (small-scale integration):
 - Up to 10 gates per chip
- MSI (medium-scale integration):
 - From 10 to 1,000 gates per chip
- LSI (large-scale integration):
 - thousands of gates per chip
- VLSI (very large-scale integration):
 - hundreds of thousands of gates per chip
- ULSI (ultra large-scale integration):
 - Over a million gates per chip



32 billion transistors




Digital Logic Families

- Circuit Technologies
 - TTL → transistor-transistor logic
 - ECL → Emitter-coupled logic
 - fast
 - MOS → metal-oxide semiconductor
 - high density
 - CMOS → Complementary MOS
 - low power

Parameters of Logic Gates - 1

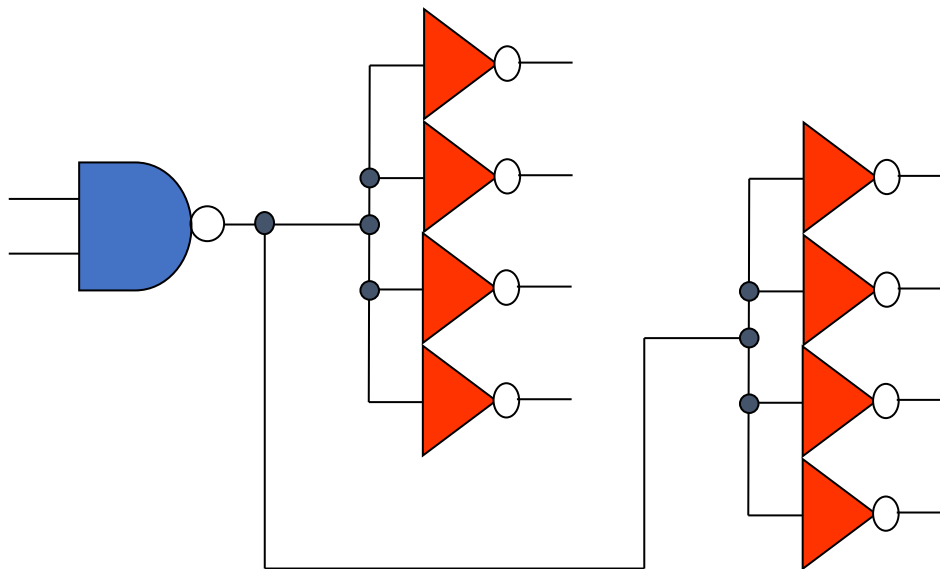- Fan-out
 - load that the output of a gate drives




- If a, say NAND, gate drives four such inverters, then the fan-out is equal to 4.0 standard loads.

Parameters of Logic Gates - 2

- Fan-in
 - number of inputs that a gate can have in a particular logic family
 - In principle, we can design a CMOS NAND or NOR gate with a very large number of inputs
 - In practice, however, we may have some limits
 - 4 for NOR gates
 - 6 for NAND gates
- Power dissipation
 - power needed by the gate that must be available from the power supply



Power Dissipation

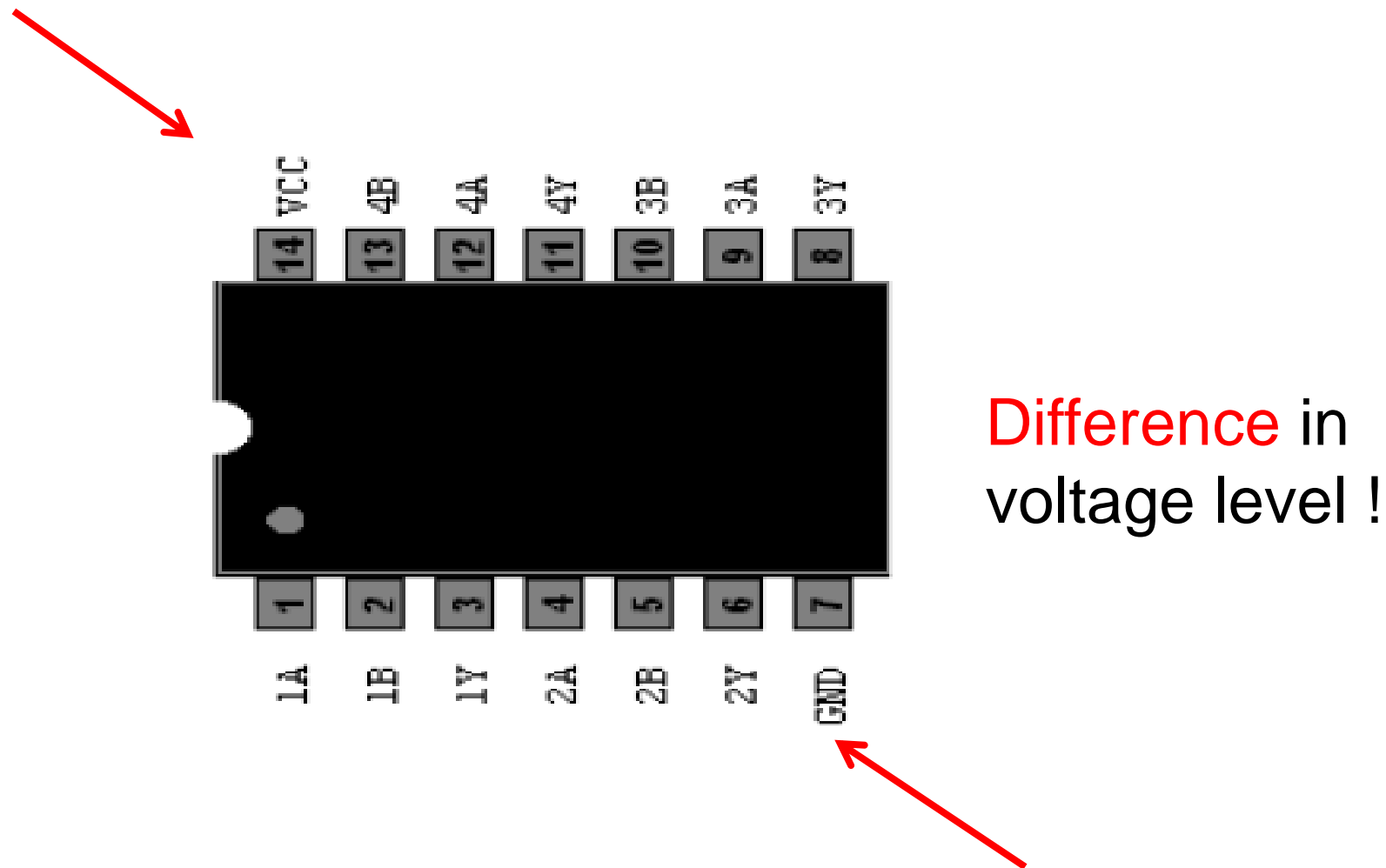

Parameters of Logic Gates - 3

■ Propagation delay:

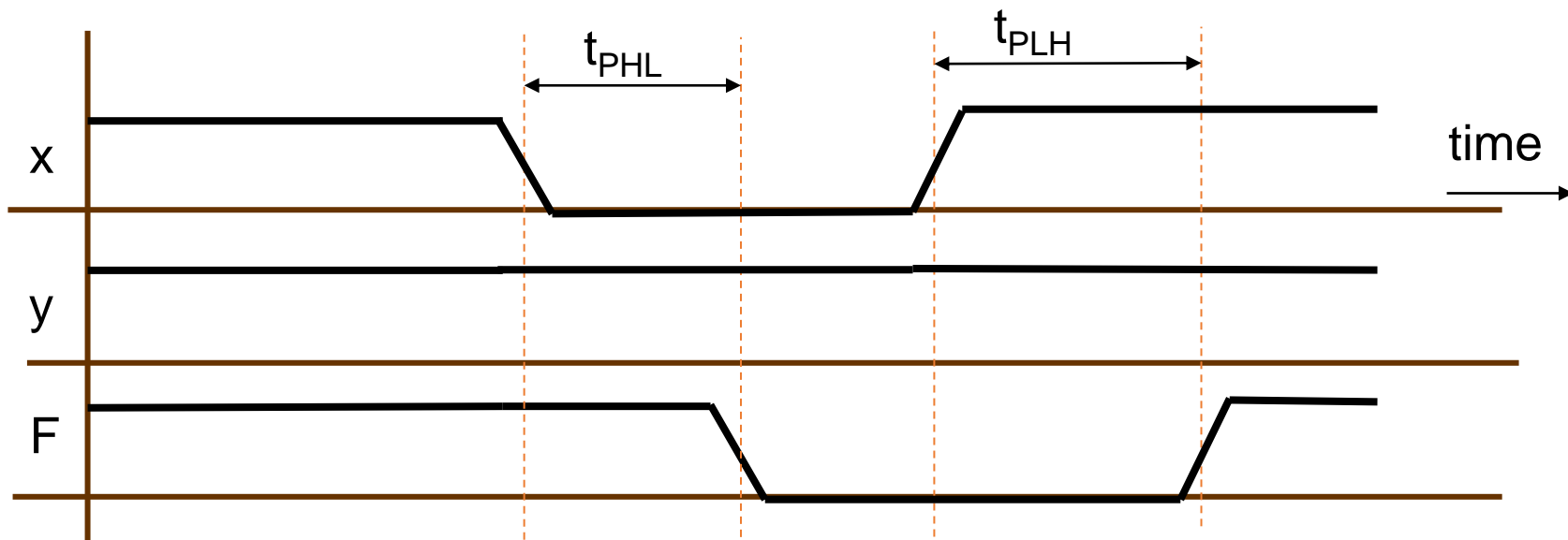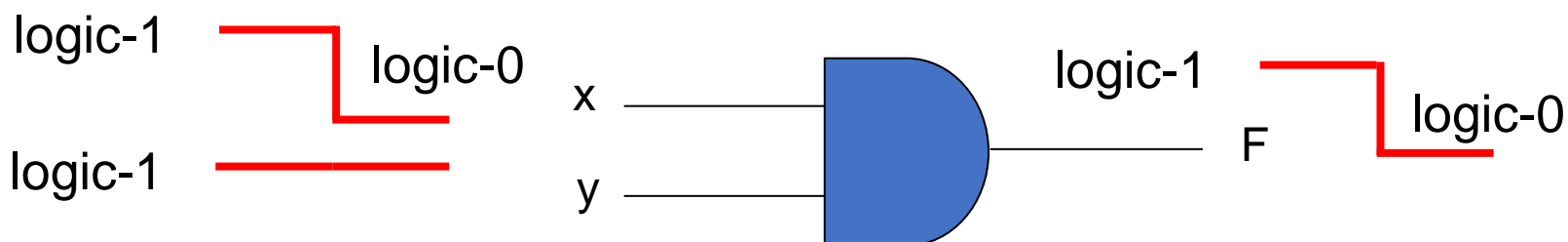- the time required for a change in value of a signal to propagate from input to output.



Computer-Aided Design - 1

- CAD
 - Design of digital systems with VLSI circuits containing millions of transistors is not easy and cannot be done manually.
- To develop & verify digital systems we need CAD tools
 - software programs that support computer-based representation of digital circuits.
- Design process
 - design entry
 - ...
 - database that contains the photomask used to fabricate the IC
 - Configuration file to program FPGA

Computer-Aided Design - 2

- Different physical realizations
 - ASIC (application specific integrated circuit)
 - PLD
 - FPGA
 - Other reconfigurable devices
- For every piece of device we have an array of software tools to facilitate
 - designing,
 - simulating,
 - testing,
 - and even programming




Schematic Editor


- Editing programs for creating and modifying schematic diagrams on a computer screen
 - schematic capturing or schematic entry
 - you can drag-and-drop digital components from a list in an internal library (gates, decoders, multiplexers, registers, etc.)
 - You can draw interconnect lines from one component to another



Schematic Editor

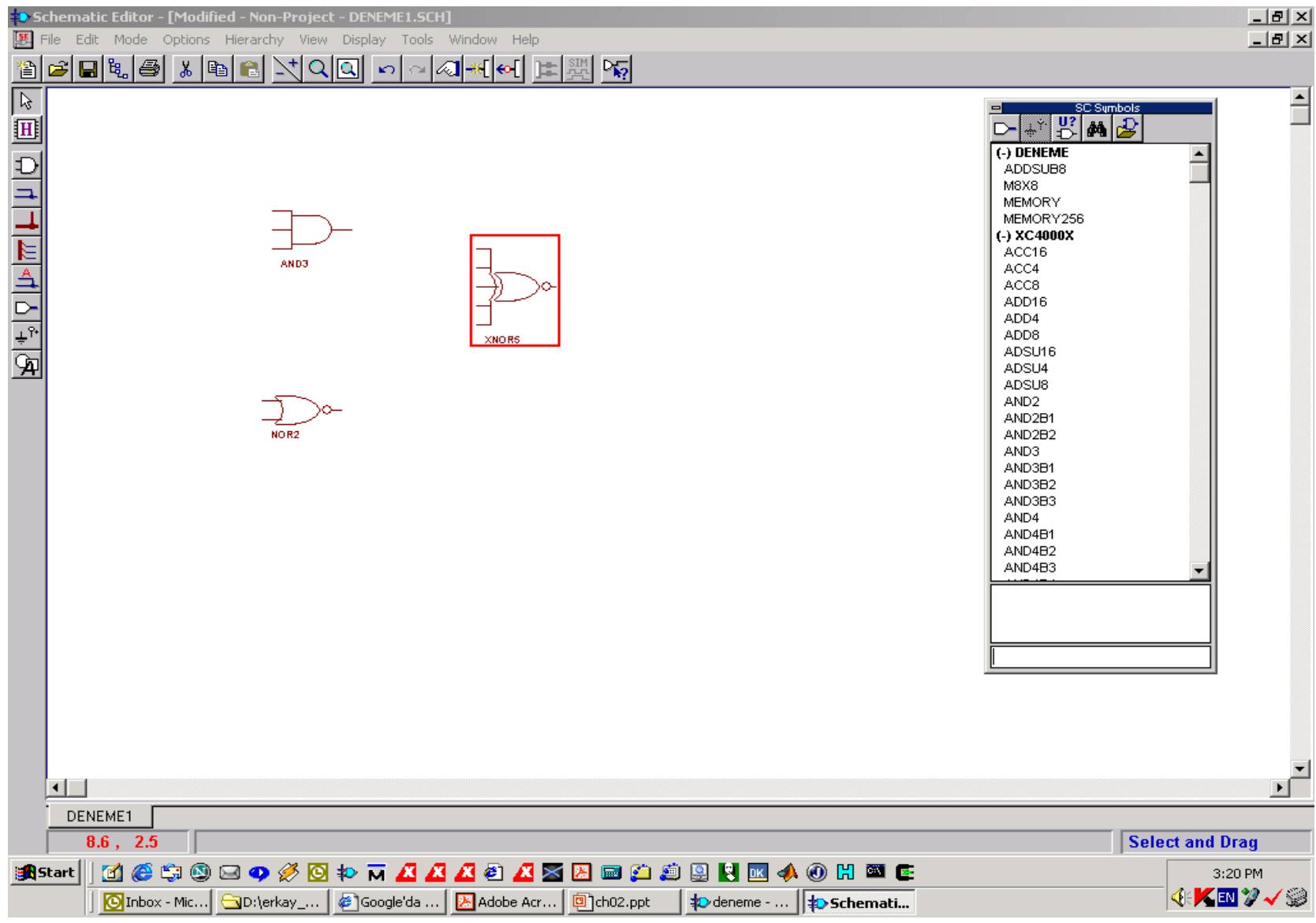


A Schematic Design

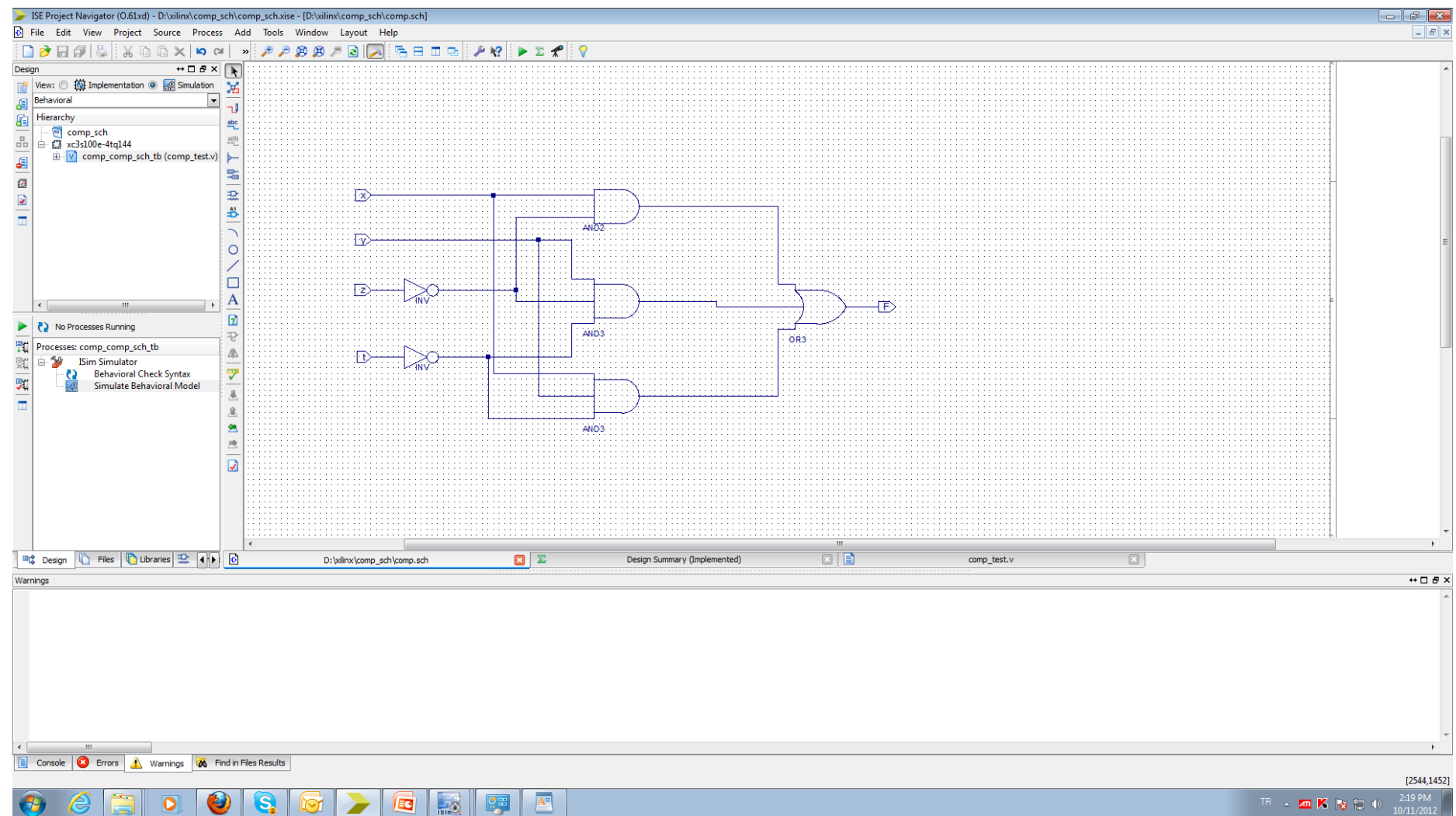

Hardware Description Languages

▪ HDL

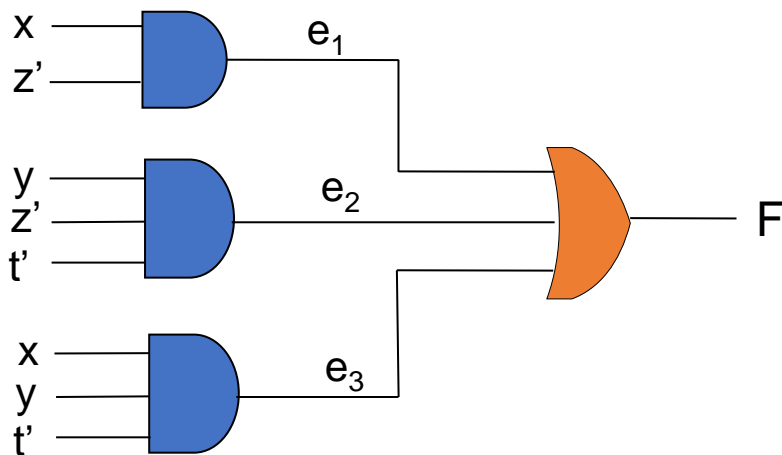- Verilog, VHDL
- resembles a programming language
- designed to describe digital circuits so that we can develop and test digital circuits




$$F(x, y, z, t) = xz' + yz't' + xyt'$$

```
module comp(F, x, y, z, t);  
    input x, y, z, t;  
    output F;  
    wire e1, e2, e3;  
    and g1(e1, x, ~z);  
    and g2(e2, y, ~z, ~t);  
    and g3(e3, x, y, ~t);  
    or g4(F, e1, e2, e3);  
endmodule
```




Simulation Results 1/3

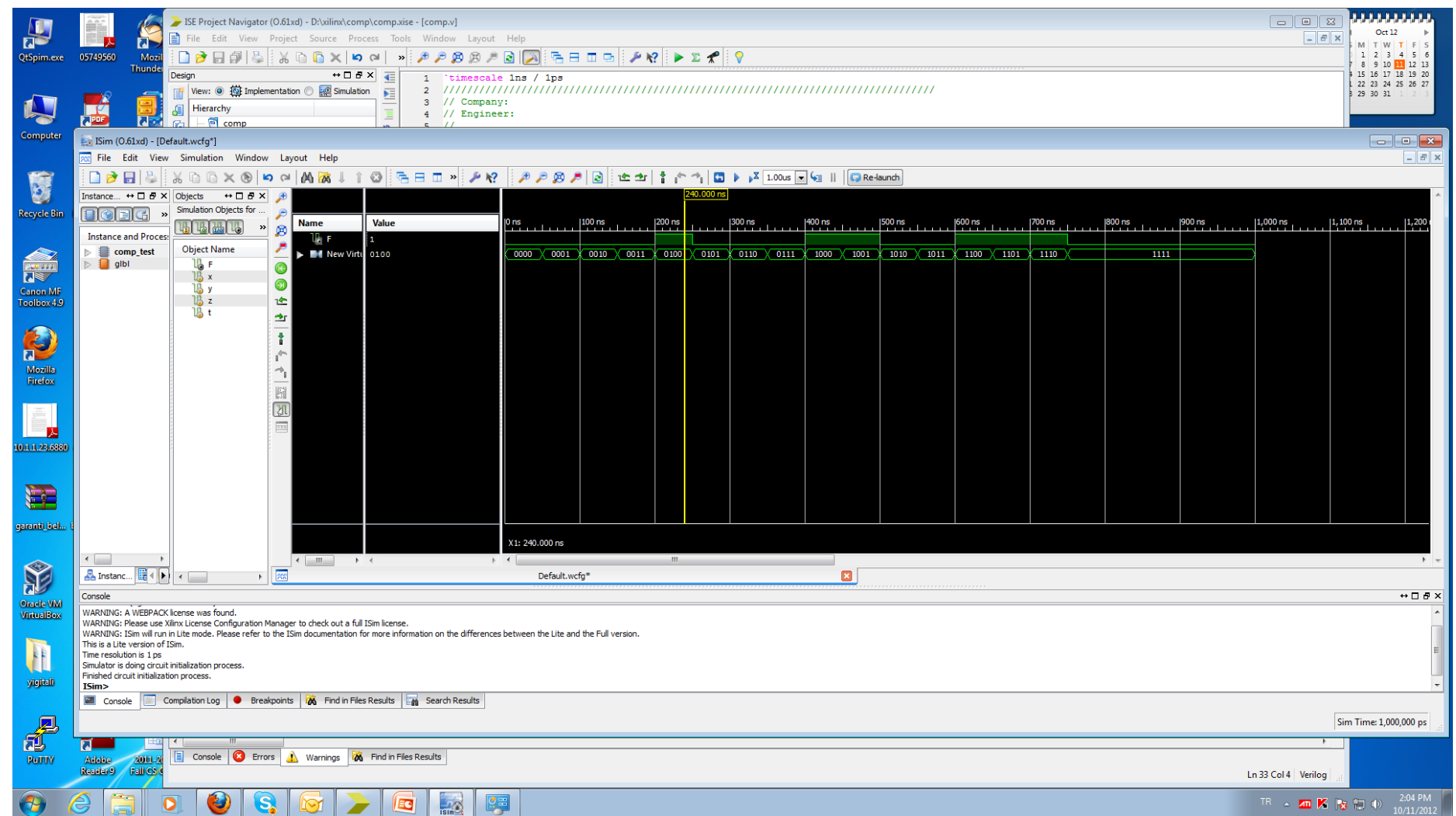



Simulation Results 2/3

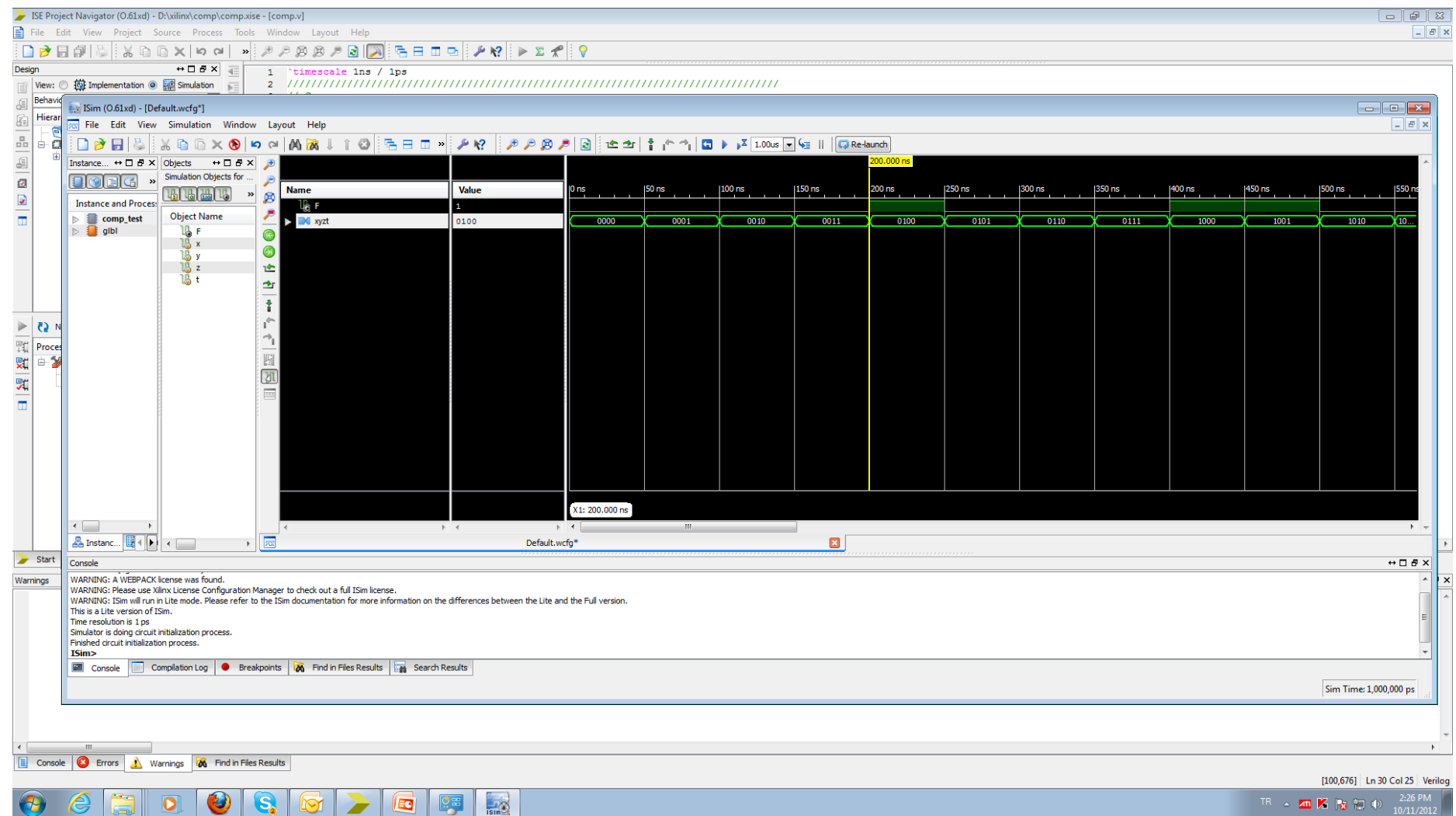

Simulation Results 3/3

