

# **CS 303**

# **Logic & Digital System Design**

---

**Ömer Ceylan**

**. Sabancı .  
Universitesi**



# **Chapter 6**


## **Registers & Counters**

---

- Registers are clocked sequential circuits
- A register is a group of flip-flops
  - Each flip-flop capable of storing one bit of information
  - An n-bit register
    - consists of n flip-flops
    - capable of storing n bits of information
  - besides flip-flops, a register usually contains combinational logic to perform some simple tasks
  - In summary
    - flip-flops to hold information
    - combinational logic to control the state transition
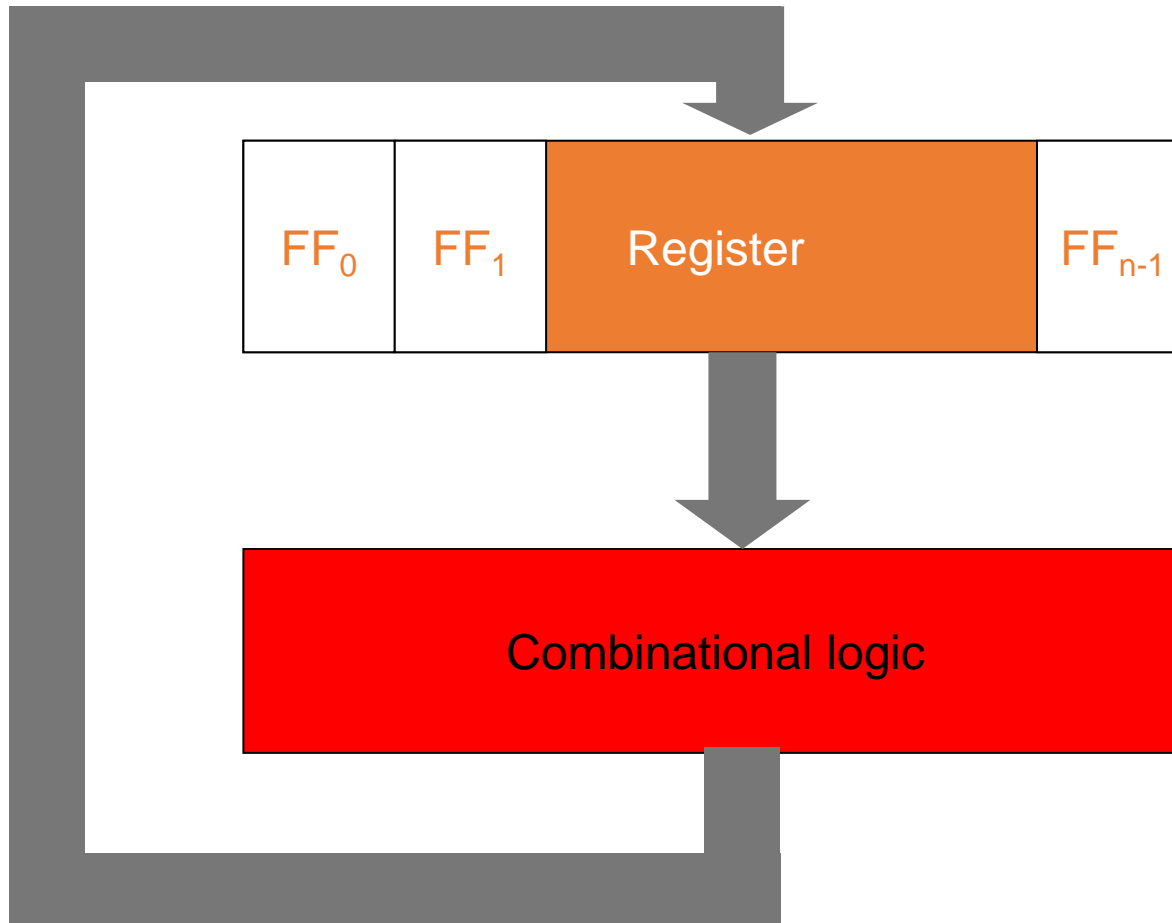
# Counters

- A counter is essentially a register that goes through a predetermined sequence of states
- i.e., “Counting sequence”






# Uses of Registers and Counters


---

- Registers are useful for storing and manipulating information
  - internal registers in microprocessors to manipulate data
- Counters are extensively used in control logic
  - PC (program counter) in microprocessors

# 4-bit Register

 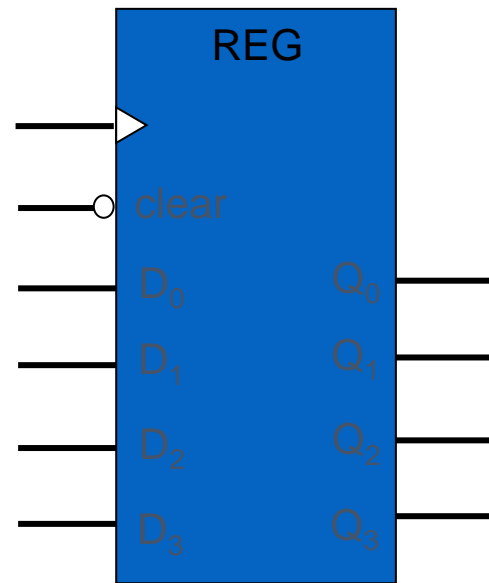 


# Register with Parallel Load

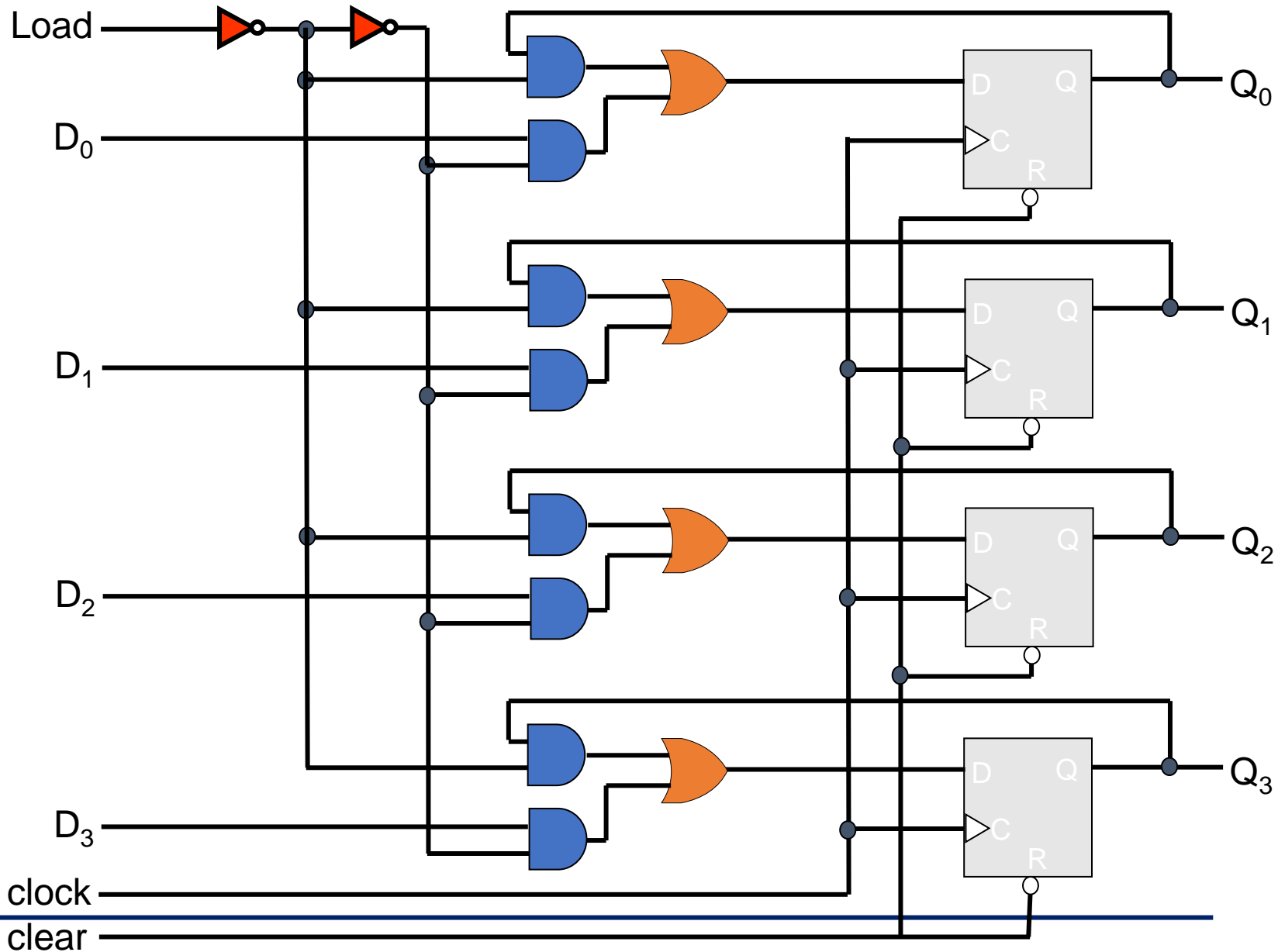




# Register Transfer 1/2

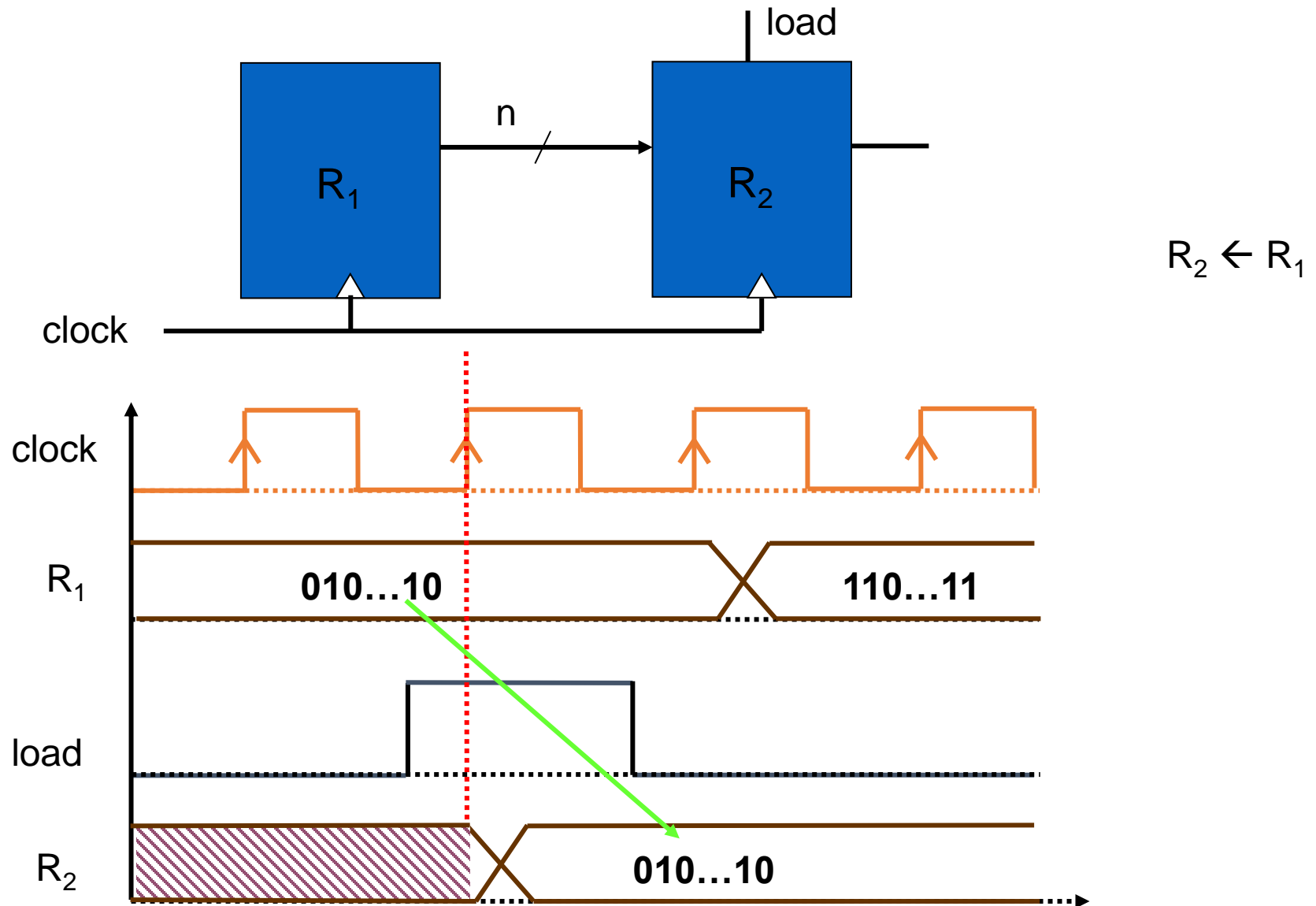






# Register Transfer 2/2

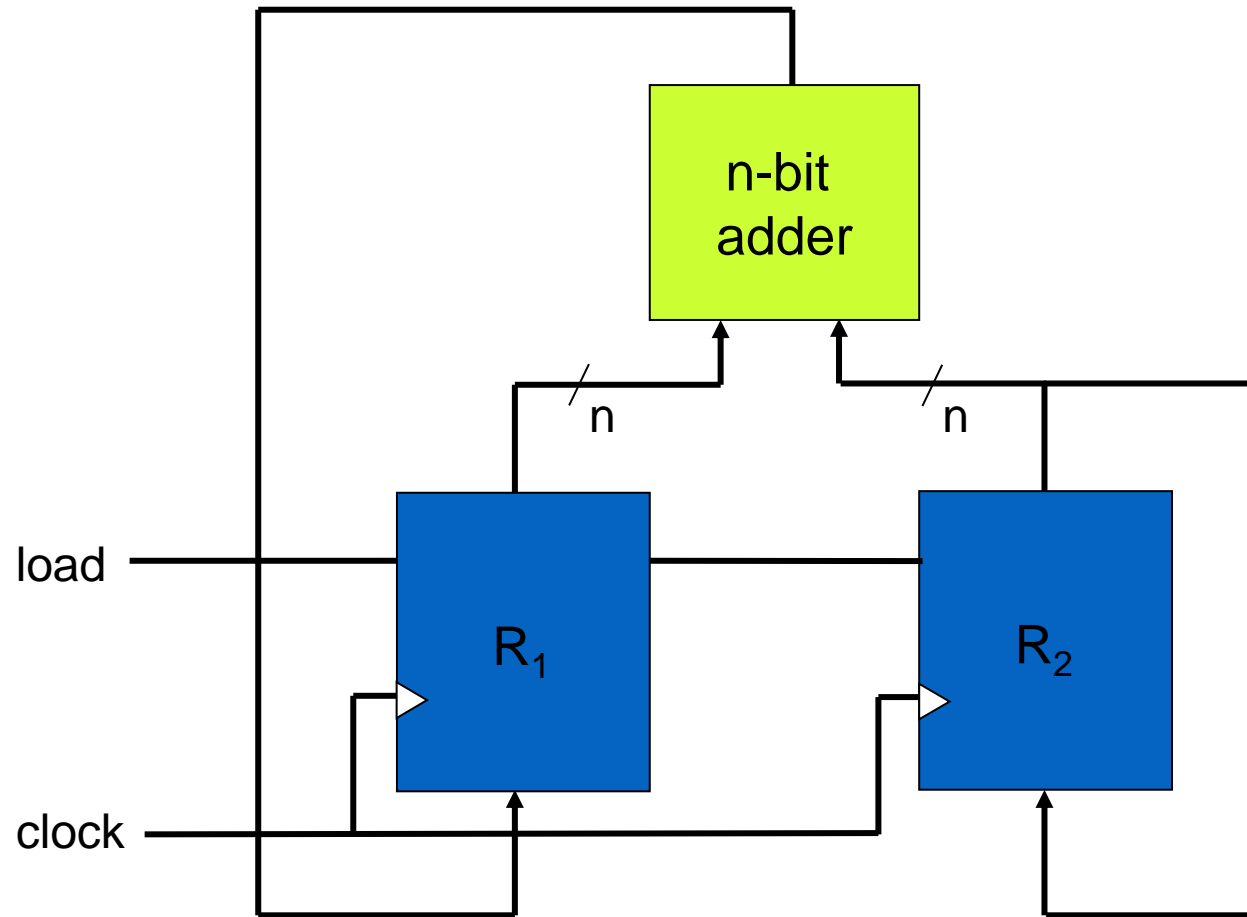

$$R_1 \leftarrow R_1 + R_2$$
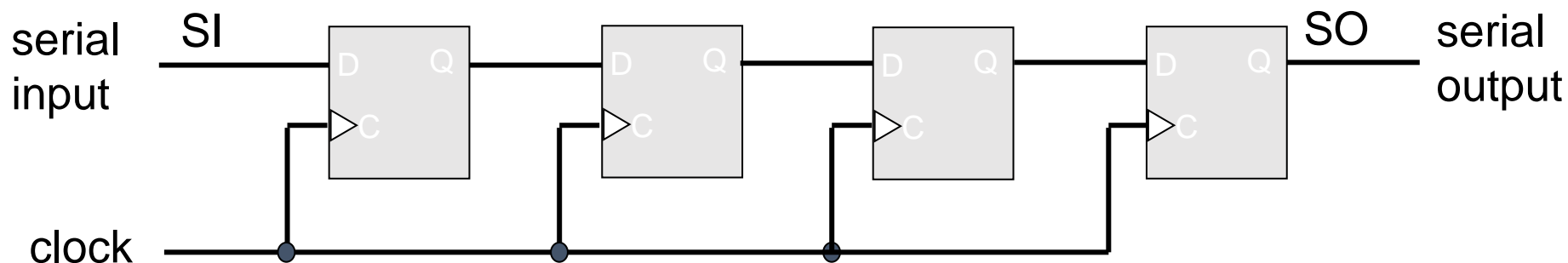
# Shift Registers


- A register capable of shifting its content in one or both directions
  - Flip-flops in cascade



- The state of an n-bit shift register can be transferred in n clock cycles
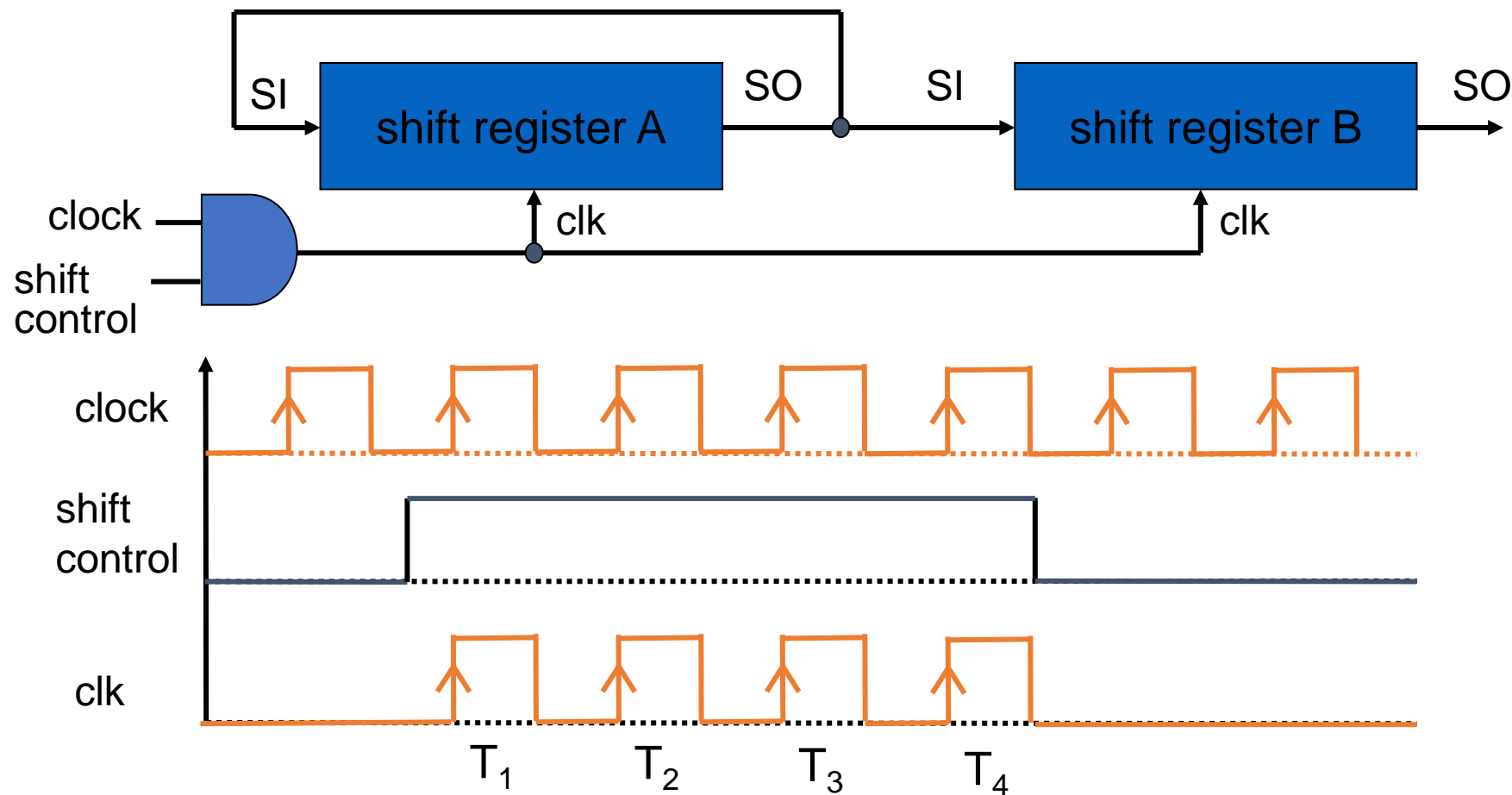
# Serial Mode

- A digital system is said to operate in serial mode when information is transferred and manipulated one bit a time.





# Serial Transfer

- Suppose we have two 4-bit shift registers


$B \leftarrow A$

Timing pulse	Shift register A				Shift register B			
initial value	1	0	1	1	0	0	1	0
After $T_1$								
After $T_2$								
After $T_3$								
After $T_4$	1	0	1	1	1	0	1	1

  

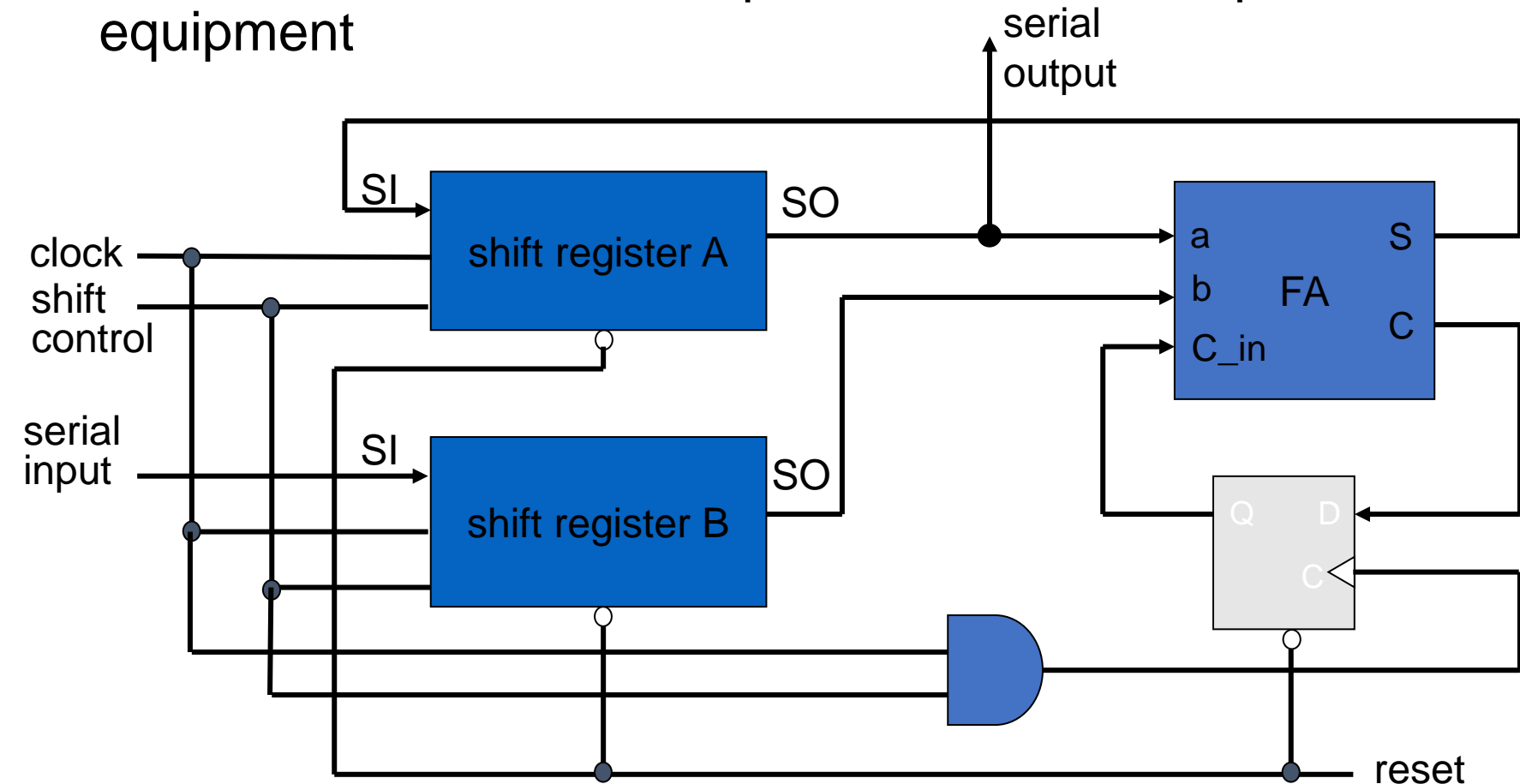
# Serial Addition

- In digital computers, operations are usually executed in parallel, since it is faster
- Serial mode is sometimes preferred since it requires less equipment






- A and B are 2-bit shift registers

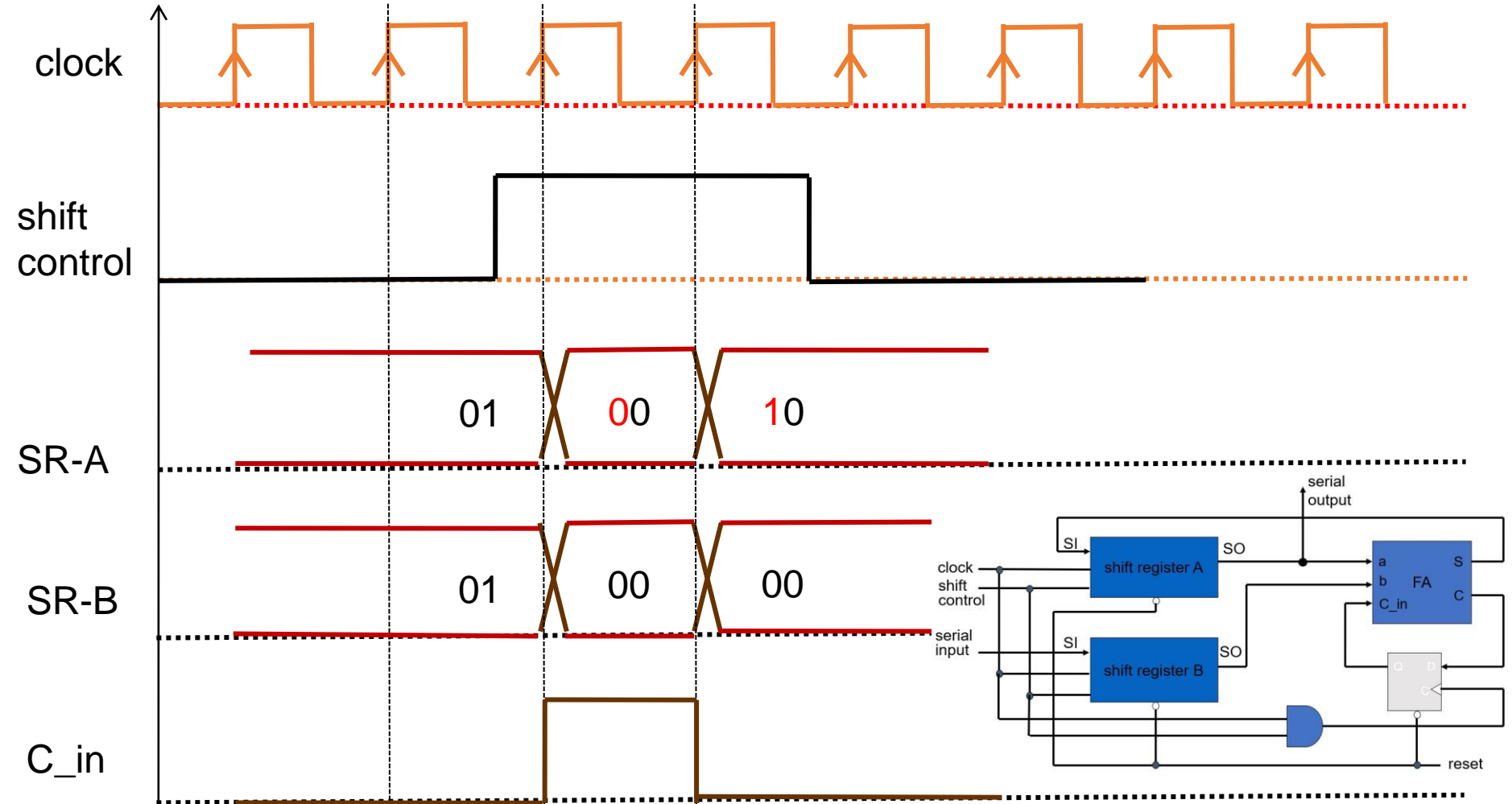


# How to Write Inputs to Registers?

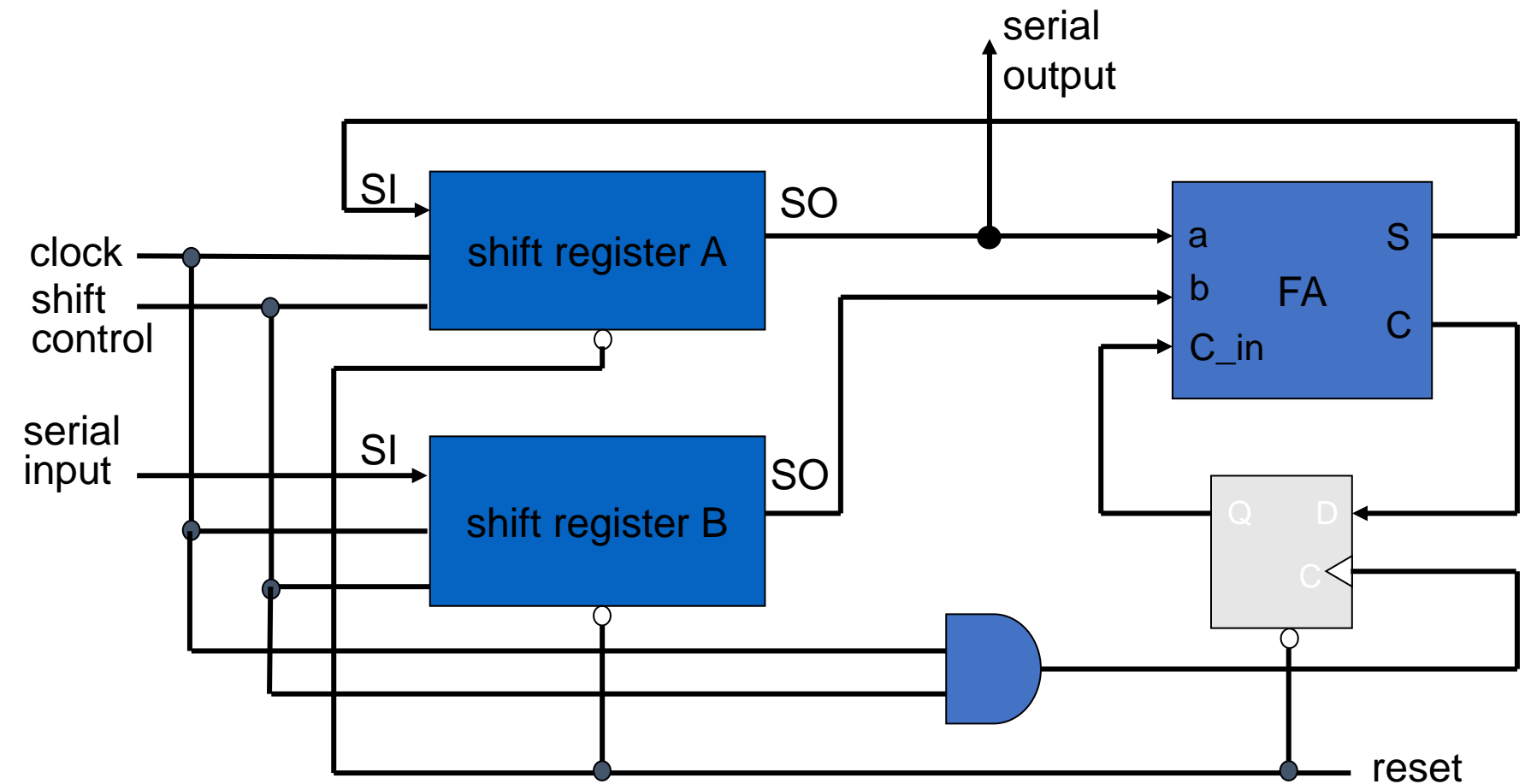



# Example: Serial Addition

- A and B are 2-bit shift registers

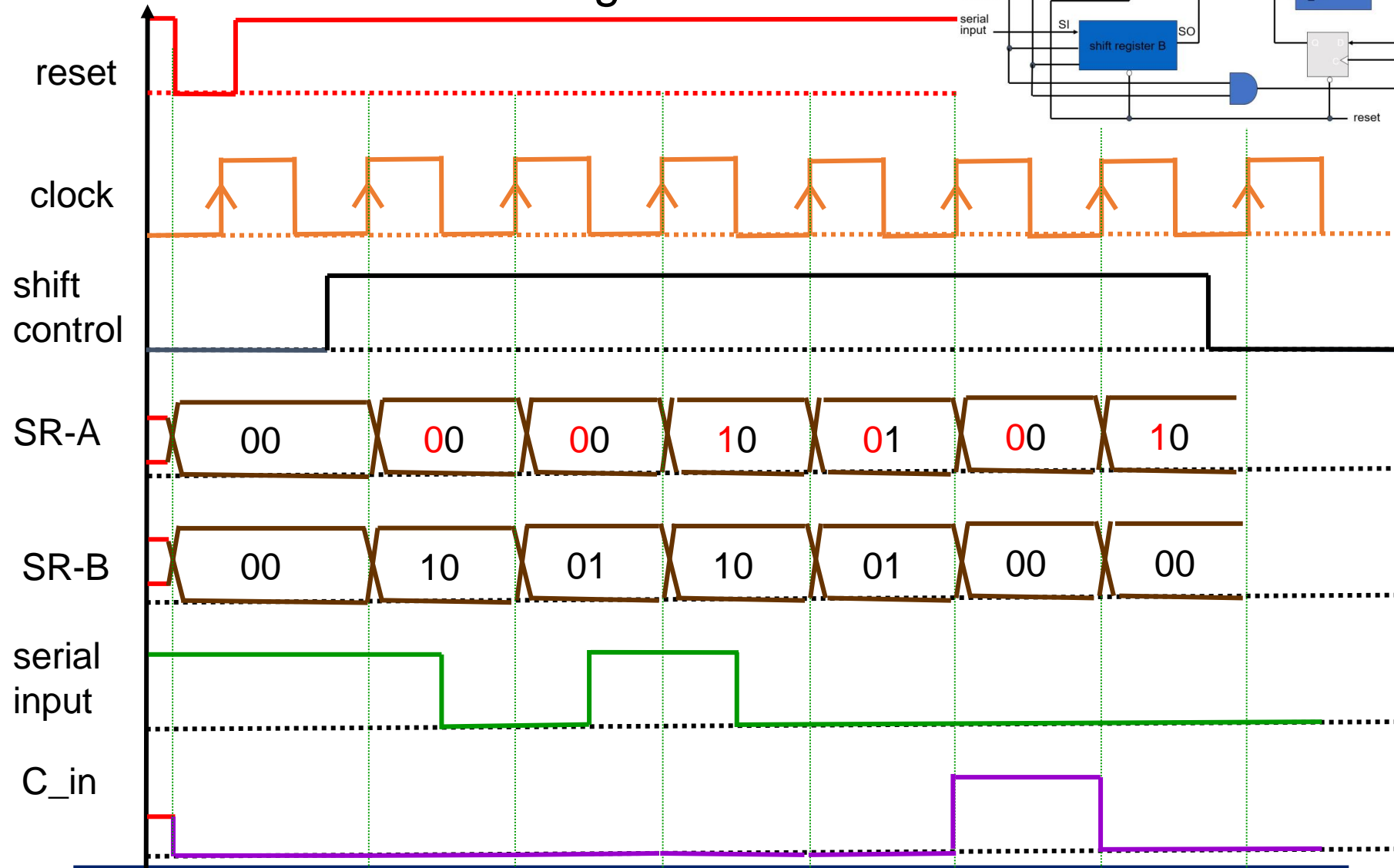






# Universal Shift Register

---

- Capabilities:
  1. A “clear” control to set the register to 0.
  2. A “clock” input
  3. A “shift-right” control
  4. A “shift-left” control
  5. n input lines & a “parallel-load” control
  6. n parallel output lines

# 4-Bit Universal Shift Register

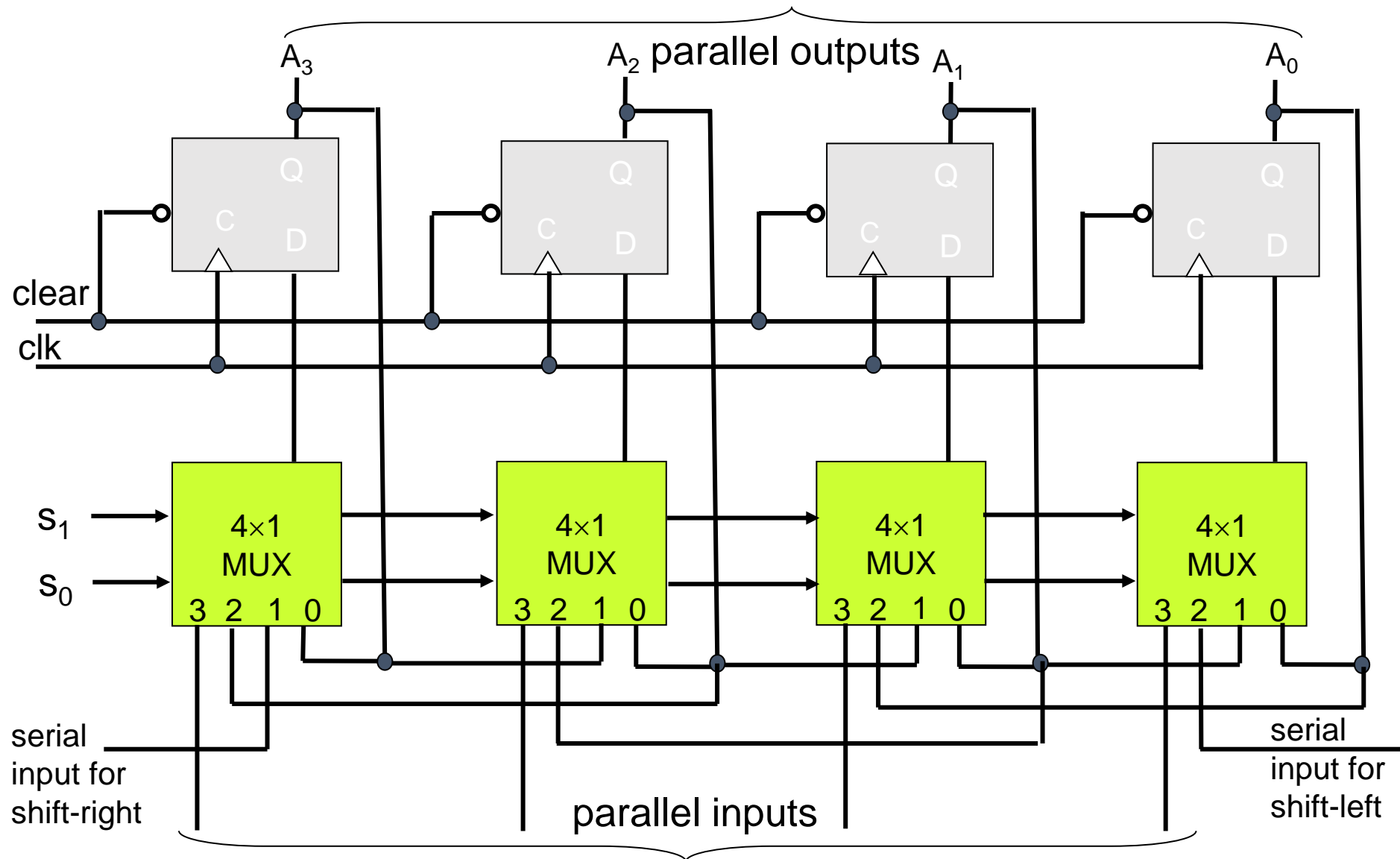



# Universal Shift Register

---

Mode Control		Register operation
$S_1$	$S_0$	
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load



# Coding Universal 32-bit Shift Register

```
module SR_32_BEH(  
    output reg [31:0] A_par,           // Register output  
    input      [31:0] I_par,           // Parallel input  
    input      s1, s0,                 // selection inputs  
                                MSB_in, LSB_in, // Serial inputs  
                                clk, clear);    // clock, reset  
  
    always @(posedge clk, negedge clear)  
        if(~clear) A_par <= 32'h00000000;  
        else  
            case ({s1,s0})  
                2b'00: A_par <= A_par           // no change  
                2b'01: A_par <= {MSB_in, A_par[31:1]}; // shift right  
                2b'10: A_par <= {A_par[30:0], LSB_in}; // shift left  
                2b'11: A_par <= I_par;           // parallel load  
            endcase  
        endmodule
```

# Counters

---

- registers that go through a prescribed sequence of states upon the application of input pulses
  - input pulses are usually clock pulses
- Example: n-bit binary counter
  - count in binary from 0 to  $2^n-1$
- Classification
  1. Synchronous counters
    - flip-flops receive the same common clock as *the* pulse
  2. Ripple counters
    - flip-flop output transition serves as *the* pulse to trigger other flip-flops




# Binary Ripple Counter

3-bit binary ripple counter


0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
0	0	0	0

- Idea:
  - to connect the output of one flip-flop to the C input of the next high-order flip-flop
- We need “complementing” flip-flops
  - We can use T flip-flops to obtain complementing flip-flops or
  - JK flip-flops with its inputs are tied together or
  - D flip-flops with the **complement** output connected to the D input.


# 4-bit Binary Ripple Counter

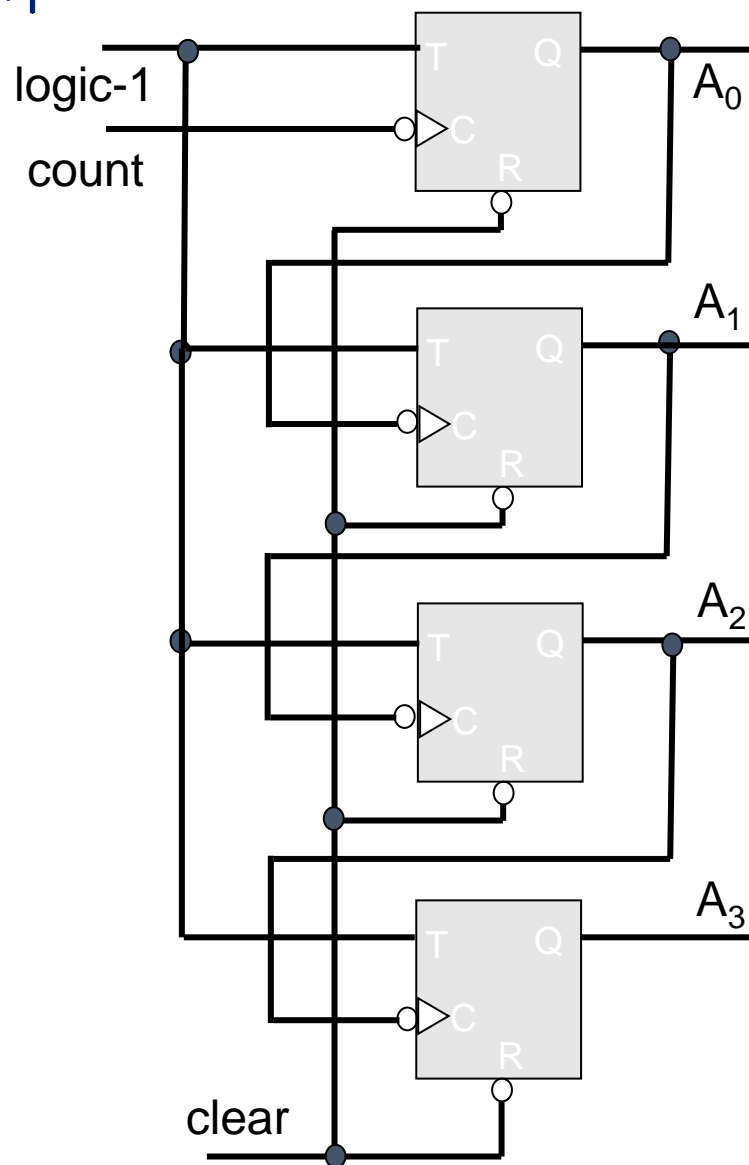

0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0
13	1	1	0	1
14	1	1	1	0
15	1	1	1	1
0	0	0	0	0

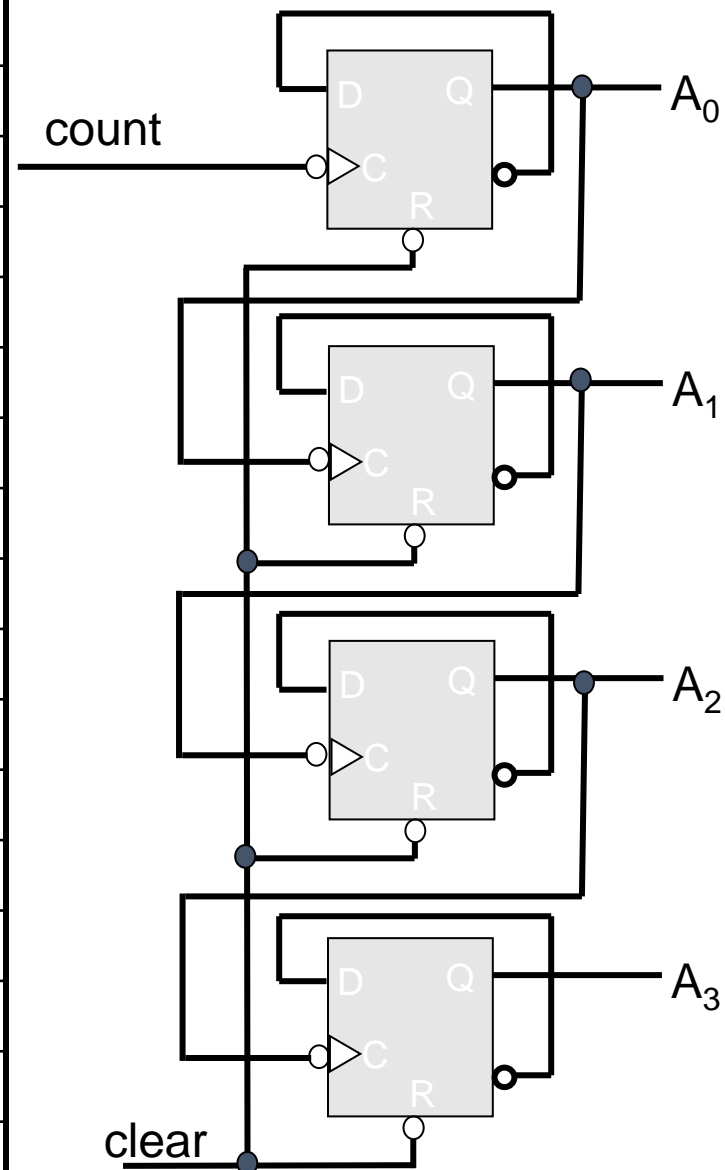

# 4-bit Binary Ripple Counter

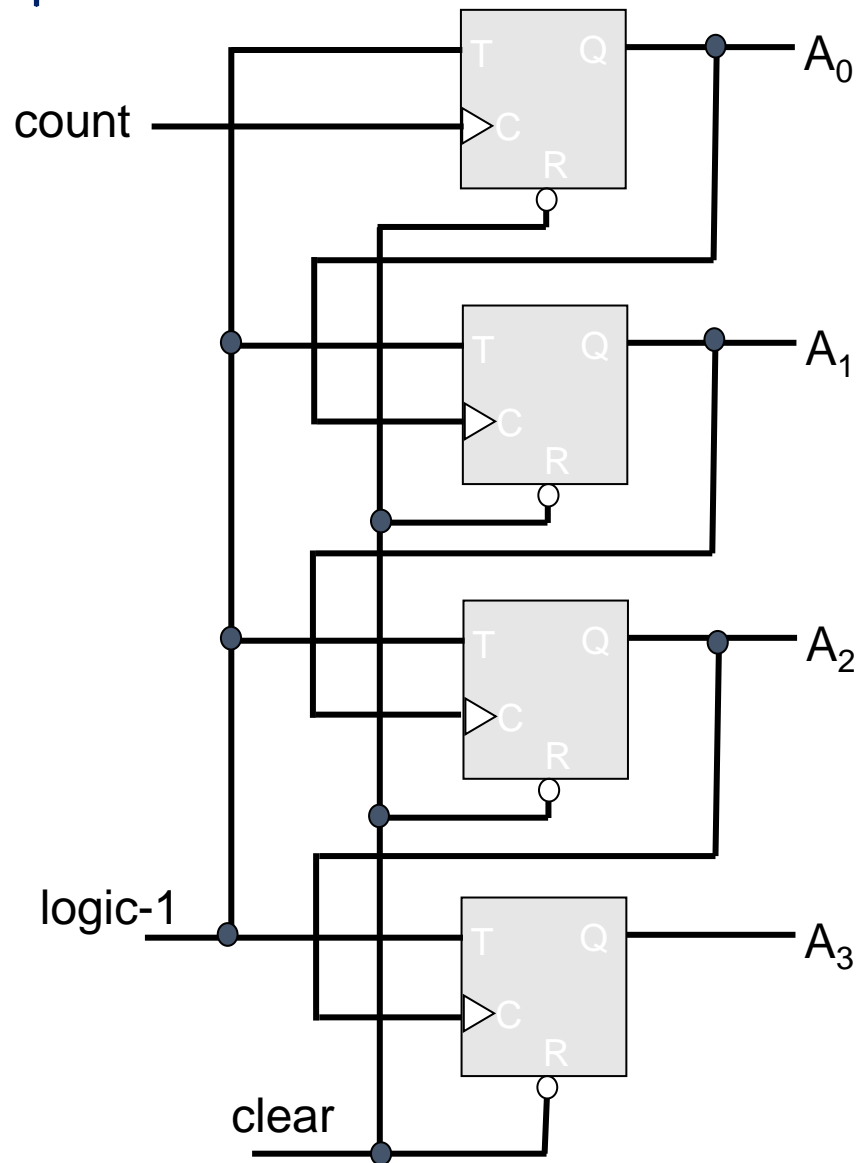


- Suppose the current state is 1100
- What is the next state?


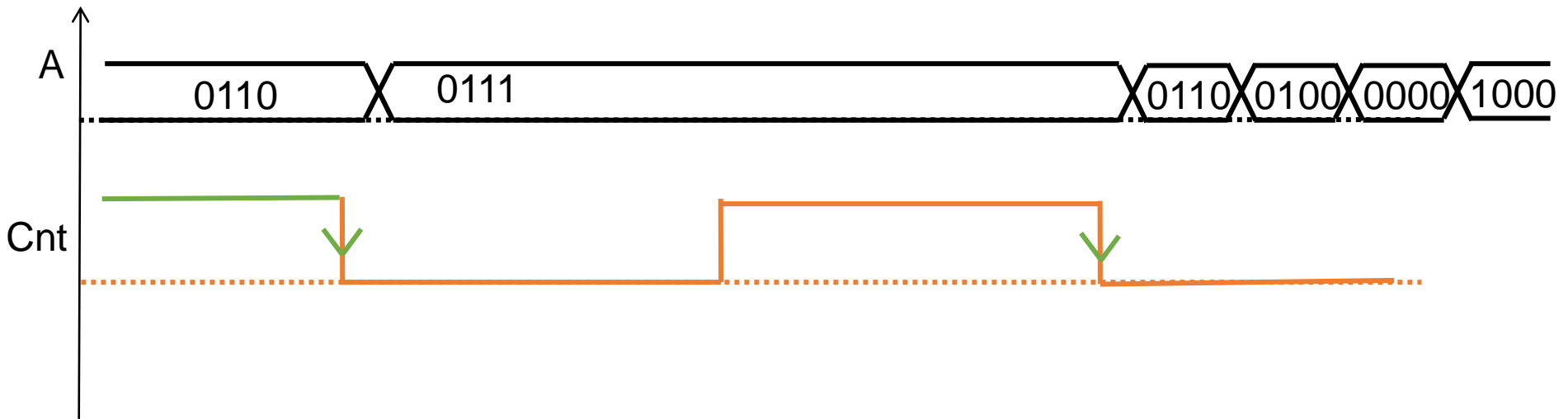
# Verilog of Binary Ripple Counter

```
`timescale 1ns / 1ps
module TFF(Q, T, clk, reset);
    input T,reset,clk;
    output reg Q;
    always @(negedge reset, negedge
clk)
        if(reset) Q <= 1'b0;
        else Q <= #1 T^Q;
endmodule
module RippleCounter(
    output [3:0] A,
    input Count, reset);
    TFF FF0(A[0], 1'b1, Count, reset);
    TFF FF1(A[1], 1'b1, A[0], reset);
    TFF FF2(A[2], 1'b1, A[1], reset);
    TFF FF3(A[3], 1'b1, A[2], reset);
endmodule
```

```
module TestRippleCounter;
    reg Cnt;
    reg Rst;
    wire [3:0] A;
    // Instantiate ripple counter
    RippleCounter Counter(A, Cnt, Rst);
    always
        #5 Cnt = ~Cnt;
    initial
        begin
            Cnt = 1'b0;
            Rst = 1'b0;
            #4 Rst = 1'b1;
        end
    initial #170 $finish;
endmodule
```






# Synchronous Counters


- There is a common clock
  - that triggers all flip-flops simultaneously
  - If  $T = 0$  or  $J = K = 0$  the flip-flop does not change state.
  - If  $T = 1$  or  $J = K = 1$  the flip-flop does change state.
- Design procedure is so simple
  - no need for going through sequential logic design process
  - $A_0$  is always complemented
  - $A_1$  is complemented when  $A_0 = 1$
  - $A_2$  is complemented when  $A_0 = 1$  and  $A_1 = 1$
  - so on

0	0 0 0
1	0 0 1
2	0 1 0
3	0 1 1
4	1 0 0
5	1 0 1
6	1 1 0
7	1 1 1
0	0 0 0


# 4-bit Binary Synchronous Counter

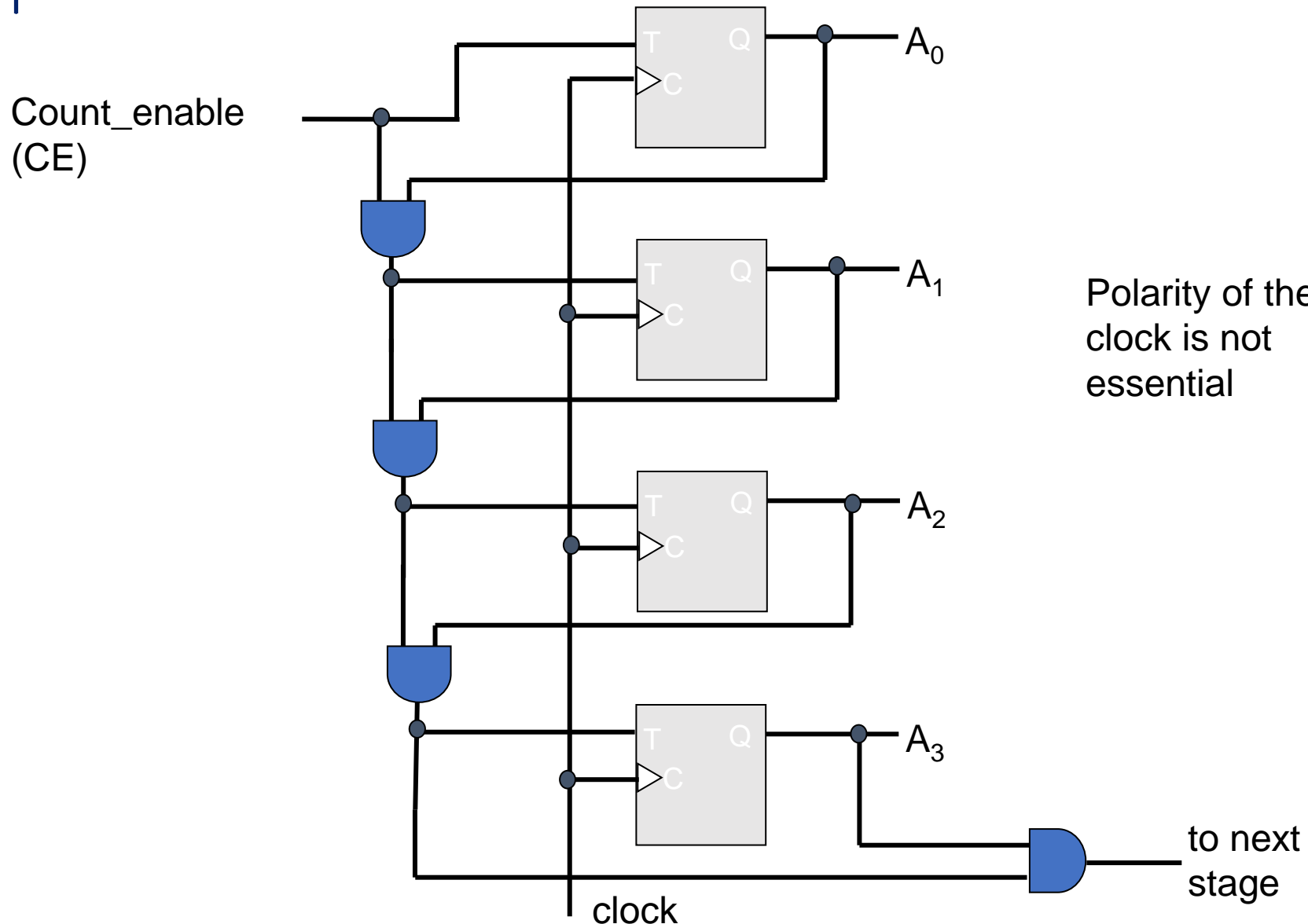

# Timing of Synchronous Counters

 

# Timing of Ripple Counters

 



# Up-Down Binary Counter

- When counting downward
  - the least significant bit is always complemented (with each clock pulse)
  - A bit in any other position is complemented if all lower significant bits are equal to 0.
  - For example:

0 1 0 0

Next state:

  - For example:


1 1 0 0

Next state:

0	0 0 0
7	1 1 1
6	1 1 0
5	1 0 1
4	1 0 0
3	0 1 1
2	0 1 0
1	0 0 1
0	0 0 0




# Up-Down Binary Counter

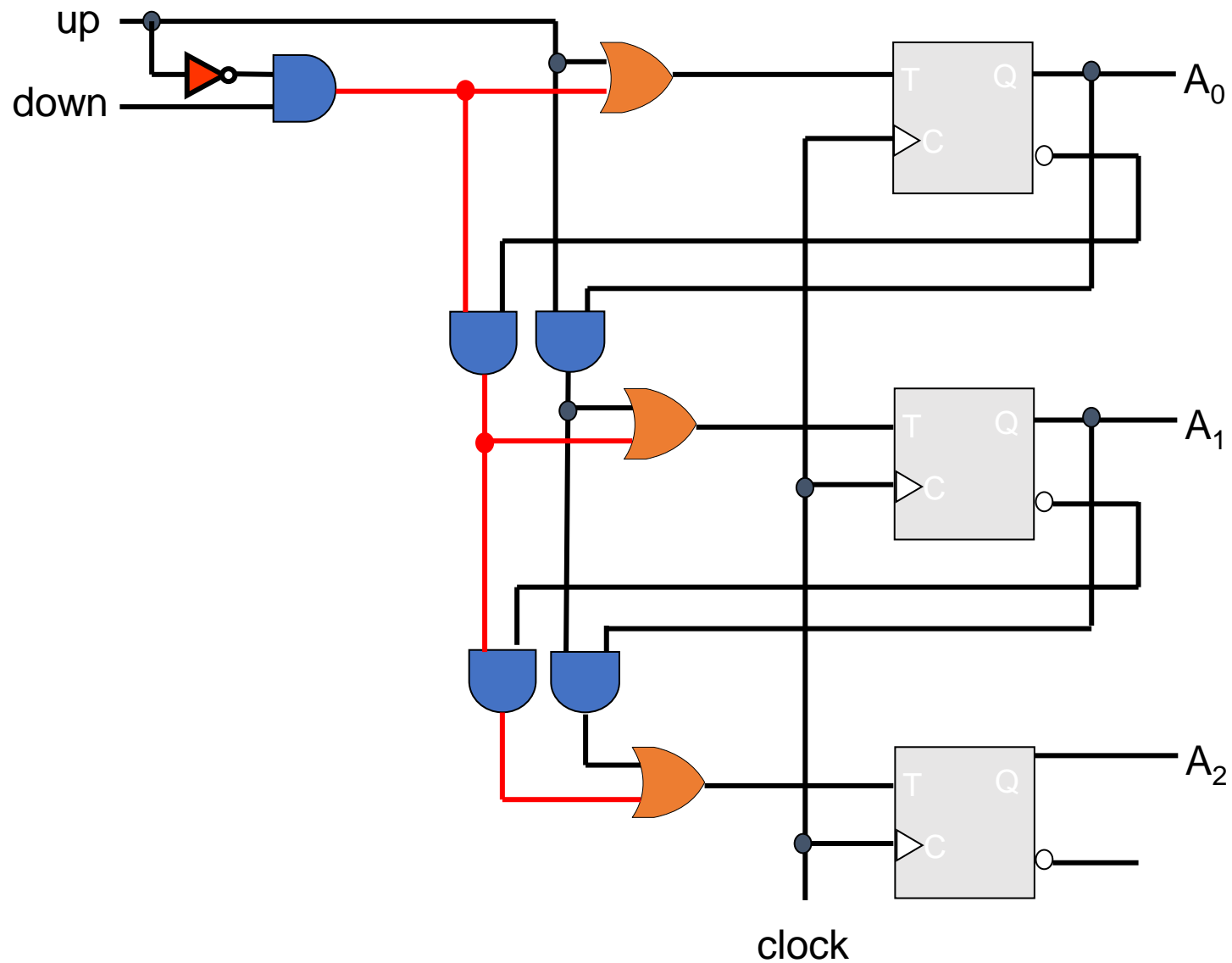



# Binary Counter with Parallel Load

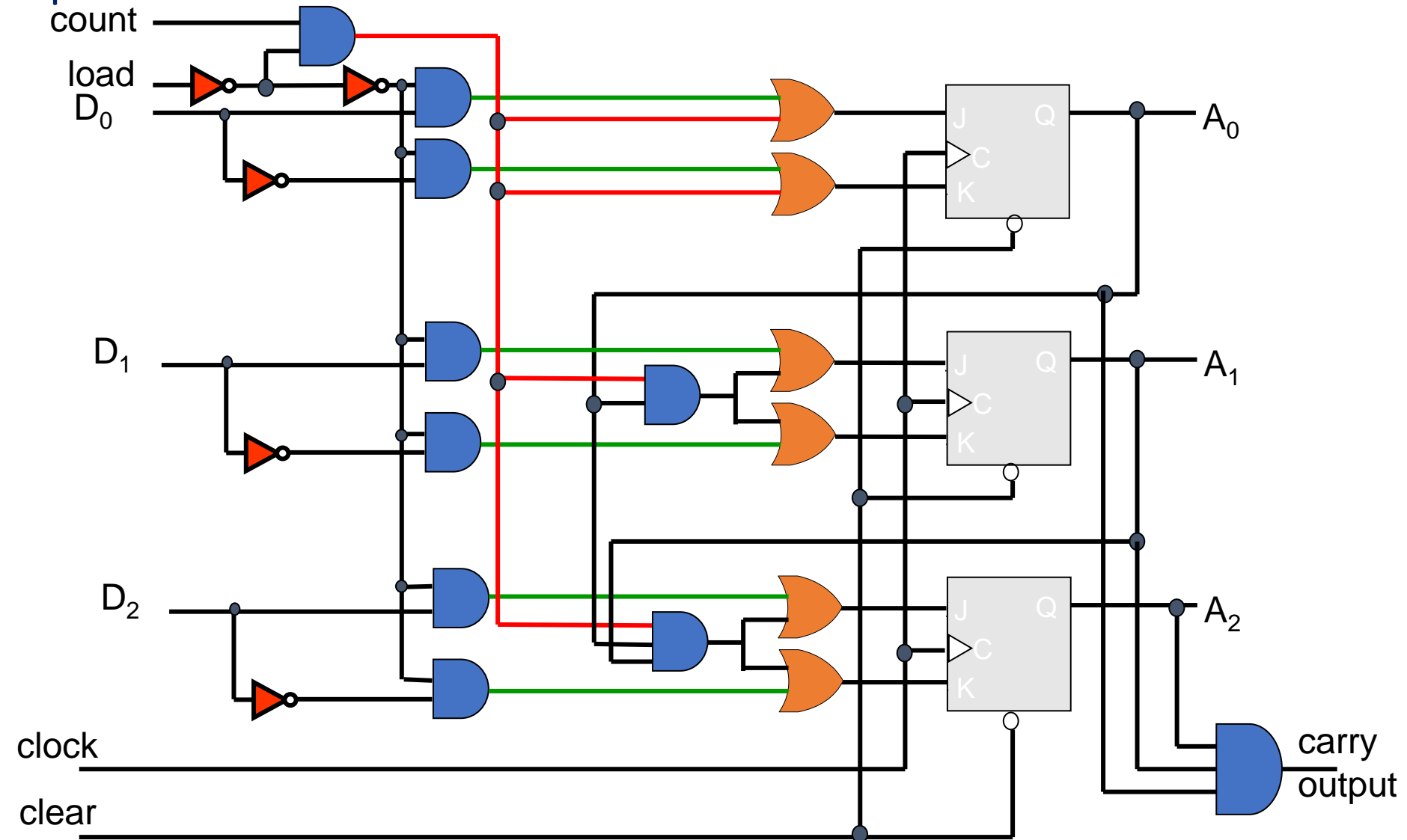

# Binary Counter with Parallel Load

## Function Table

clear	clock	load	Count	Function
0	X	X	X	clear to 0
1	↑	1	X	load inputs
1	↑	0	1	count up
1	↑	0	0	no change



# Verilog of Binary Counter


---

```
module BinaryCounter_8_BEH(  
    output reg [7:0]      A_cnt,           // Counter output  
    output              C_out,           // If a cycle is  
    completed                
    input      [7:0]      Data_in,       // Parallel input  
    input              Count,            // Active high to count  
                                Load,     // Active high to load  
                                clk, clear); // clock, reset  
  
    assign C_out = Count & (~Load) & (A_cnt == 8'hFF);  
    always @(posedge clk, negedge clear)  
        if(~clear) A_cnt <= 8'h00;  
        else if(Load) A_cnt <= Data_in;  
        else if(Count) A_cnt <= A_cnt + 1'b1;  
        else A_cnt <= A_cnt;  
  
endmodule
```

# Other Counters
 
## ▪ Ring Counter

- A ring counter is a circular shift register with only one flip-flop being set at any particular time, all others are cleared.




## • Usage

- Timing signals control the sequence of operations in a digital system


# Ring Counter

- Sequence of timing signals

 
 
# Ring Counter

- To generate  $2^n$  timing signals,
  - we need a shift register with  $2^n$  flip-flops
- or, we can construct the ring counter with a binary counter and a decoder



## Cost:


- 2 flip-flops
- 2-to-4 line decoder

## Cost in general case:

- $n$  flip-flops
- $n$ -to- $2^n$  line decoder
  - $2^n$   $n$ -input AND gates
  - $n$  NOT gates
 
# Johnson Counter

- A k-bit ring counter can generate k distinguishable states
- The number of states can be doubled if the shift register is connected as a switch-tail ring counter



# Johnson Counter


- Count sequence and required decoding

sequence number	Flip-flop outputs				Output
	X	Y	Z	T	
1	0	0	0	0	$S_0 = X'T'$
2					$S_1 = XY'$
3					$S_2 = YZ'$
4					$S_3 = ZT'$
5					$S_4 = XT$
6					$S_5 = X'Y$
7					$S_6 = Y'Z$
8					$S_7 = Z'T$





# Johnson Counter


## ■ Decoding circuit

 

# Unused States in Counters

- 4-bit Johnson counter

  

 



# Johnson Counter

Present State				Next State			
X	Y	Z	T	X	Y	Z	T
0	0	0	0	1	0	0	0
1	0	0	0	1	1	0	0
1	1	0	0	1	1	1	0
1	1	1	0	1	1	1	1
1	1	1	1	0	1	1	1
0	1	1	1	0	0	1	1
0	0	1	1	0	0	0	1
0	0	0	1	0	0	0	0
0	0	1	0	1	0	0	1
1	0	0	1	0	0	0	0
0	1	0	0	1	0	1	0
1	0	1	0	1	1	0	1
1	1	0	1	0	1	1	0
0	1	1	0	1	0	1	1
1	0	1	1	0	1	0	1
0	1	0	1	0	0	1	0

# K-Maps

XY \ ZT					
		00	01	11	10
XY	00	1			1
	01	1			1
	11	1			1
	10	1			1

$$X(t+1) = T'$$

XY \ ZT					
		00	01	11	10
XY	00				
	01				
	11	1	1	1	1
	10	1	0	1	1

$$Y(t+1) = XY + XZ + XT'$$

XY \ ZT					
		00	01	11	10
XY	00				
	01	1	1	1	1
	11	1	1	1	1
	10				

$$Z(t+1) = Y$$

XY \ ZT					
		00	01	11	10
XY	00			1	1
	01			1	1
	11			1	1
	10			1	1

$$T(t+1) = Z$$

# Unused States in Counters

- Remedy  $X(t+1) = T'$        $Y(t+1) = XY + XZ + XT'$   
 $Z(t+1) = Y$        $T(t+1) = Z$

