

CS 303

Logic & Digital System Design

Ömer Ceylan

**. Sabancı .
Universitesi**

Chapter 5

Synchronous Sequential Logic Part II




State Reduction and Assignment

- In the design process of sequential circuits, certain techniques are useful in reducing the circuit complexity
 - state reduction
 - state assignment
- State reduction
 - Fewer states → fewer number of flip-flops
 - m flip-flops → 2^m states
 - Example: $m = 5 \rightarrow 2^m = 32$
 - If we reduce the number of states to 21, do we reduce the number of flip-flops?




Example: State Reduction

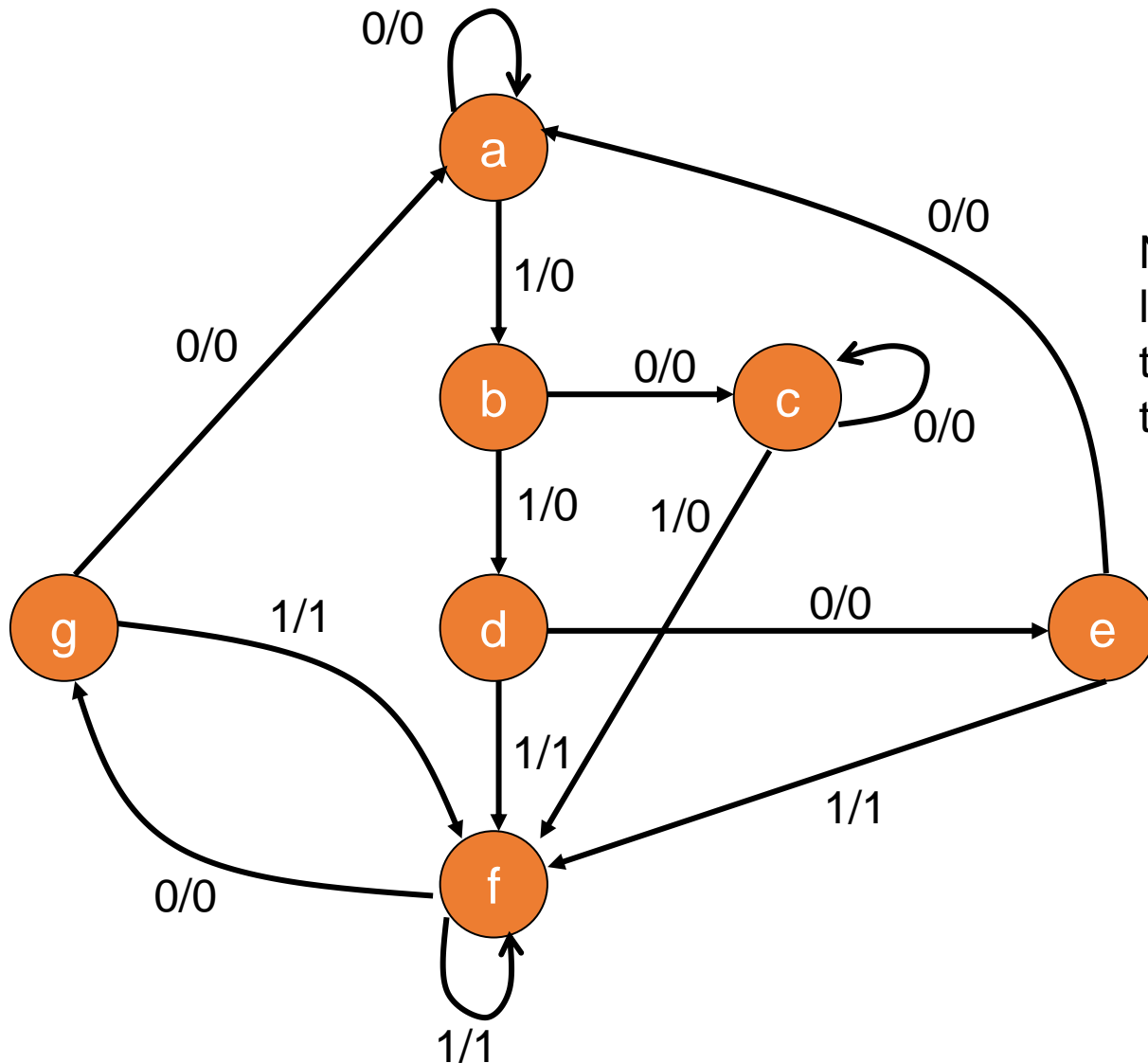

Note that we use letters to designate the states for the time being

State Reduction Technique 1/7

- Step 1: get **a** state table

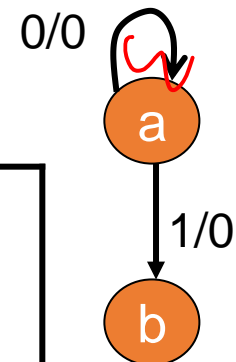

present state	next state		Output	
	x = 0	x = 1	x = 0	x = 1
a	a	b	0	0
b	c	d	0	0
c	c	f	0	0
d	e	f	0	1
e	a	f	0	1
f	g	f	0	1
g	a	f	0	1

State Reduction Technique 2/7

- Step 2: Inspect the state table for equivalent states
 - Equivalent states: Two states,
 1. that produce exactly the same output
 2. whose next states are identical
 - for each input combination

State Reduction Technique 3/7

present state	next state		Output	
	x = 0	x = 1	x = 0	x = 1
a	a	b	0	0
b	c	d	0	0
c	c	f	0	0
d	e	f	0	1
e	a	f	0	1
f	g	f	0	1
g	a	f	0	1

- States “e” and “g” are equivalent
- One of them can be removed

State Reduction Technique 4/7

present state	next state		Output	
	x = 0	x = 1	x = 0	x = 1
a	a	b	0	0
b	c	d	0	0
c	c	f	0	0
d	e	f	0	1
e	a	f	0	1
f	e	f	0	1

- We keep looking for equivalent states

State Reduction Technique 5/7

present state	next state		Output	
	x = 0	x = 1	x = 0	x = 1
a	a	b	0	0
b	c	d	0	0
c	c	d	0	0
d	e	d	0	1
e	a	d	0	1


- We keep looking for equivalent states

State Reduction Technique 6/7

present state	next state		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
a	a	b	0	0
b	b	d	0	0
d	e	d	0	1
e	a	d	0	1

- We stop when there are no equivalent states

State Reduction Technique 7/7

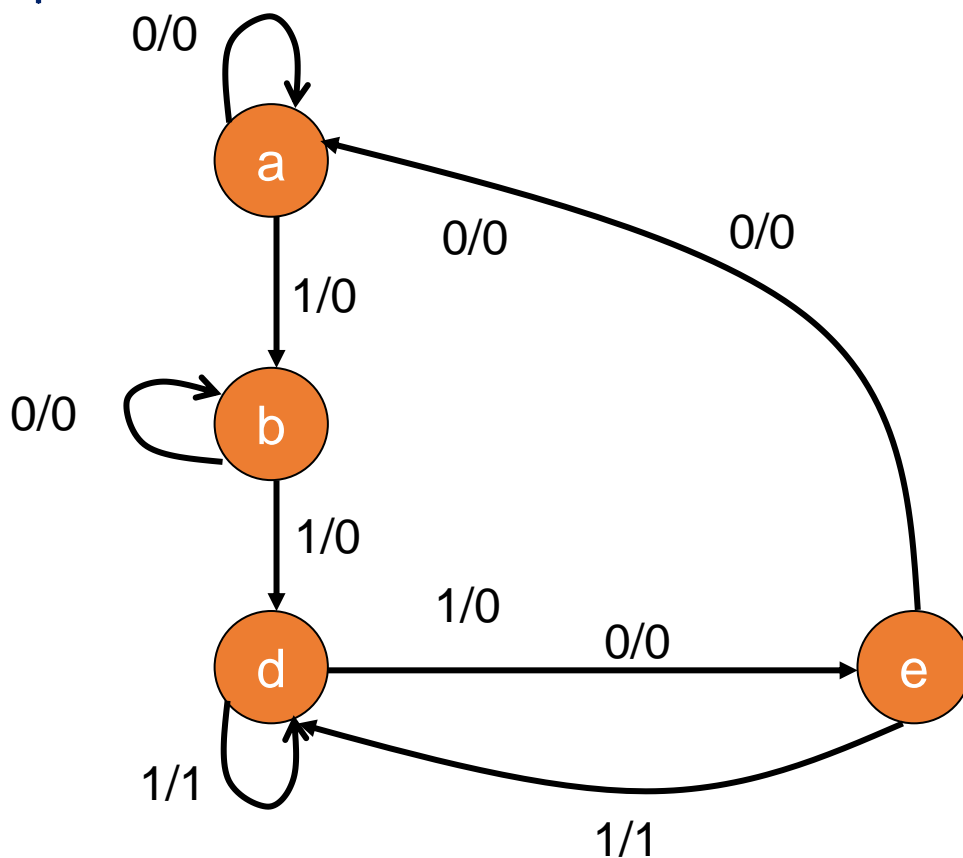

present state	next state		Output	
	x = 0	x = 1	x = 0	x = 1
a	a	b	0	0
b	b	d	0	0
d	e	d	0	1
e	a	d	0	1

We need two flip-flops

state	a	a	b	b	d	e	d	d	e	a	a		
input	0	1	0	1	0	1	1	0	0	0	0		
output	0	0	0	0	0	1	1	0	0	0			



State Assignments 1/4

- We have to assign binary values to each state
- If we have m states, then we need a code with minimum n bits, where $n = \lceil \log_2 m \rceil$
- There are different ways of encoding
- Example: Eight states: $S_0, S_1, S_2, S_3, S_4, S_5, S_6, S_7$

State	Binary	Gray	One-hot
S_0	000	000	00000001
S_1	001	001	00000010
S_2	010	011	00000100
S_3	011	010	00001000
S_4	100	110	00010000
S_5	101	111	00100000
S_6	110	101	01000000
S_7	111	100	10000000



State Assignments 2/4


- The circuit complexity depends on the state encoding (assignment) scheme
- Previous example: binary state encoding

present state	next state		Output	
	x = 0	x = 1	x = 0	x = 1
(a) 00	00	01	0	0
(b) 01	01	10	0	0
(d) 10	11	10	0	1
(e) 11	00	10	0	1



State Assignments 3/4

- Gray encoding

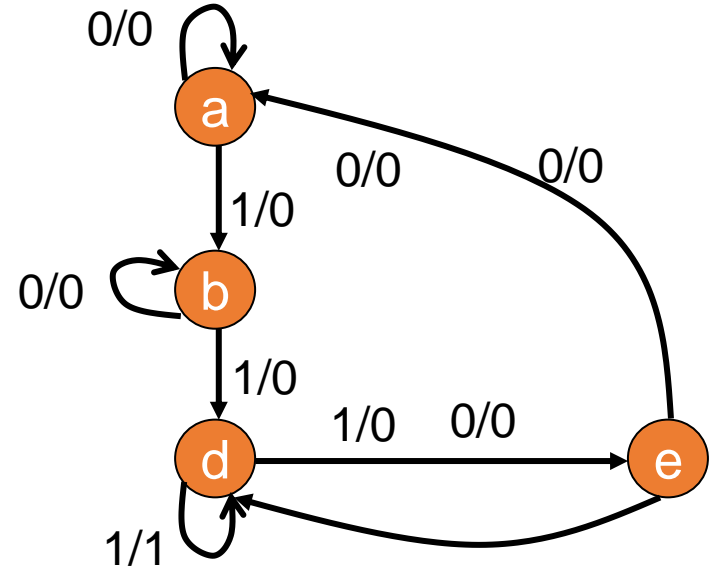

present state	next state		Output	
	x = 0	x = 1	x = 0	x = 1
(a) 00	00	01	0	0
(b) 01	01	11	0	0
(d) 11	10	11	0	1
(e) 10	00	11	0	1



State Assignments 4/4

- One-hot encoding

present state	next state		Output	
	x = 0	x = 1	x = 0	x = 1
(a) 0001	0001	0010	0	0
(b) 0010	0010	0100	0	0
(d) 0100	1000	0100	0	1
(e) 1000	0001	0100	0	1

Designing Sequential Circuits

- Combinational circuits
 - can be designed given a truth table
- Sequential circuits
 - We need,
 - state diagram or
 - state table
 - Two parts
 - flip-flops: number of flip-flops is determined by the number of states
 - combinational part:
 - output equations
 - flip-flop input equations



Design Process

- Once we know the number of flip-flops, design process is reduced to design process of combinational circuits
- Therefore, we can apply the techniques of combinational circuit design
- The design steps
 1. Given a verbal description of desired operation, derive state diagram
 2. Reduce the number of states if necessary and possible
 3. State assignment




Design Steps (cont.)

4. Obtain the encoded state table
 5. Derive the simplified flip-flop input equations
 6. Derive the simplified output equations
 7. Draw the logic diagram
- Example: Verbal description
 - “we want a (sequential) circuit that detects three or more consecutive 1’s in a string of bits”
 - Input: string of bits of any length
 - Output:
 - “1” if the circuit detects **the** pattern in the string
 - “0” otherwise



Example: State Diagram

- Step 1: Derive the state diagram

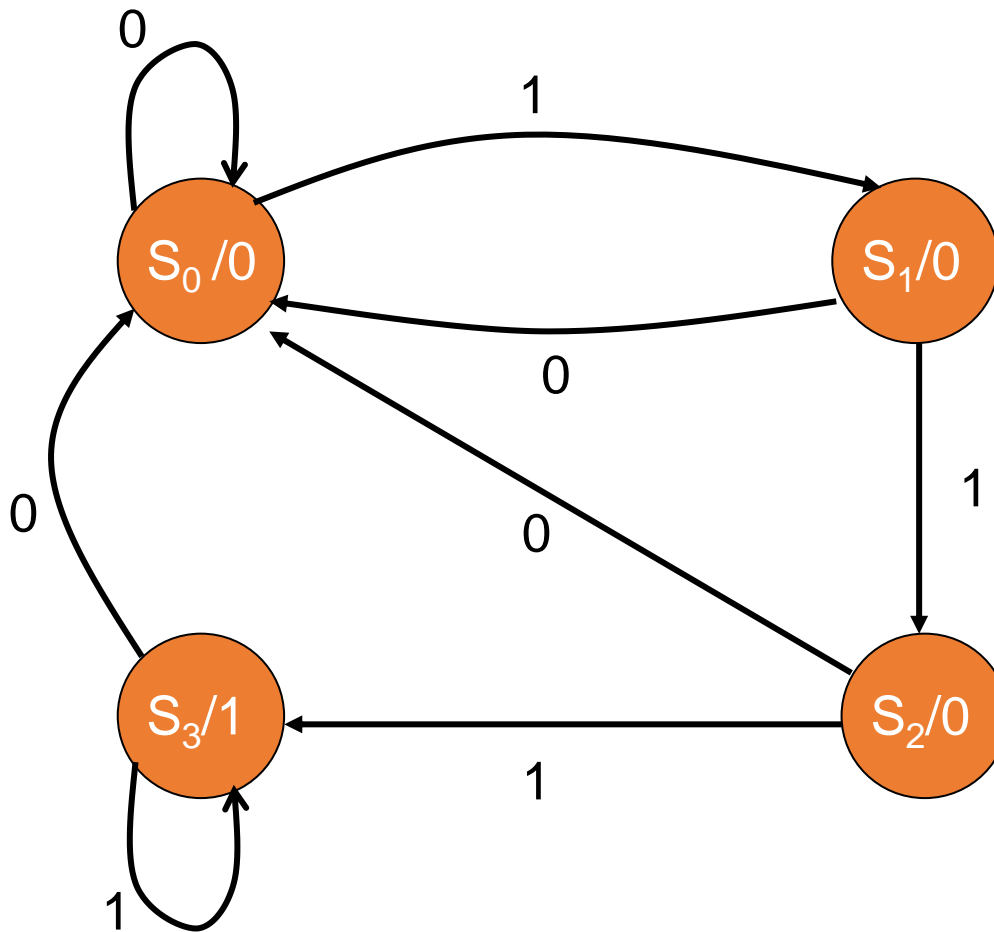


Moore Machine

[Handwritten signature]

Synthesis with D Flip-Flops 1/5

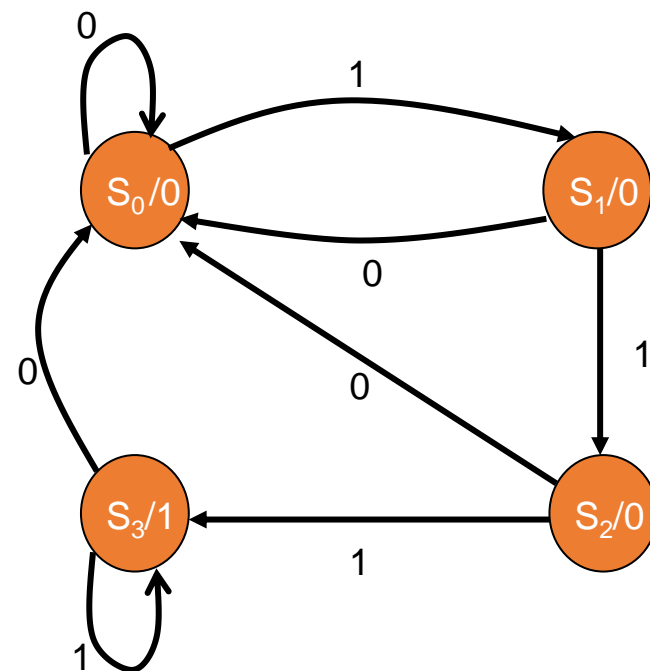
- The number of flip-flops
 - Four states
 - **2 or 4** flip-flops
- State reduction
 - not possible in this case
- State Assignment
 - Use binary encoding
 - $s_0 \rightarrow 00$
 - $s_1 \rightarrow 01$
 - $s_2 \rightarrow 10$
 - $s_3 \rightarrow 11$



Synthesis with D Flip-Flops 2/5

- Step 4: Obtain the state table

Present state		Input	Next state		Output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

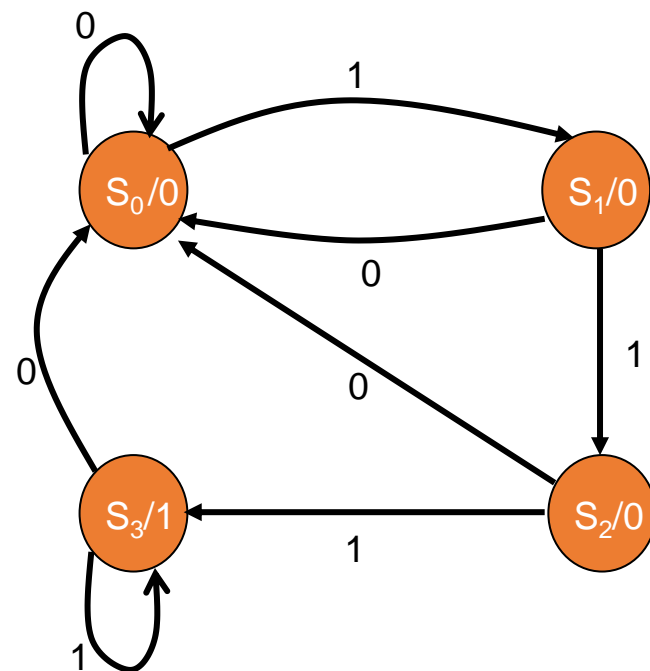

Synthesis with D Flip-Flops 3/5

- Step 5: Choose the flip-flops
 - D flip-flops
- Step 6: Derive the simplified flip-flop input equations
 - Boolean expressions for D_A and D_B

Present state		Input	Next state		Output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

		Bx			
		00	01	11	10
A	0	0	0	1	0
	1	0	1	1	0

$$D_A = Ax + Bx$$

Synthesis with D Flip-Flops 3/5

Present state		Input	Next state		Output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

A \ Bx				
	00	01	11	10
0	0	1	0	0
1	0	1	1	0

$$D_B = Ax + B'x$$

A \ Bx				
	00	01	11	10
0	0	0	0	0
1	0	0	1	1

$$y = AB$$

- Step 7: Derive the simplified output equations
 - Boolean expressions for y.


Synthesis with D Flip-Flops 5/5

- Step 8: Draw the logic diagram

$$D_A = Ax + Bx$$


$$D_B = Ax + B'x$$

$$y = AB$$

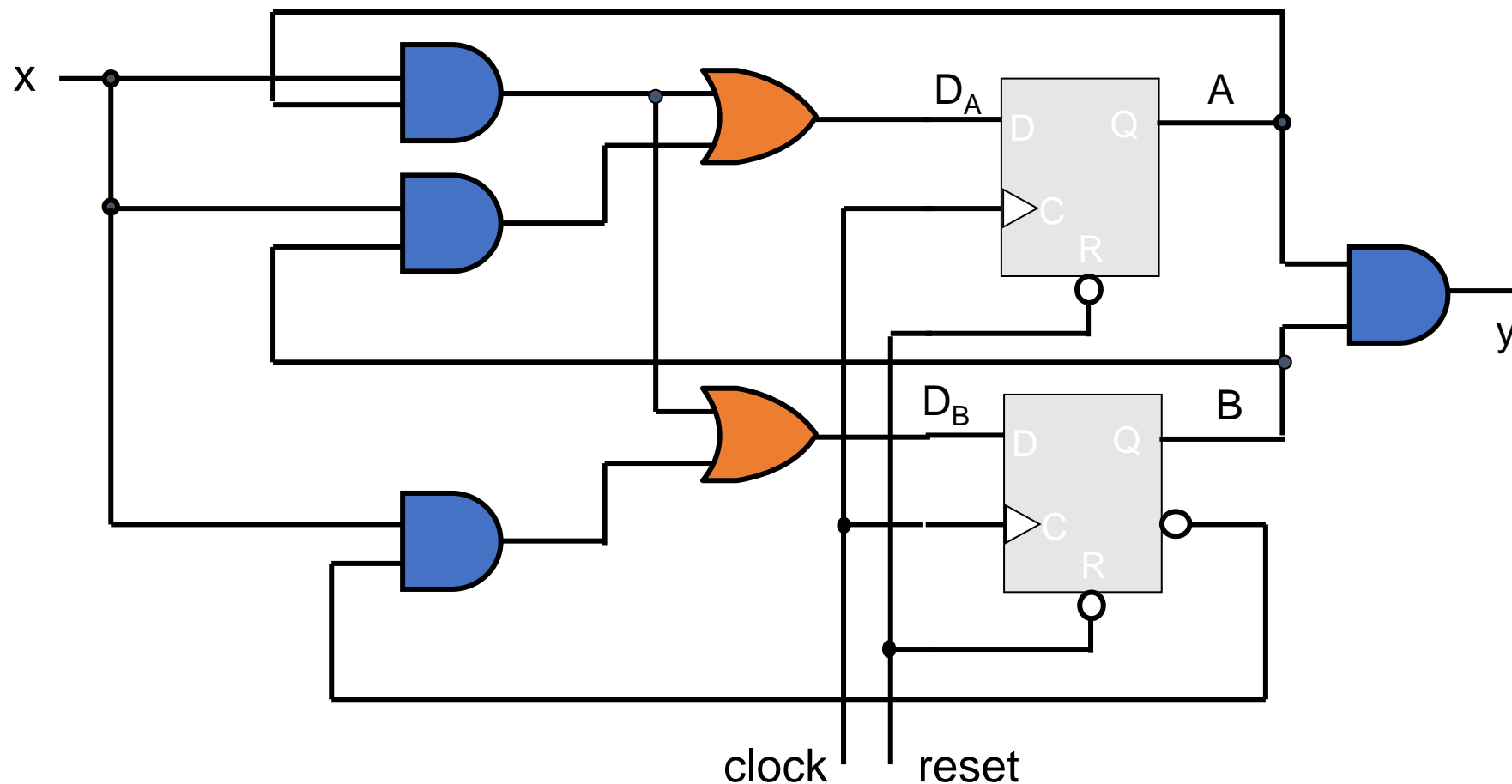

Synthesis with T Flip-Flops 1/4

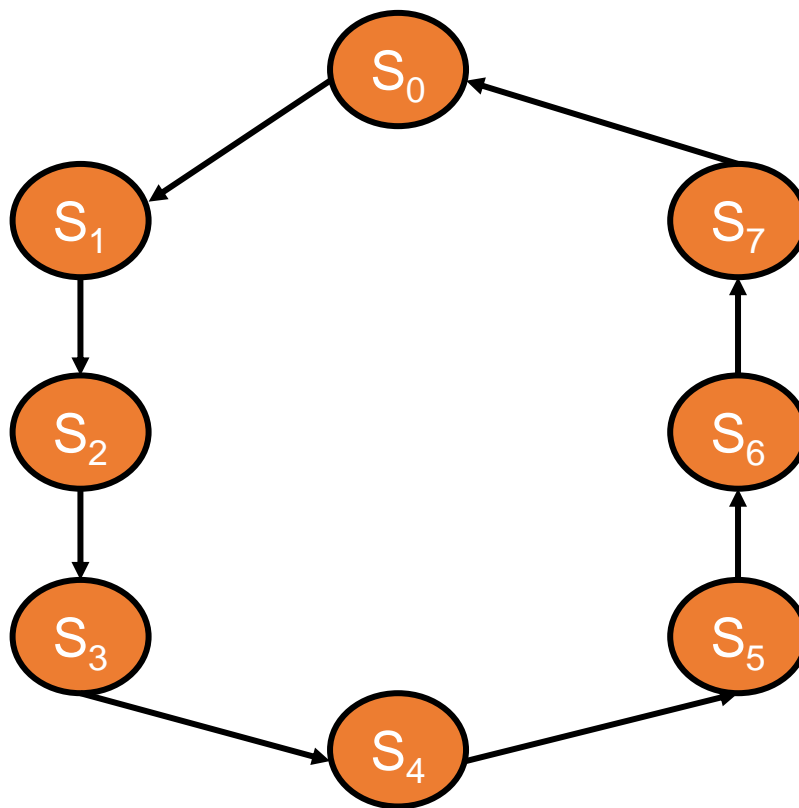- Example: 3-bit binary counter with T flip-flops
 - $0 \rightarrow 1 \rightarrow 2 \rightarrow \dots \rightarrow 7 \rightarrow 0 \rightarrow 1 \rightarrow 2$



How many flip-flops?

State assignments:

- $S_0 \rightarrow 000$
- $S_1 \rightarrow 001$
- $S_2 \rightarrow 010$
- ...
- $S_7 \rightarrow 111$

State Diagram

Synthesis with T Flip-Flops 2/4

■ State Table

present state			next state			FF inputs		
A_2	A_1	A_0	A_2	A_1	A_0	T_2	T_1	T_0
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

Synthesis with T Flip-Flops 3/4

Present state			FF inputs		
A_2	A_1	A_0	T_2	T_1	T_0
0	0	0	0	0	1
0	0	1	0	1	1
0	1	0	0	0	1
0	1	1	1	1	1
1	0	0	0	0	1
1	0	1	0	1	1
1	1	0	0	0	1
1	1	1	1	1	1

- Flip-Flop input equations

		$A_1 A_0$			
		00	01	11	10
A_2	0	0	0	1	0
	1	0	0	1	0

$$T_2 = A_1 A_0$$

$$T_0 = 1$$

		$A_1 A_0$			
		00	01	11	10
A_2	0	0	1	1	0
	1	0	1	1	0

$$T_1 = A_0$$


Synthesis with T Flip-Flops 4/4

■ Circuit

$$T_2 = A_1 A_0$$

$$T_1 = A_0$$

$$T_0 = 1$$

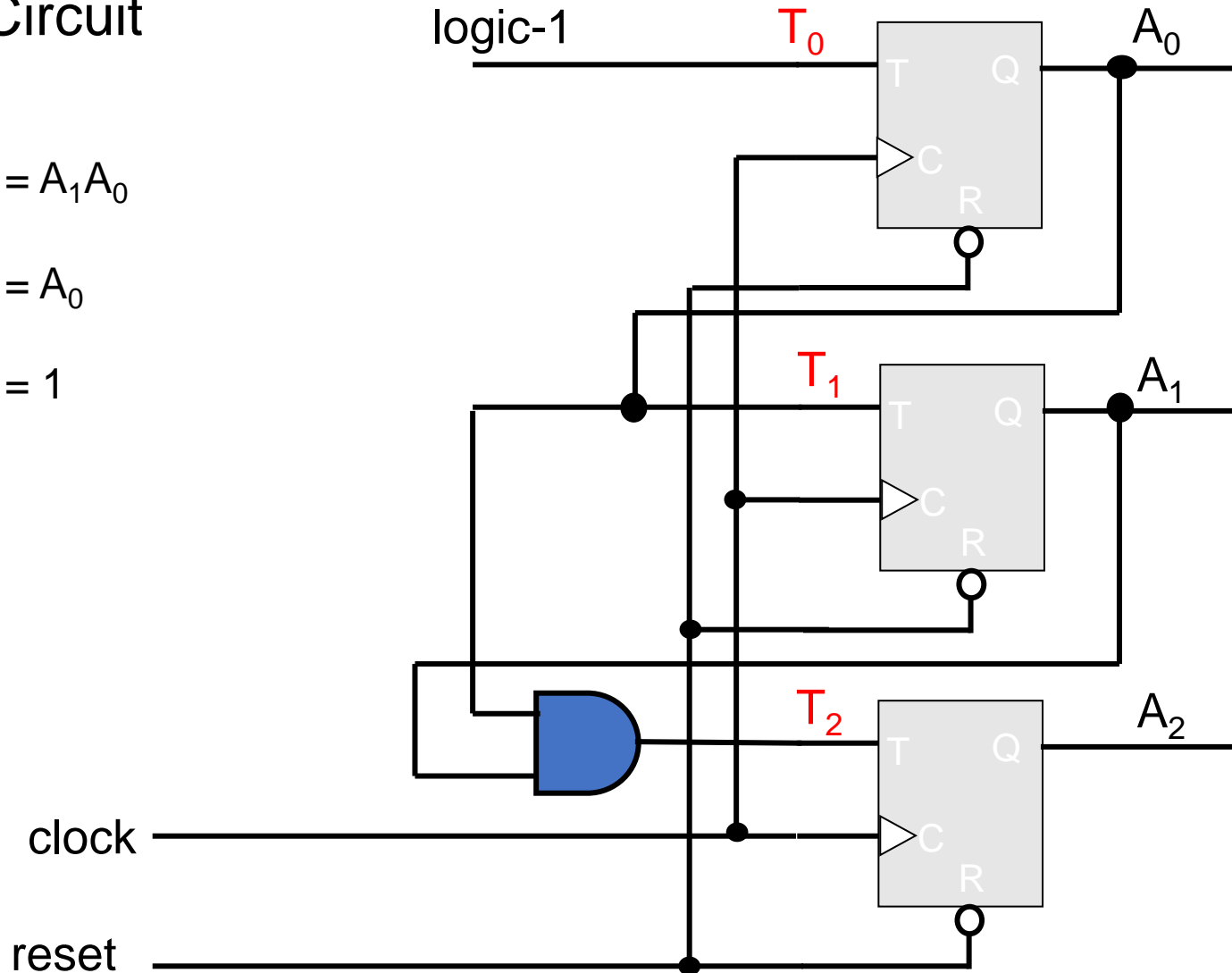

Synthesis with JK Flip-Flops 1/4

$$Q(t+1) = JQ' + K'Q$$

J	K	Q(t+1)
0	0	Q
0	1	0
1	0	1
1	1	Q'

■ State Table & JK FF Inputs

Present state		Input	next state		Flip-flop inputs			
A	B	x	A	B	J _A	K _A	J _B	K _B
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1

Synthesis with JK Flip-Flops 2/4

- Optimize the flip-flop input equations

A	B	x	Flip-flop inputs					
			A(t+1)	B(t+1)	J _A	K _A	J _B	K _B
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1

A	Bx			
	00	01	11	10
0	0	0	0	1
1	X	X	X	X

$$J_A = Bx'$$

A	Bx			
	00	01	11	10
0	0	1	X	X
1	0	1	X	X

$$J_B = x$$

Synthesis with JK Flip-Flops 3/4

A	B	x	Flip-flop inputs					
			A(t+1)	B(t+1)	J _A	K _A	J _B	K _B
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1

A	Bx			
	00	01	11	10
0	X	X	X	X
1	0	0	1	0

$$K_A = Bx$$


A	Bx			
	00	01	11	10
0	X	X	0	1
1	X	X	1	0

$$K_B = (A \oplus x)'$$




- Logic diagram

$$K_B = (A \oplus x)'$$

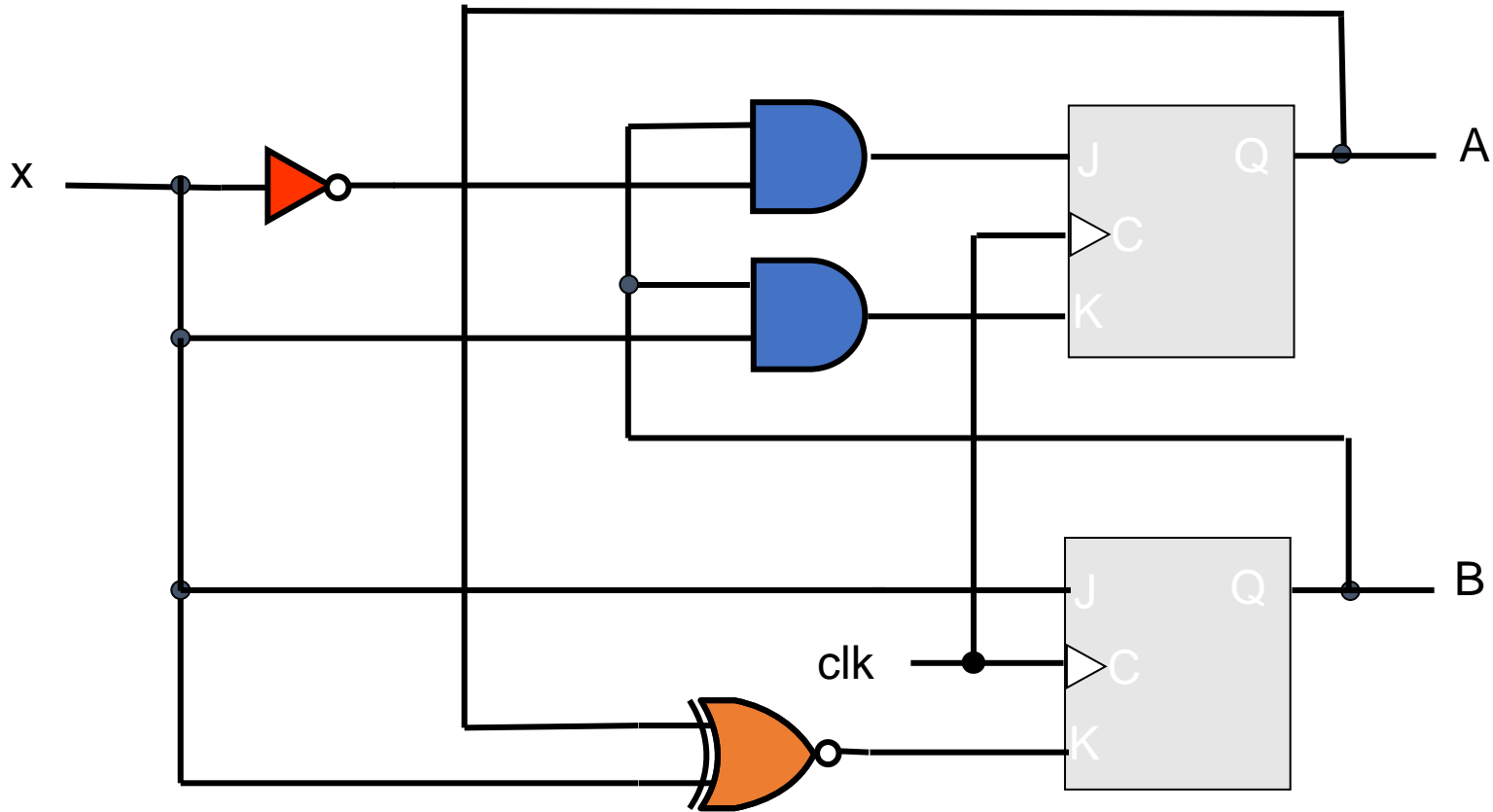

Unused States

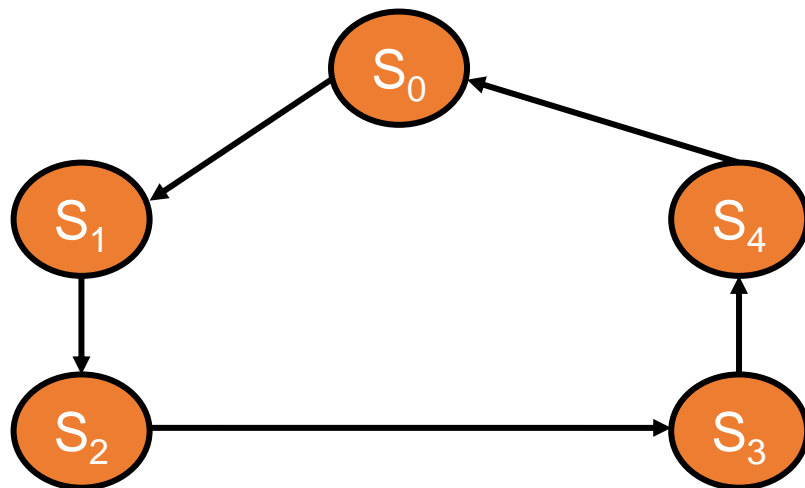

Modulo-5 counter

Present State			Next State		
A	B	C	A	B	C
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	0	0	0

Example: Unused States 1/4

Present State			Next State		
A	B	C	A	B	C
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	0	0	0

A \ BC				
	00	01	11	10
0	0	0	1	0
1	0	X	X	X

$$A(t+1) = BC$$

A \ BC				
	00	01	11	10
0	0	1	0	1
1	0	X	X	X

$$B(t+1) = B'C + BC'$$

A \ BC				
	00	01	11	10
0	1	0	0	1
1	0	X	X	X

$$C(t+1) = A'C'$$


Example: Unused States 2/4

Present State			Next State		
A	B	C	A	B	C
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	0	1	0
1	1	0	0	1	0
1	1	1	1	0	0

$$A(t+1) = BC$$

$$B(t+1) = B \oplus C$$

$$C(t+1) = A'C'$$

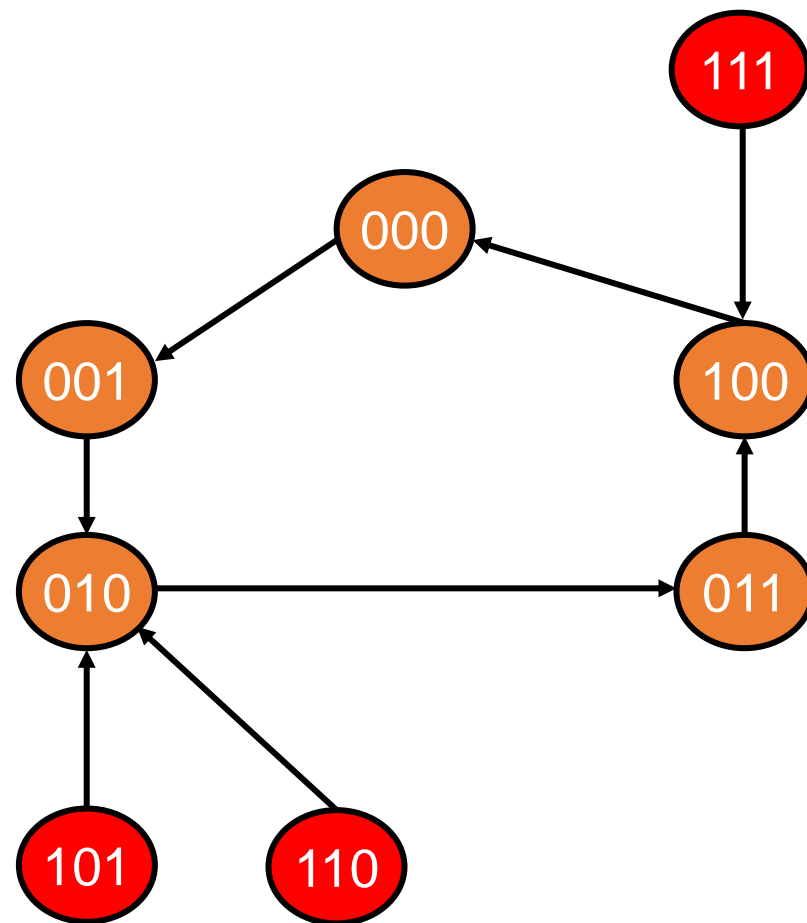

Example: Unused States 3/4

- Not using don't care conditions

Present State			Next State		
A	B	C	A	B	C
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	0	0	0

		BC			
A		00	01	11	10
	0	0	1	0	1
	1	0	0	0	0

$$\begin{aligned} B(t+1) &= A'B'C + A'BC' \\ &= A'(B \oplus C) \end{aligned}$$

		BC			
A		00	01	11	10
	0	0	0	1	0
	1	0	0	0	0


$$A(t+1) = A'BC$$

		BC			
A		00	01	11	10
	0	1	0	0	1
	1	0	0	0	0

$$C(t+1) = A'C'$$

Example: Unused States 4/4

Present State			Next State		
A	B	C	A	B	C
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	0	0	0
1	1	0	0	0	0
1	1	1	0	0	0

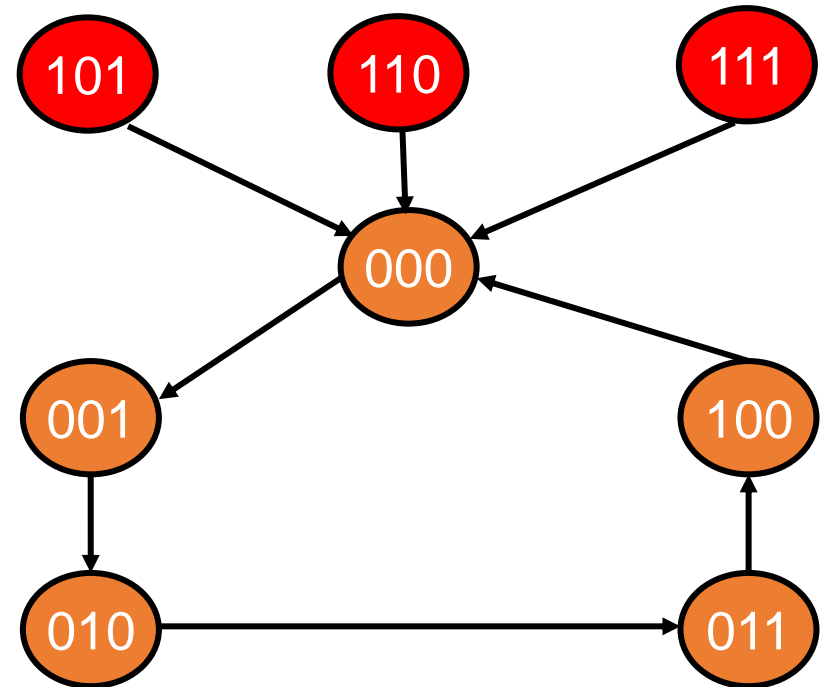


$$A(t+1) = A'BC$$

$$B(t+1) = A'(B \oplus C)$$


$$C(t+1) = A'C'$$

Sequential Circuit Timing 1/3

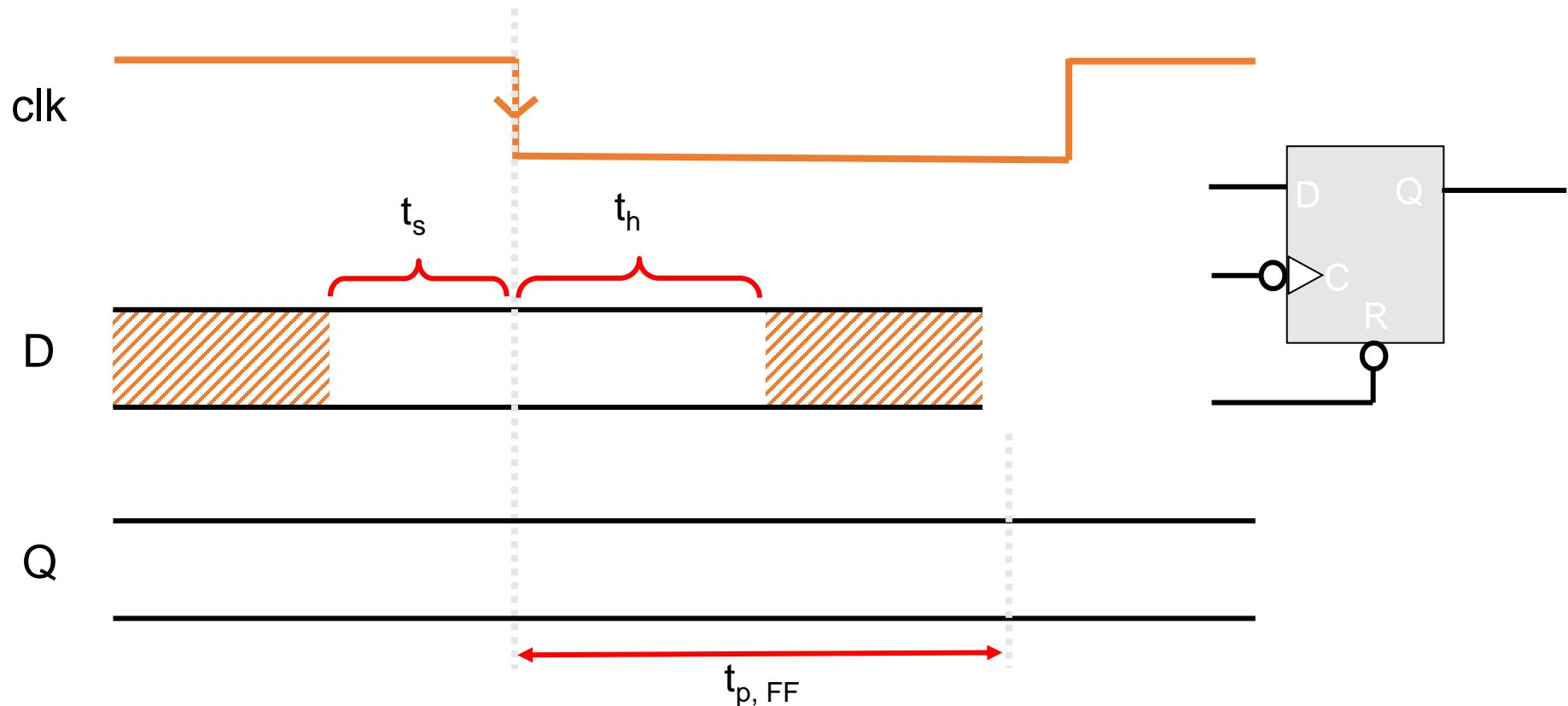
- It is important to analyze the timing behavior of a sequential circuit
 - Ultimate goal is to determine the maximum clock frequency



Sequential Circuit Timing 2/3

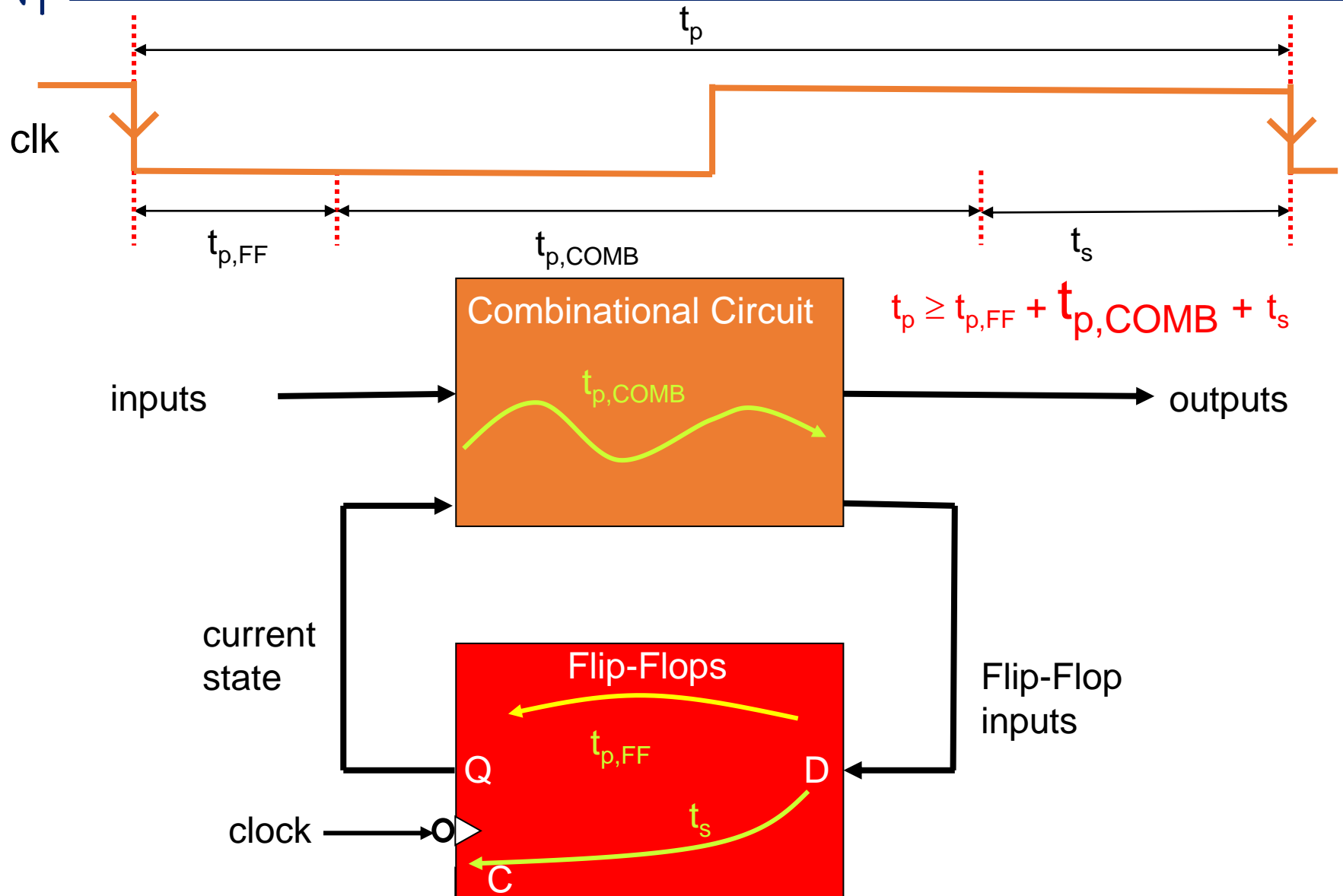


Sequential Circuit Timing 2/3

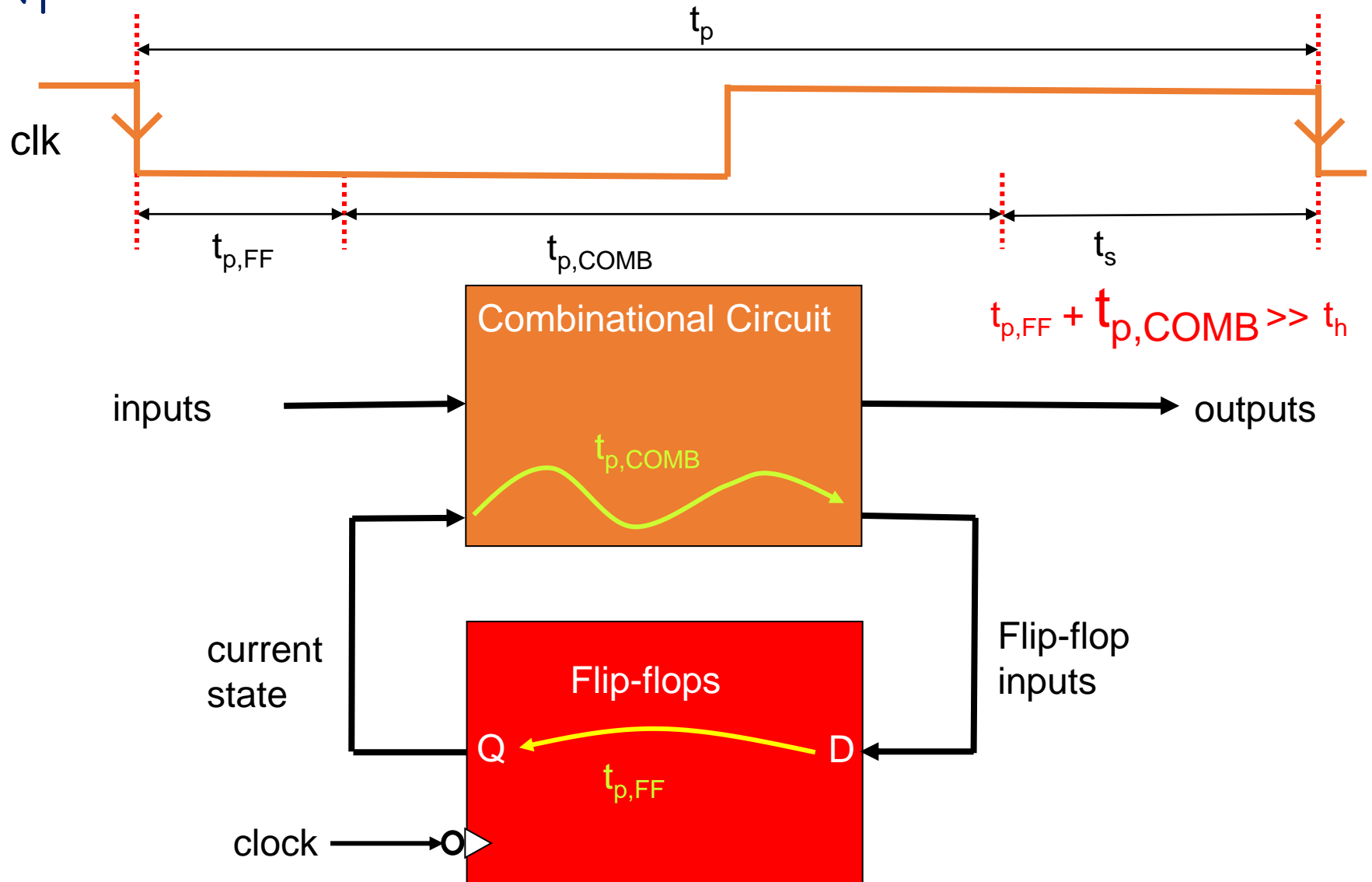


Sequential Circuit Timing 3/3

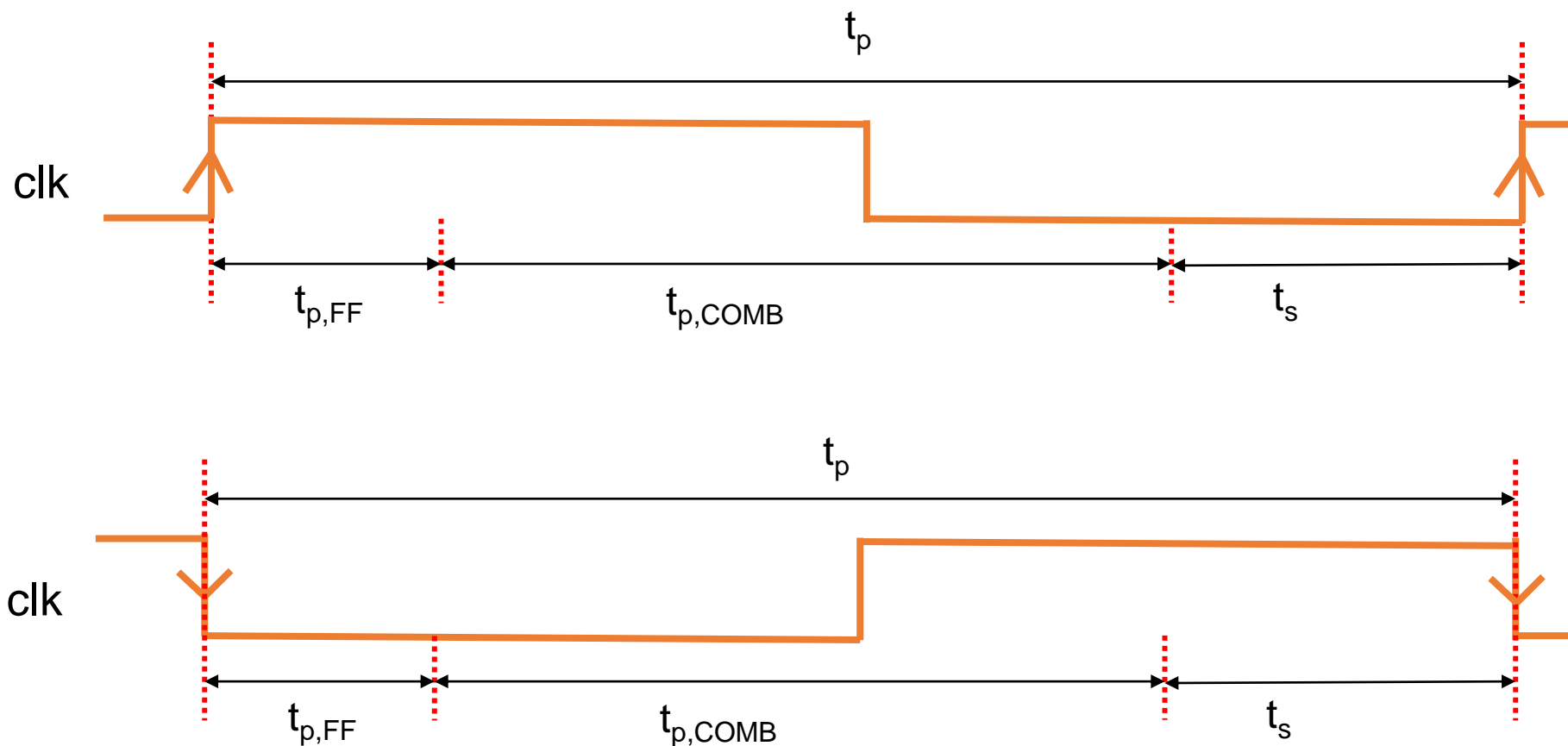- Minimum clock period (or maximum clock frequency)





Example: Counter

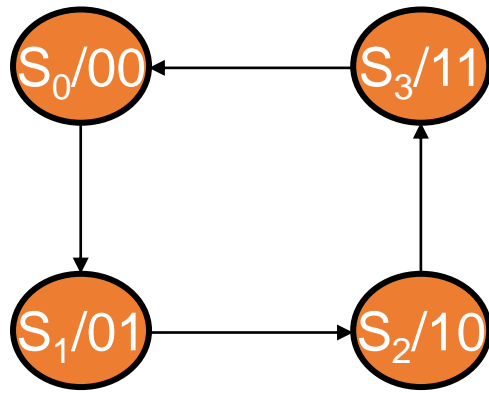

$$t_{p,XOR} = 2.0 \text{ ns}$$


$$t_{p,FF} = 2.0 \text{ ns}$$

$$t_s = 1.0 \text{ ns}$$

$$t_p = t_{p,FF} + t_{p,XOR} + t_s = 2.0 + 2.0 + 1.0 = 5.0 \text{ ns}$$

$$f_{\max} = 1/t_p = 1/(5.0 \times 10^{-9}) \approx 200 \text{ MHz}$$

Binary encoding

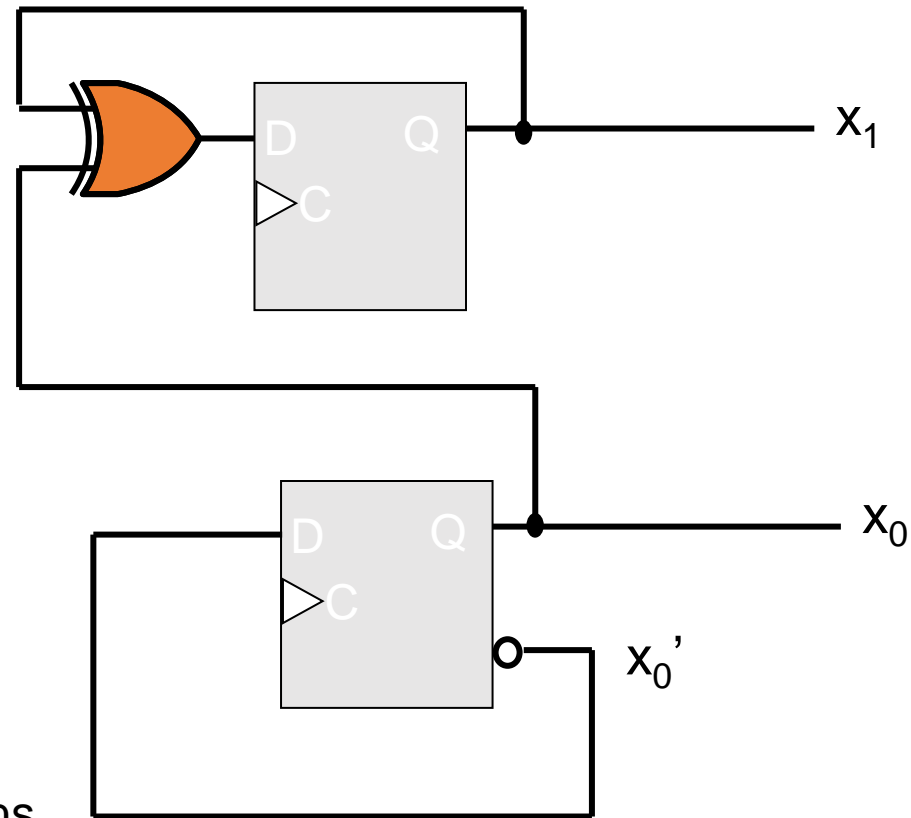

Example: One-Hot-Encoding

$S_0 \rightarrow 0001$

$S_1 \rightarrow 0010$

$S_2 \rightarrow 0100$


$S_3 \rightarrow 1000$

$t_{p,FF} = 2.0 \text{ ns}$


$t_s = 1.0 \text{ ns}$

$t_p = t_{p,FF} + t_s = 2.0 + 1.0 = 3.0 \text{ ns}$

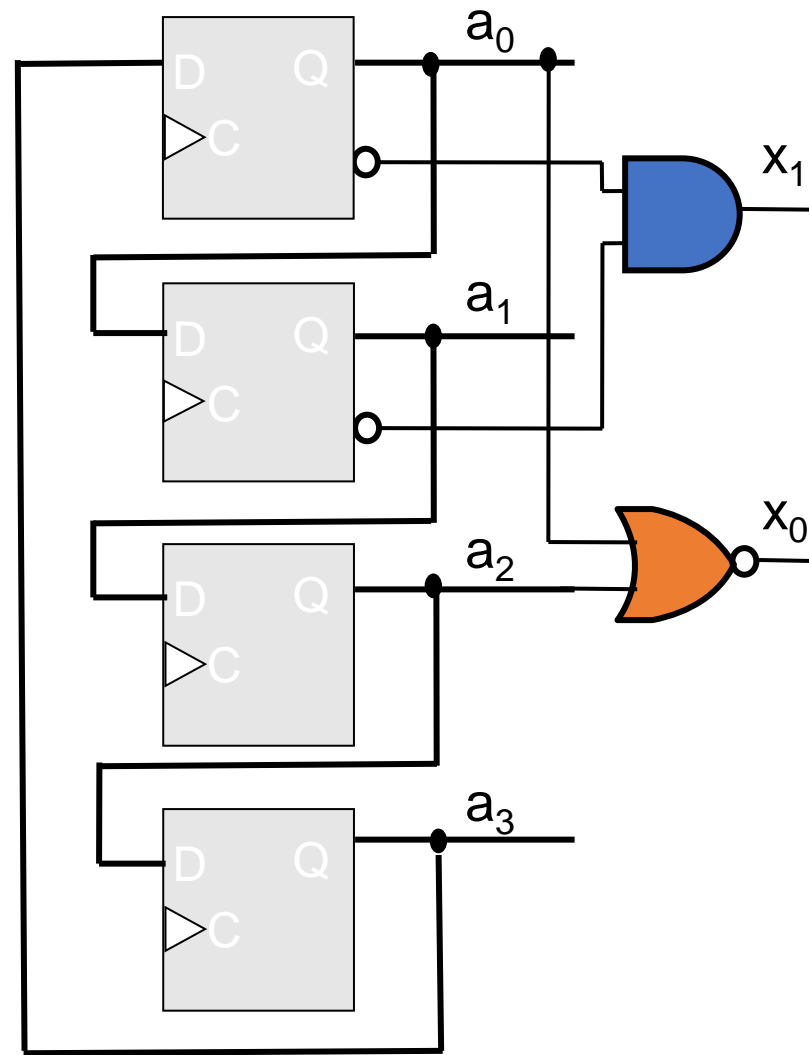$f_{\max} = 1/t_p = 1/(3.0 \times 10^{-9}) \approx 333 \text{ MHz}$



Example: Sequential Circuit Timing

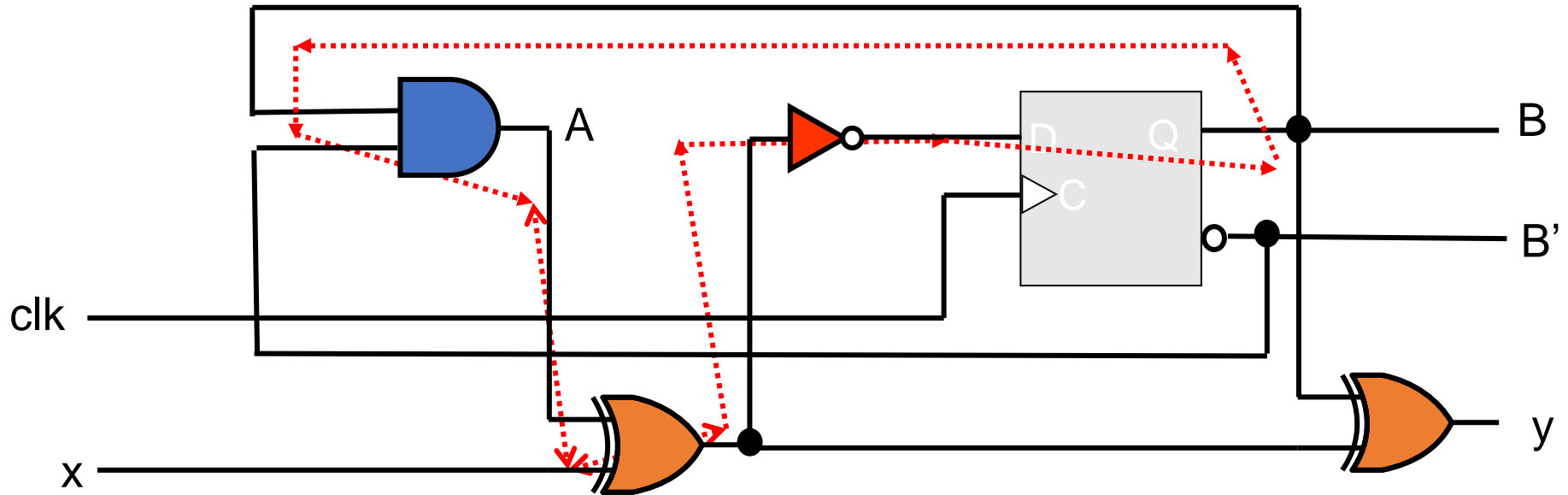

$$t_{p,\text{NOT}} = 0.5 \text{ ns}$$

$$t_{p,\text{XOR}} = 2.0 \text{ ns}$$

$$t_{p,\text{FF}} = 2.0 \text{ ns}$$


$$t_{p,\text{AND}} = t_s = 1.0 \text{ ns}$$

$$t_h = 0.25 \text{ ns}$$

Find the longest path delay from positive clock edge to the flip-flop input

$$\begin{aligned} & t_{p,\text{FF}} + t_{p,\text{AND}} + t_{p,\text{XOR}} + t_{p,\text{NOT}} \\ &= 2.0 + 1.0 + 2.0 + 0.5 = 5.5 \text{ ns} \end{aligned}$$

Example: Sequential Circuit Timing

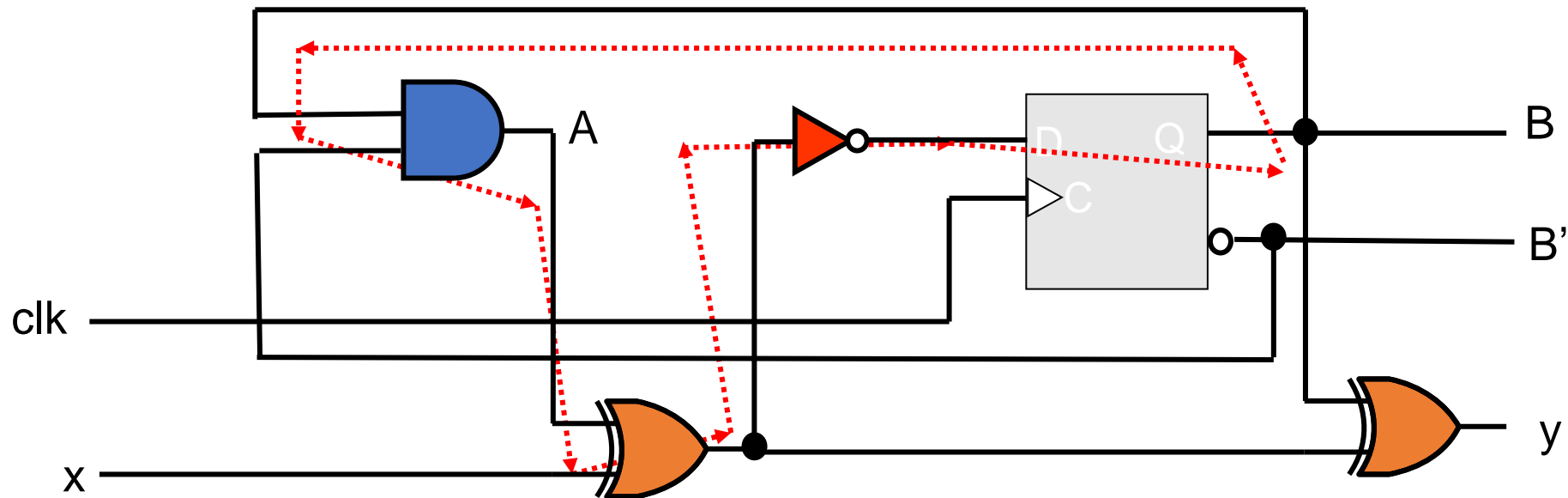

$$t_{p,NOT} = 0.5 \text{ ns}$$

$$t_{p,XOR} = 2.0 \text{ ns}$$

$$t_{p,FF} = 2.0 \text{ ns}$$

$$t_{p,AND} = t_s = 1.0 \text{ ns}$$

$$t_h = 0.25 \text{ ns}$$

Determine the maximum frequency of operation of the circuit in megahertz

$$\begin{aligned} t_p &= t_{p,FF} + t_{p,AND} + t_{p,XOR} + t_{p,NOT} + ? \\ &= 2.0 + 1.0 + 2.0 + 0.5 + 1.0 = 6.5 \text{ ns} \end{aligned}$$

$$f_{\max} = 1/t_p = 1/(6.5 \times 10^{-9}) \approx 154 \text{ MHz}$$